

FPGAs Architecture

Andrew Lukefahr


Portions borrowed from:

http://www.gstitt.ece.ufl.edu/courses/fall15/eel4720_5721/index.html

Topics

- FPGA internals
- Synthesis Process

Review: RAM

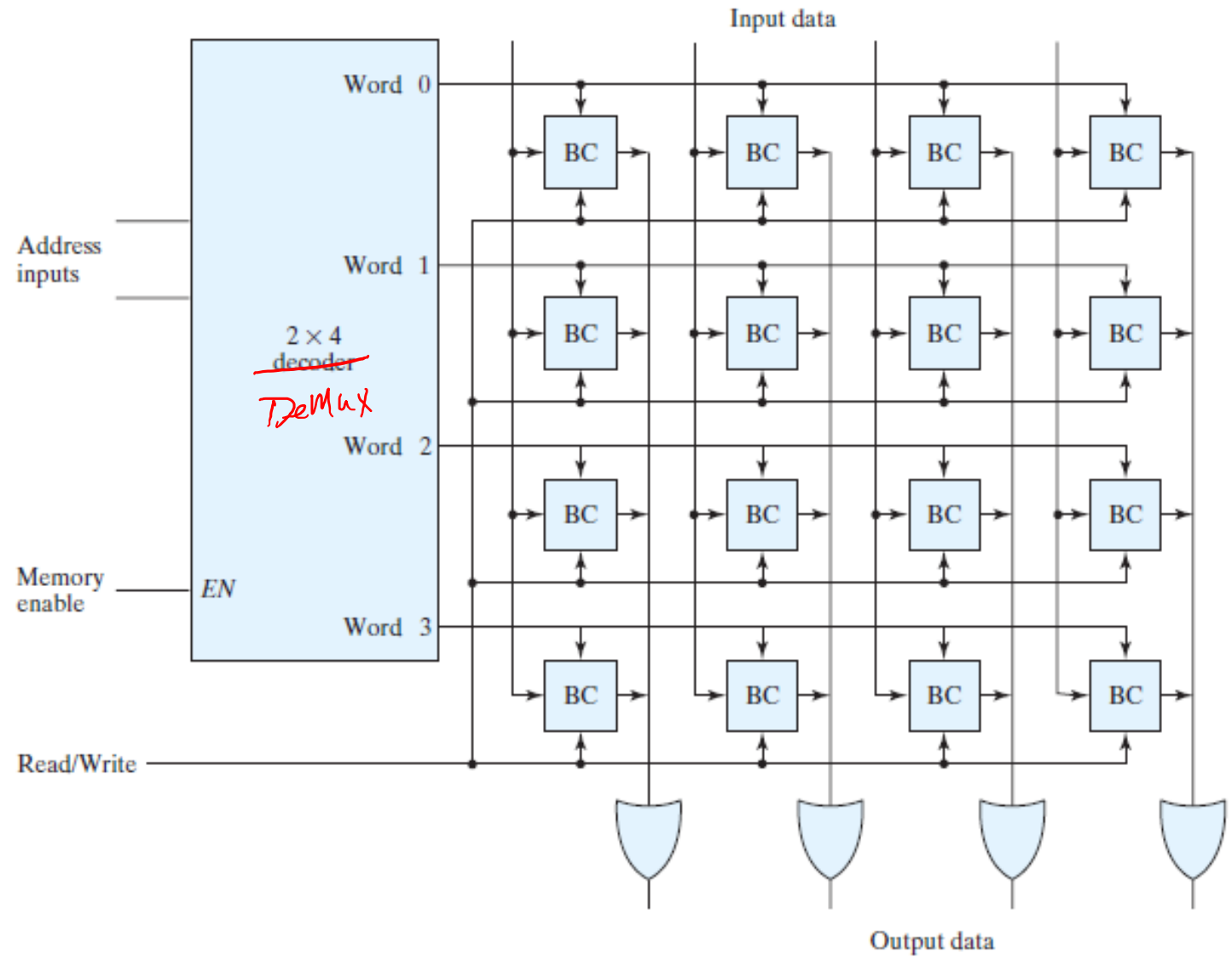

Look-Up Table (LUT)

- DON'T compute a Boolean equation
- DO pre-compute all solutions in a table
- DO look up the Boolean result in the table

- Examples:

$s = a \wedge b;$


$c = a \& b;$

RAM to LUT


- Can I use a RAM to build a Half-Adder LUT?

$$s = a \oplus b;$$

$$c = a \& b;$$

 

Full-Adder LUT

 

Input			Output	
A	B	Cin	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

LUT size

- Why not a 1000-input,100-output LUT?
- 3 inputs $\Rightarrow 2^3$ rows = 8 rows
- 4 inputs $\Rightarrow 2^4$ rows = 16 rows
- 5 inputs $\Rightarrow 2^5$ rows = 32 rows
- ...
- 64 inputs $\Rightarrow 2^{64}$ rows = 1.85×10^{19} rows
- LUT input size does not scale well.

Divide and Conquer with LUTs

- 3-Bit Full Adder

Sequential Logic

- Problem: How do we handle sequential logic?
 - LUTs cannot contain state
- Solution: Add a Flip-Flop

Configurable Logic Block (CLB)

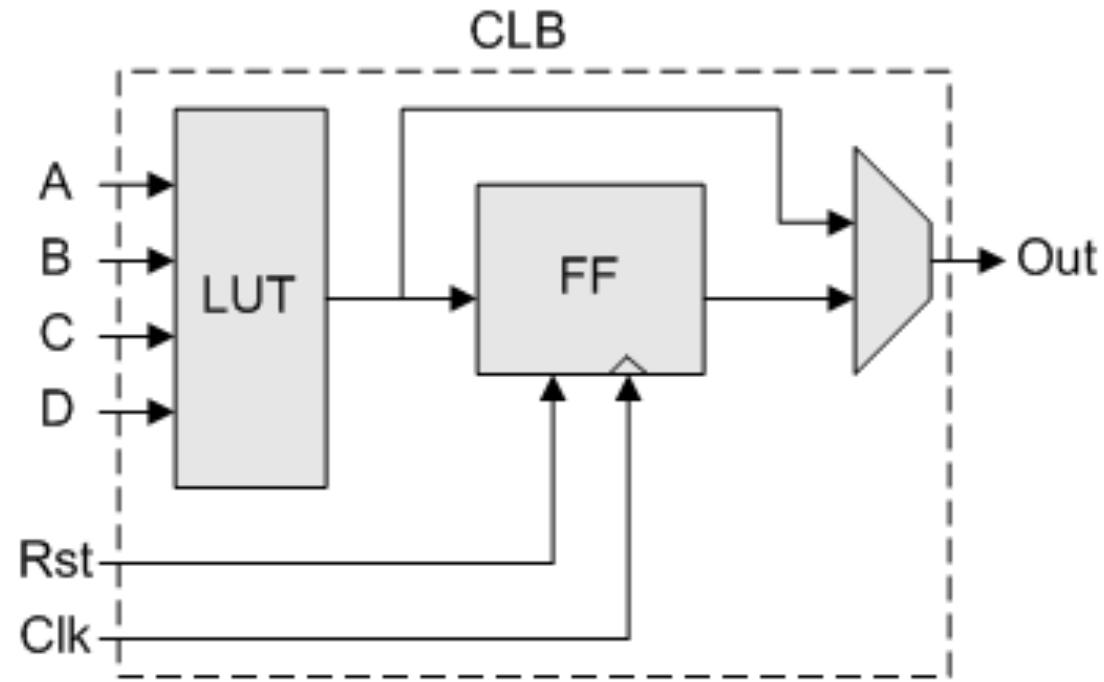


Fig.4 Example of Configurable Logic Cell.

Configurable Logic Block (CLB)

- What if I only want to store a value?



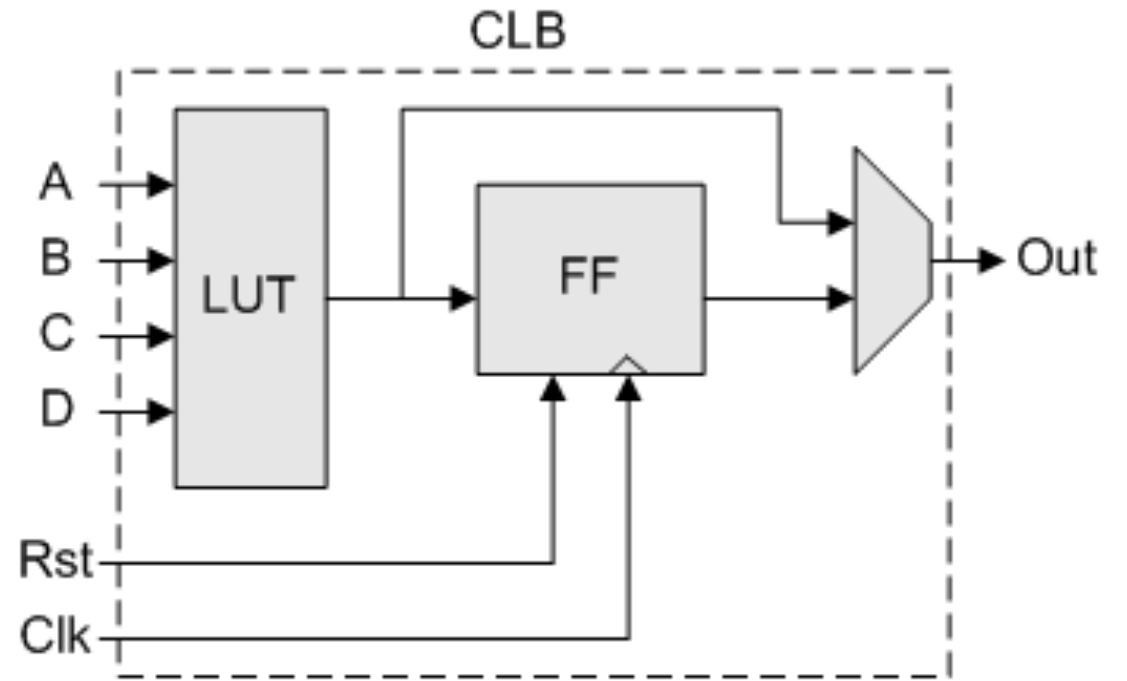


Fig.4 Example of Configurable Logic Cell.


Improved CLB

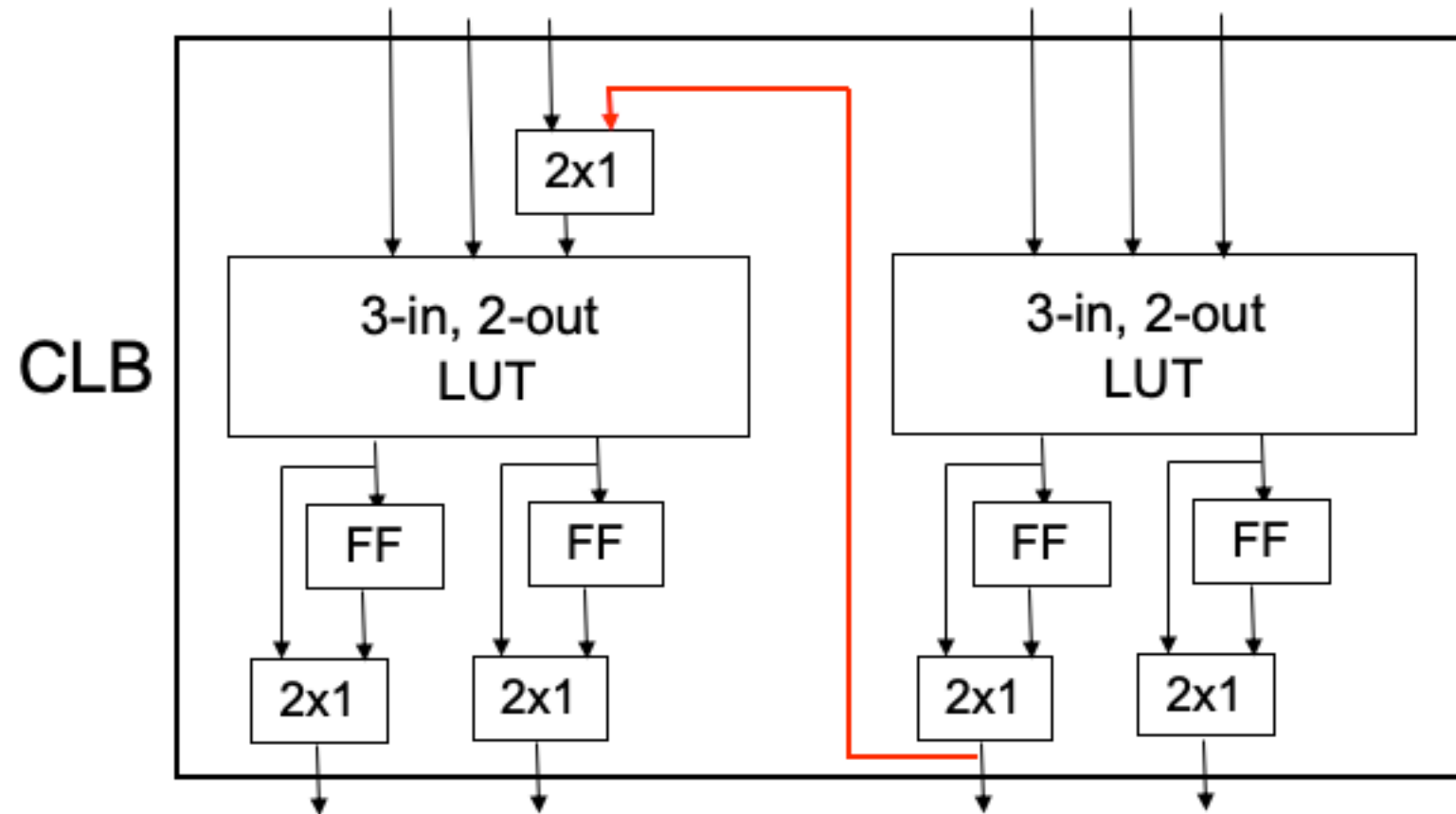

2-Bit Ripple-Carry w/ CLB





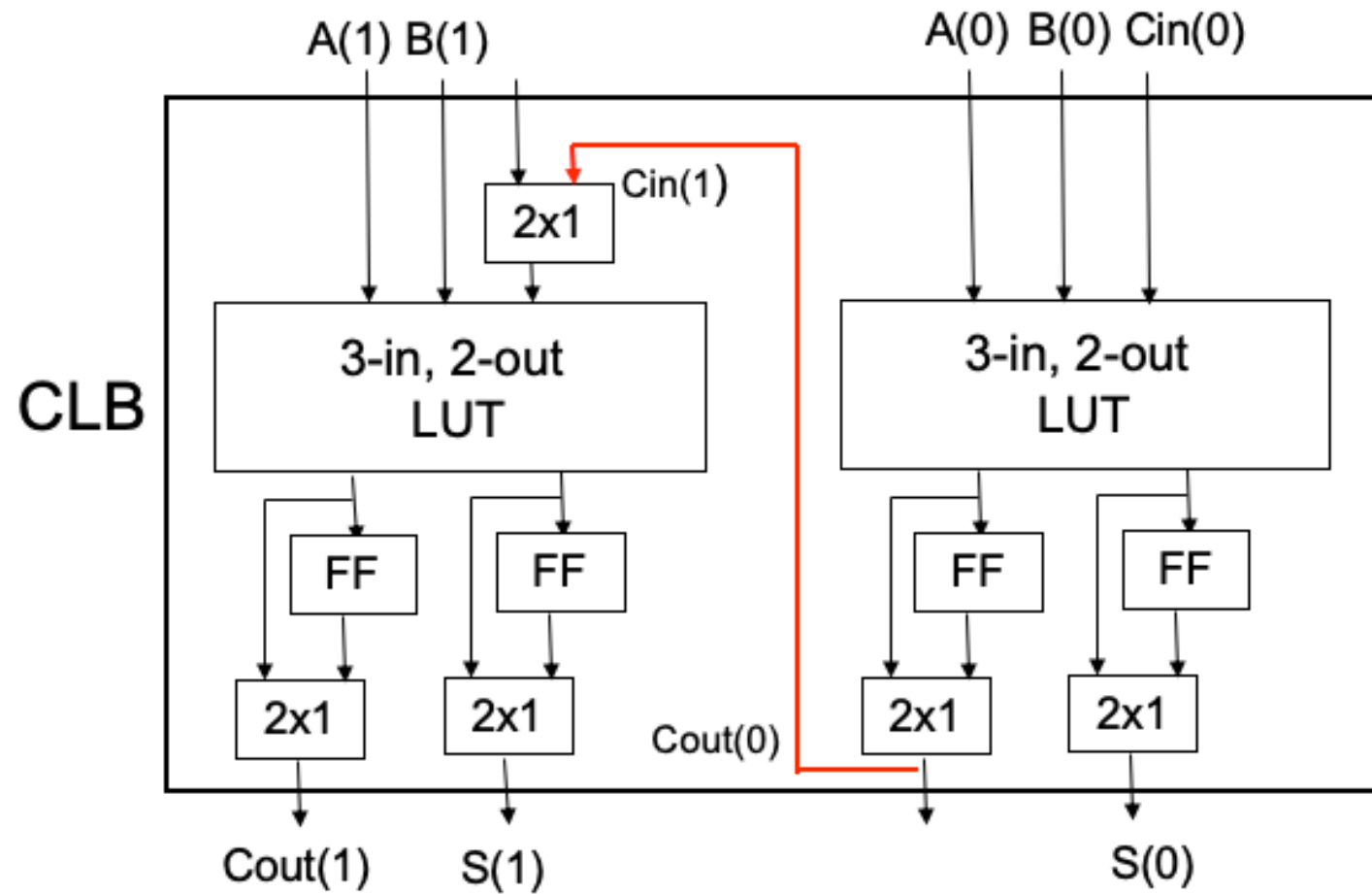


Realistic CLB: Xilinx

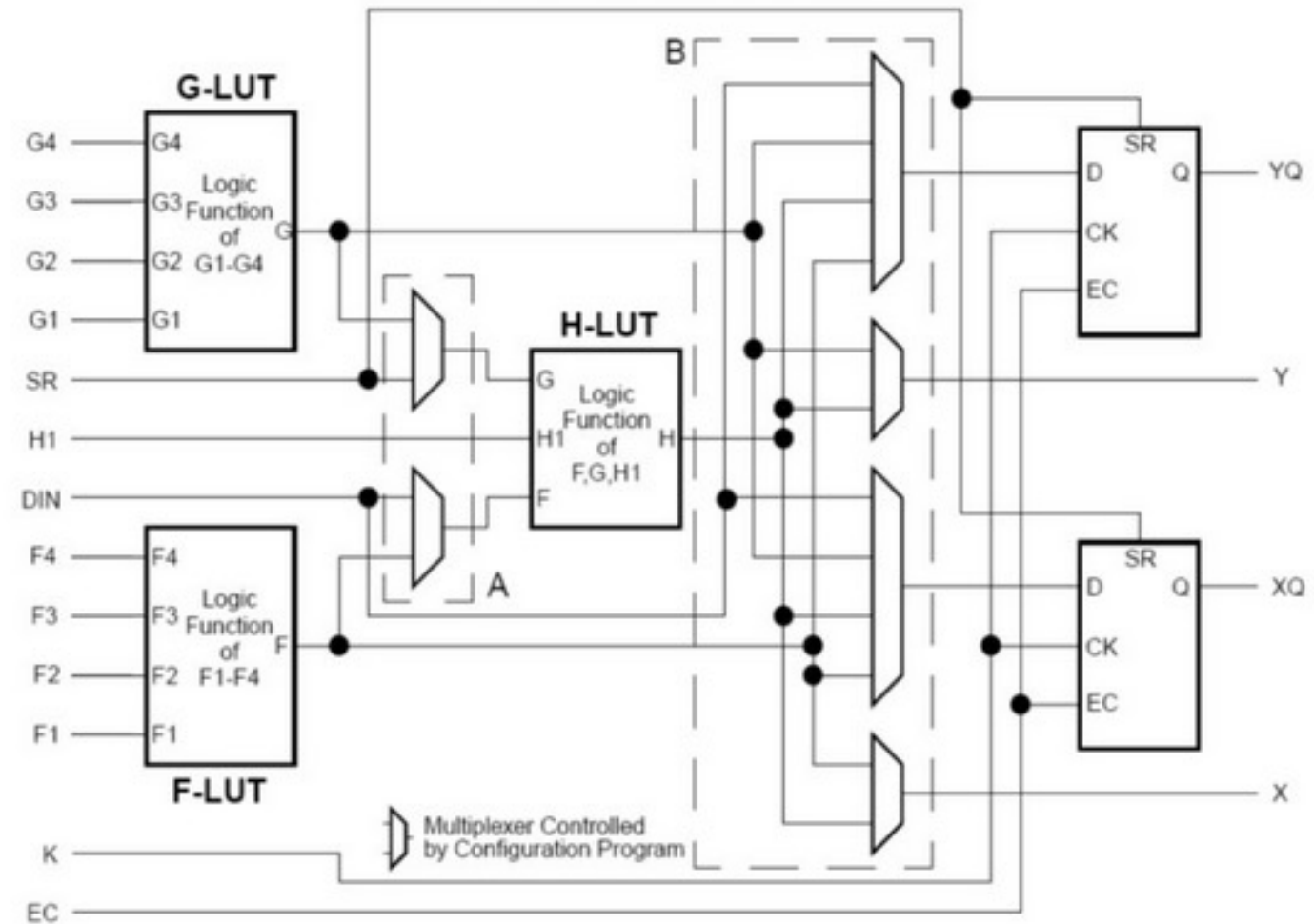


Connecting CLBs

     - Q: How do CLBs talk to each other?
- A: Put wires everywhere!




Connecting CLBs

 - Q: How do CLBs talk to each other?
- A: Put wires everywhere (ok, almost everywhere)!




How to connect CLBs to wires?

 - “Connection box”
 - Device that allows inputs and outputs of CLB to connect to different wires



Connection Box Flexibility

 


Dots represent **possible connections*

How to connect wires to each other?



Switch Box

 - Connects horizontal and vertical routing channels





Switch Box Connections

  - Programmable connections between inputs and outputs




**Not all possible
connections shown*

Switch Box Connections

  

FPGA “Fabric”


- 2D array of CLBs + interconnects

 


- Am I missing anything?

Block RAM

 
- Special blocks of just RAM
- Big CLBs without LUTs




DSPs

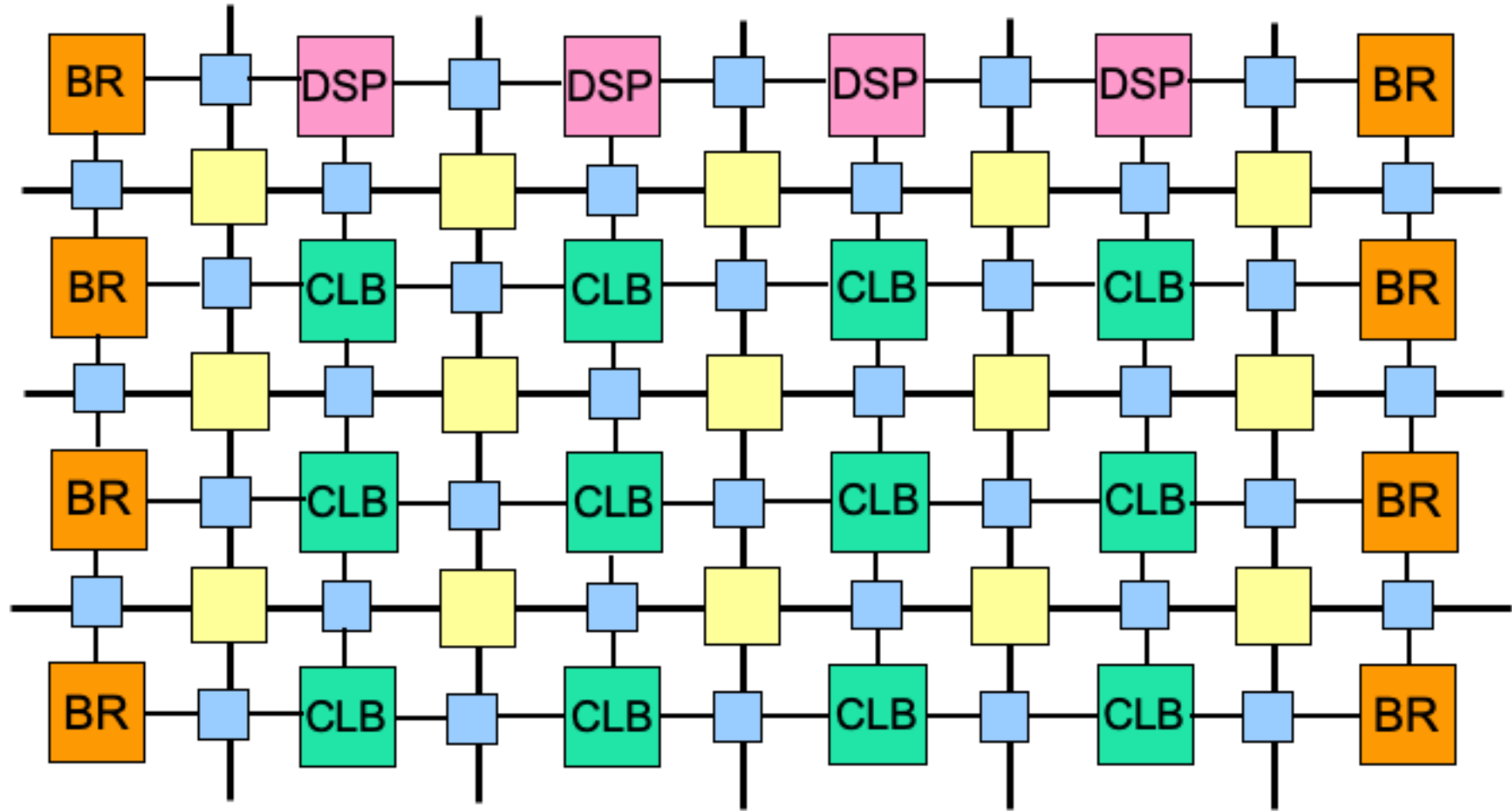


Input/Output (IO)

 

2-bit ROM of AND + OR

 

4 x 4 static RAM

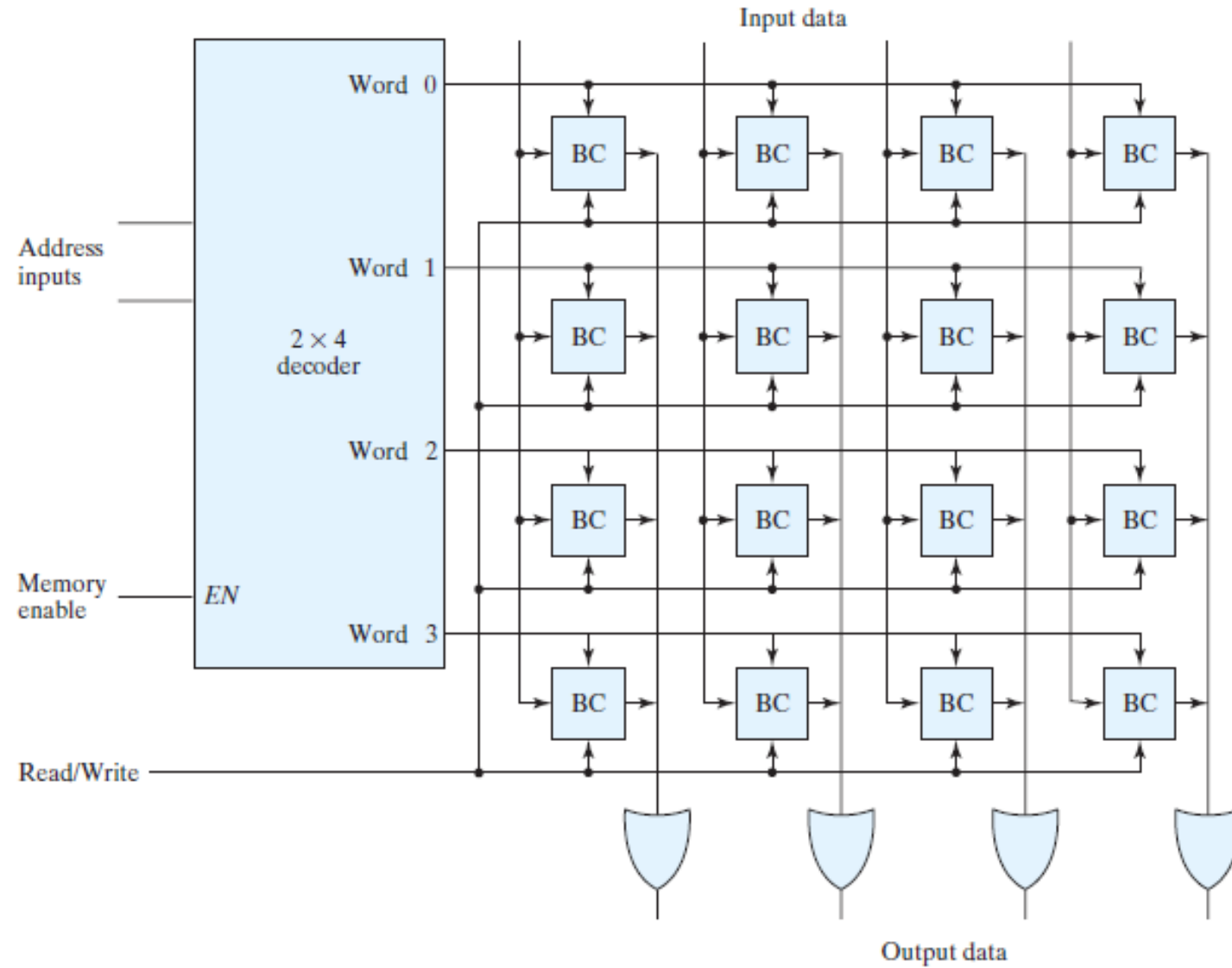

FPGAs

- Field Programmable Gate Arrays
- Tackle in this order:
 - Gate Arrays
 - Field Programmable


Sometimes
- Older technology / terminology

Look Up Table (LUT)

- Assume: 4 inputs, 1 output (all 1 bit)
- RAM-based array

Look Up Table (LUT)

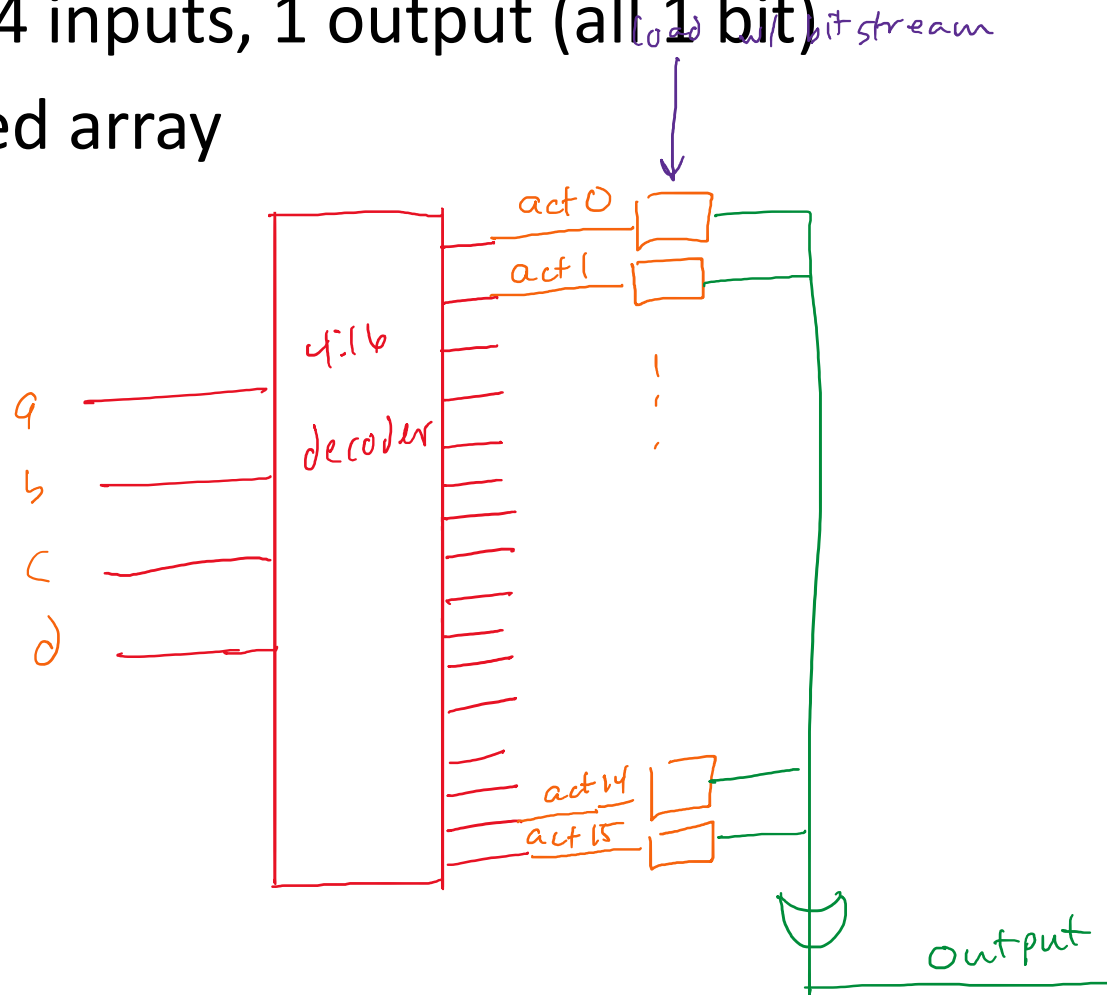- Assume: 4 inputs, 1 output (all 1 bit)
- RAM-based array



Configurable Logic Block (CLB)

 


Fig.4 Example of Configurable Logic Cell.

Configurable Logic Block (CLB)

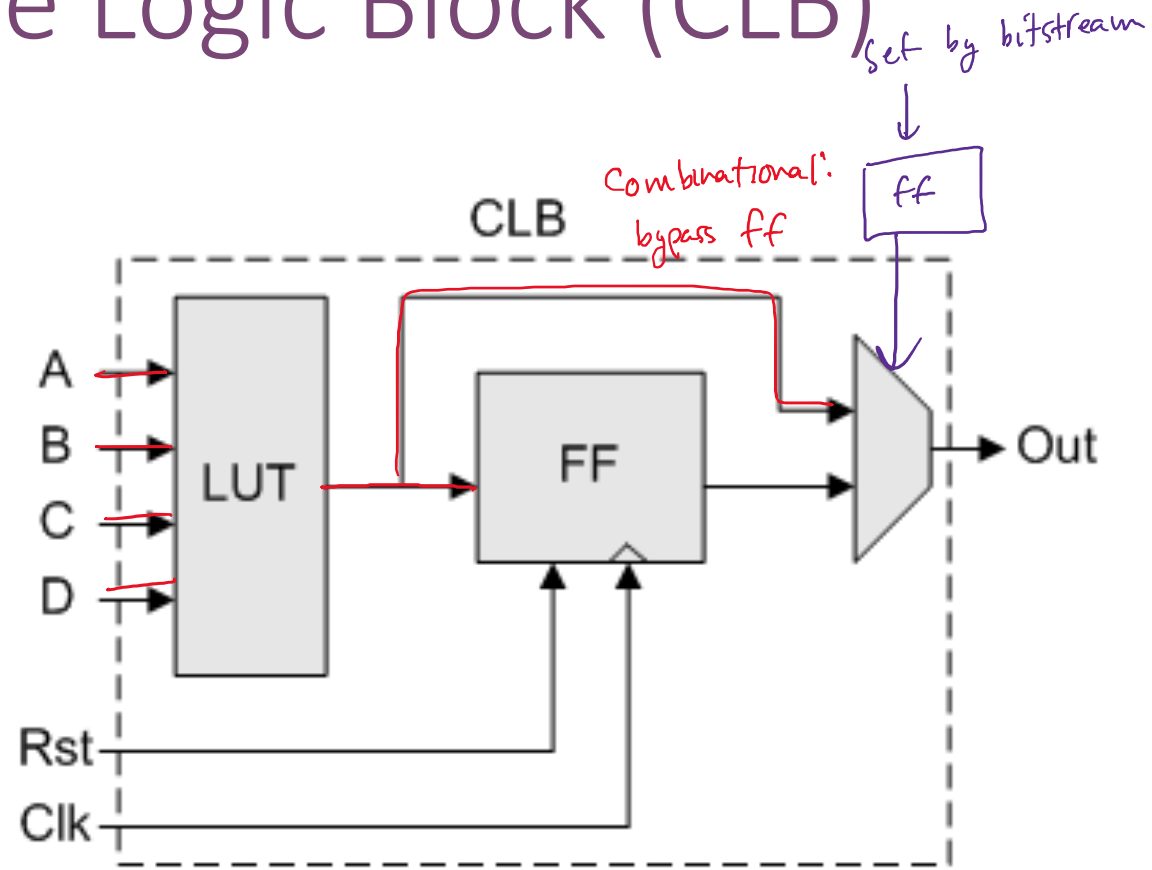


Fig.4 Example of Configurable Logic Cell.

Connecting CLBs


```
wire [7:0] value;
```

```
wire maxVal = ( value == 8'hff );
```

Connecting CLBs

wire [7:0] value;

wire maxValve = (value == 8'hff);

 


Connecting CLBs


```
wire [7:0] value;
```

```
wire maxVal = ( value == 8'hff );
```


Connecting CLB

 

CLB Interconnect

 

CLB Interconnect

 

FPGA w/BRAM

 


Figure 1: Basic Spartan-II Family FPGA Block Diagram


More on FPGAs

- There is a lot more we could say about using FPGAs
- Why synthesis takes so long:
 - Remapping state machines
 - Behavioral Verilog -> Structural Verilog
 - Mapping to LUTs / CLBs
 - Layout of CLBs / IOs
 - Interconnection
 - Generating a configuration bitstream

(one lots)


Busses

 - Boolean Logic is bi-state:
 - 1: logical true
 - 0: logical false
 - X: The simulation tools don't know if it's 1 or 0
- So you can't do things like this:




Busses

 - Boolean Logic is bi-state:
 - 1: logical true
 - 0: logical false
- X: The simulation tools don't know if it's 1 or 0
- So you can't do things like this:




Then how does this work?

 


Answer: A “Tri-State” Bus

- “Tri-State” signals:
 - 1: this is logical true
 - 0: this is logical false
 - X: The simulation tools don’t know if it’s 1 or 0
 - Z: this is “high impedance”
- Z: High Impedance
 - Stop driving a logical value
 - Pretend I’m not connected

Tri-State logic

 


Tri-State Bus

 

Problems with Tri-State Logic

- What if two signals “drive” at once?

 


Solution: Don't Do That!

Tri-State

Look Up Table (LUT)

 - Assume: 4 inputs, 1 output (all 1 bit)
- RAM-based array



Next Time

- We start designing a CPU!
- Specifically: Control / Datapath