

# Memory II

+

# Tri-State Busses

Andrew Lukefahr

# Topics


- ROMs/RAMs
- Memory + State Machines
- Tri-State Busses

# Review: ROM vs RAM


- ROM – Read-Only Memory
  - Input: address
  - Output: fixed value
- RAM – Random-Access Memory
  - Read/Write version of a ROM
 
# Review: RAM cell

The binary storage cell is the basic building block of a memory unit.




 The equivalent logic of a binary cell that stores one bit of information:


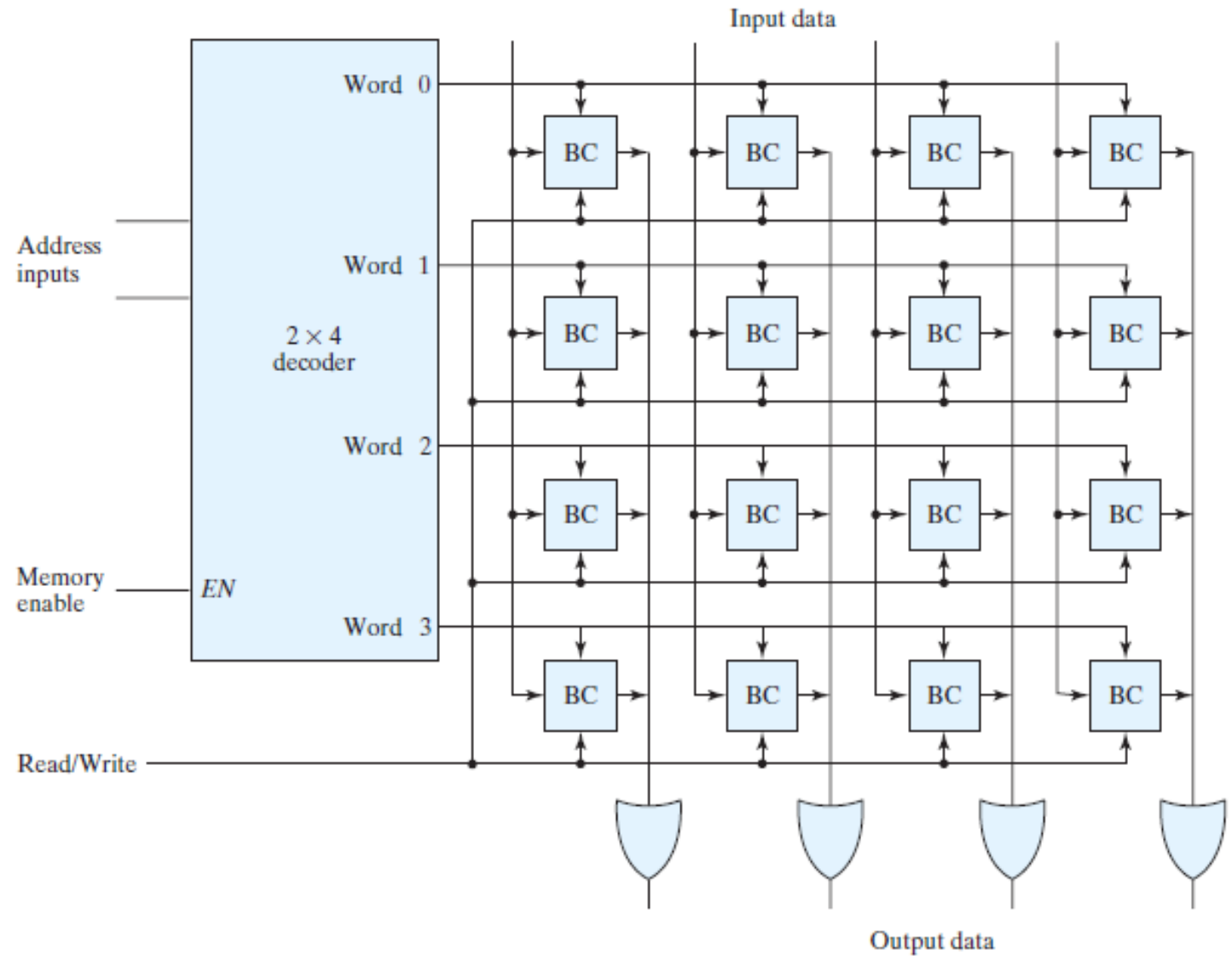
# Review: RAM

- How many address bits?
- How many data bits?



# Aside: SRAM vs DRAM

- SRAM:
  - Static RAM
  - What we've discussed so far
  - Uses full SR Latch to maintain value
- DRAM:
  - Dynamic RAM
  - Charges capacitor to store charge
  - Requires active "refresh" circuit

# Aside: SRAM vs DRAM

- SRAM:
  - Uses full SR Latch to maintain value
  - + Easier
  - Bigger cells
  - Higher power
- DRAM:
  - Charges capacitor to store charge
  - + Smaller cells, higher density
  - Requires sophisticated read and “refresh” circuits


# Aside: SRAM vs DRAM

- SRAM:
  - On Exam!
- DRAM:
  - Not on exam!



 
# Queues with RAMs

- Given: RAM array (shown)
- Make: 4-element 4-bit **Queue**
  - Recall: First-in-first-out
- Tip: Use a state machine!


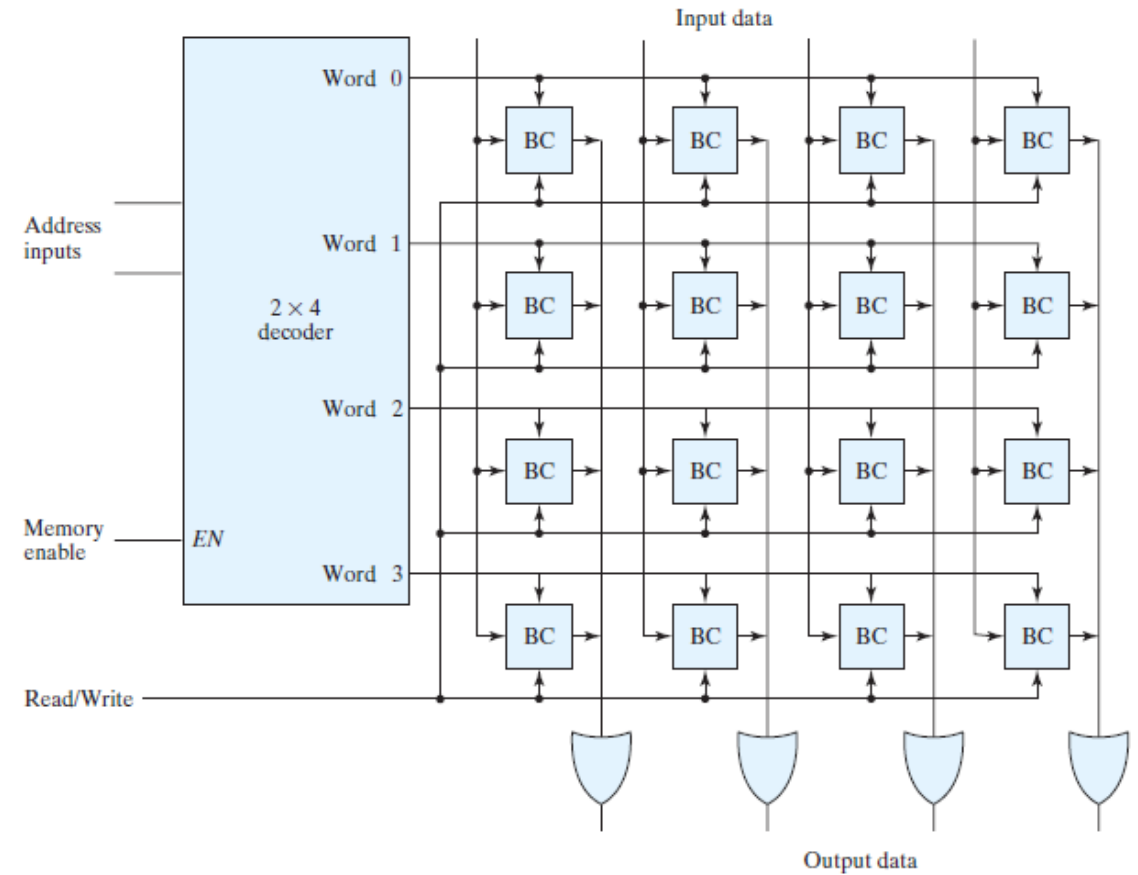
# Queues with RAMs

- Two queue “functions”
- Enqueue:
  - Adds element to queue
  - `enqueue( 4'b XXXX )`
- Dequeue:
  - Removes element from queue
  - `4'bXXXX = dequeue()`




# Enqueue with RAMs

enqueue( 4'b 0001)

enqueue( 4'b 0010)

enqueue( 4'b 0100)

enqueue( 4'b 1000)

 


# Deque with RAMs

4'b0001 = deque()

4'b0010 = deque()


4'b0100 = deque()

4'b1000 = deque()

 
 
# Enqueue/Deque with RAMs

enqueue( 4'b 0001)  
enqueue( 4'b 0010)  
enqueue( 4'b 0100)  
4'b0001 = deque()  
4'b0010 = deque()  
enqueue( 4'b 1000)  
enqueue( 4'b 0011)  
4'b0100 = deque()  
4'b1000 = deque()  
enqueue( 4'b 0110)  
4'b0011 = deque()



# Enque State Machine

- Inputs: enq\_req, [3:0] enq\_data
- To RAM: mem\_en, address, read\_writeN, [3:0] input

# Deque State Machine

- Inputs: `deq_req`
- Outputs: `[3:0] deq_data`
- To RAM: `mem_en`, `address`, `read_writeN`
- From RAM: `[3:0] output`

# Challenge: Enqueue/Deque State Machine

- Inputs: enq\_req, deq\_req, [3:0] enq\_data
- Outputs: [3:0] deq\_data
- To RAM: mem\_en, address, read\_writeN, [3:0] input
- From RAM: [3:0] output



# Challenge II: Enqueue/Deque State Machine

- Inputs: enq\_req, deq\_req, [3:0] enq\_data
- Outputs: [3:0] deq\_data, **enq\_err**, **deq\_err**
- To RAM: mem\_en, address, read\_writeN, [3:0] input
- From RAM: [3:0] output

# Challenge III: Enqueue/Deque State Machine

- Inputs: `enq_req`, `deq_req`, `[3:0] enq_data`
  - Outputs: `[3:0] deq_data`, **`enq_err`**, **`deq_err`**
  - To RAM: `mem_en`, `address`, `read_writeN`, `[3:0] input`
  - From RAM: `[3:0] output`
- 
- What if `enq_req == 1 AND deq_req == 1`?

Topic-Shift:


## Tri-State Busses

# Busses

- Boolean Logic is bi-state:
  - 1: logical true
  - 0: logical false
  - X: The simulation tools don't know if it's 1 or 0
- So you can't do things like this:

 
# Busses

- Boolean Logic is bi-state:
  - 1: logical true
  - 0: logical false
  - X: The simulation tools don't know if it's 1 or 0
- So you can't do things like this:


 
# Question: Then how does I2C work?

- I2C: **Inter - Integrated Circuit Communication**




- Clearly multiple “drivers” for 1 wire?

# Answer: A “Tri-State” Bus


- “Tri-State” signals:
  - 1: this is logical true
  - 0: this is logical false
  - X: The simulation tools don’t know if it’s 1 or 0
  - Z: this is “high impedance”
- Z: High Impedance
  - Stop driving a logical value
  - Pretend I’m not connected

# Tri-State logic

 




# Tri-State Bus

 

# Problems with Tri-State Logic

- What if two signals “drive” at once?

 

Solution: Don't Do That!

# 2-bit ROM of AND + OR

