

Finite State Machines II

Andrew Lukefahr

Always specify
defaults for
always_comb!

BLOCKING (=) FOR


always_comb

NON-BLOCKING (<=) for

always_ff


Review: States, Transitions, and Guards

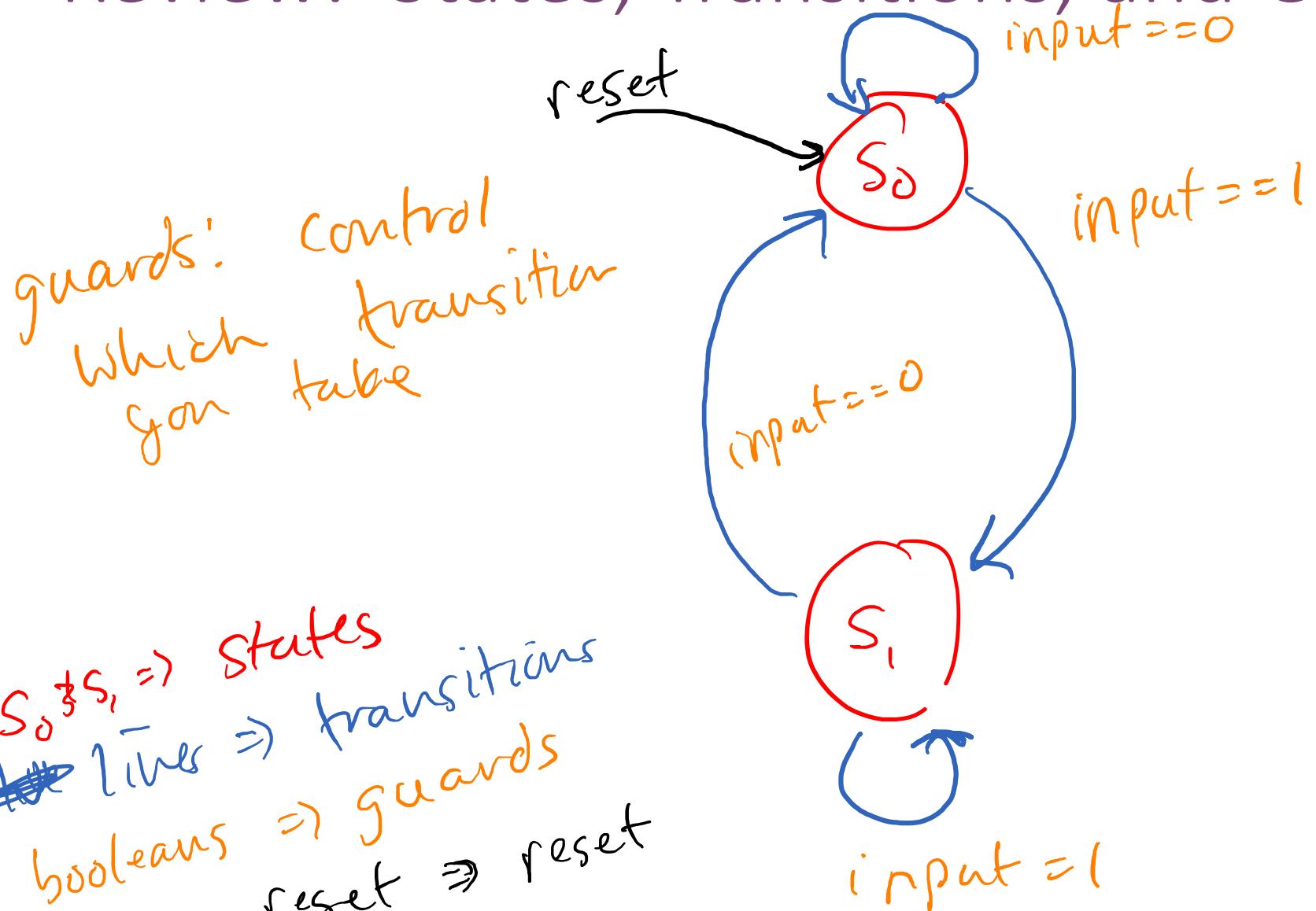~~S₀ + S₁ ⇒ states~~
~~lives ⇒ transitions~~
booleans ⇒ guards
reset ⇒ reset




S_0 & S_1 are states
two states in this machine
guards: control which transition you take
transitions
→ leaving one state & going to another
(happen @posede c(k))

What are the 'States'?


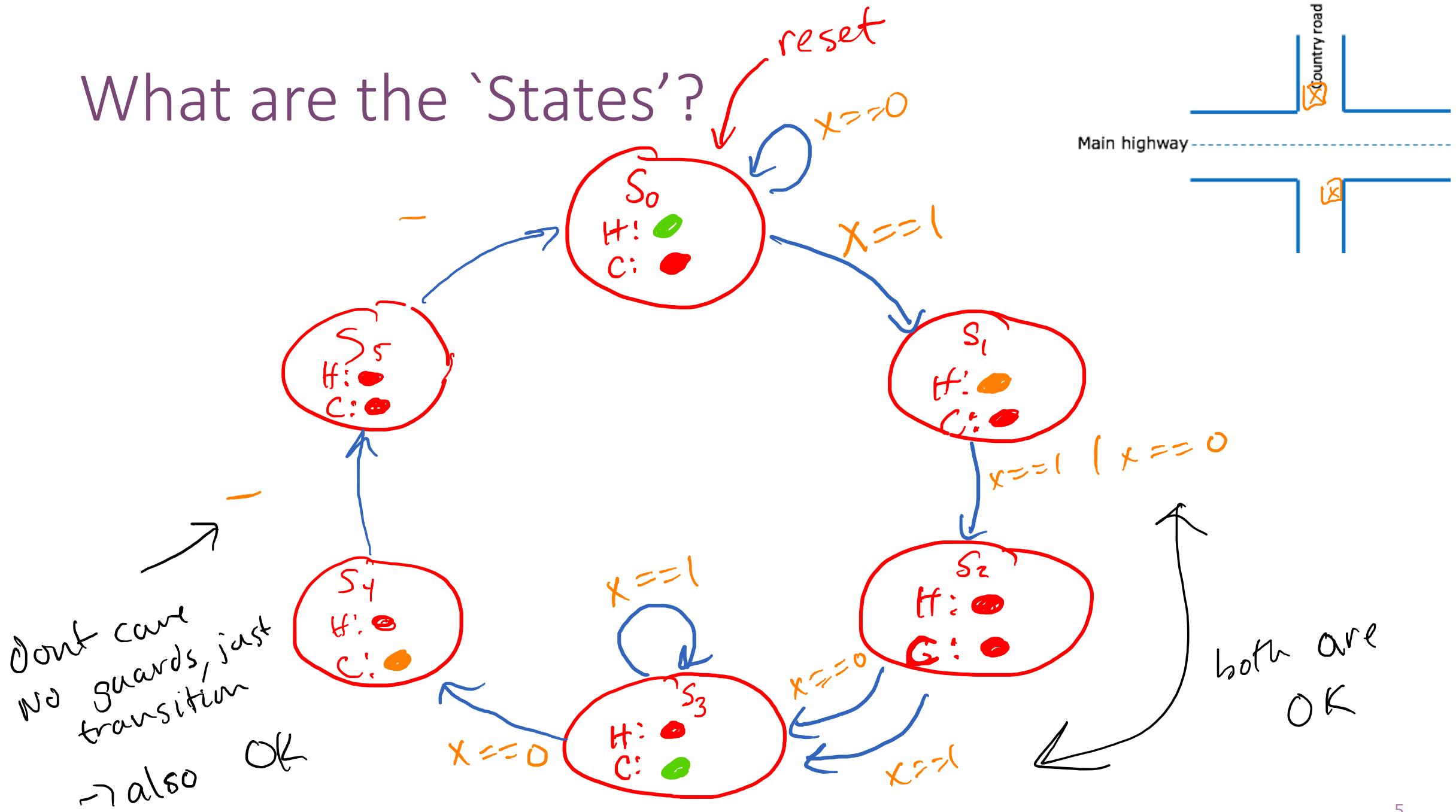


Moore vs. Mealy Type FSMs

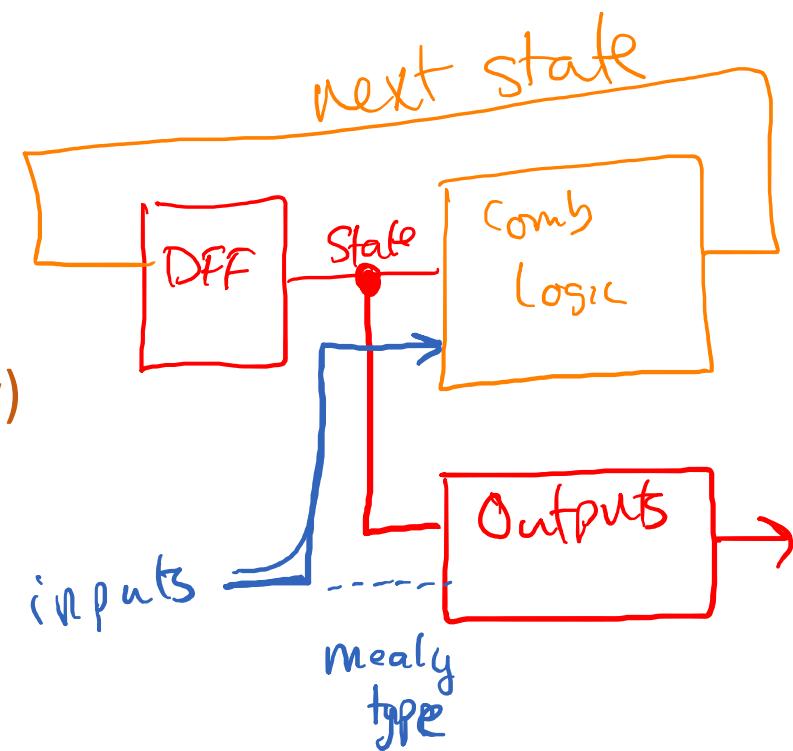
- Thus far we've done "Moore" Type
 - Moore Type: Outputs determined by the state (circle)
- Another technique: "Mealy" Type
 - Mealy Type: Output determined by the transition (arrow)
- Moore: Easier, but more states
- Mealy: Less states, more complicated transitions



Traffic Light: Moore vs. Mealy

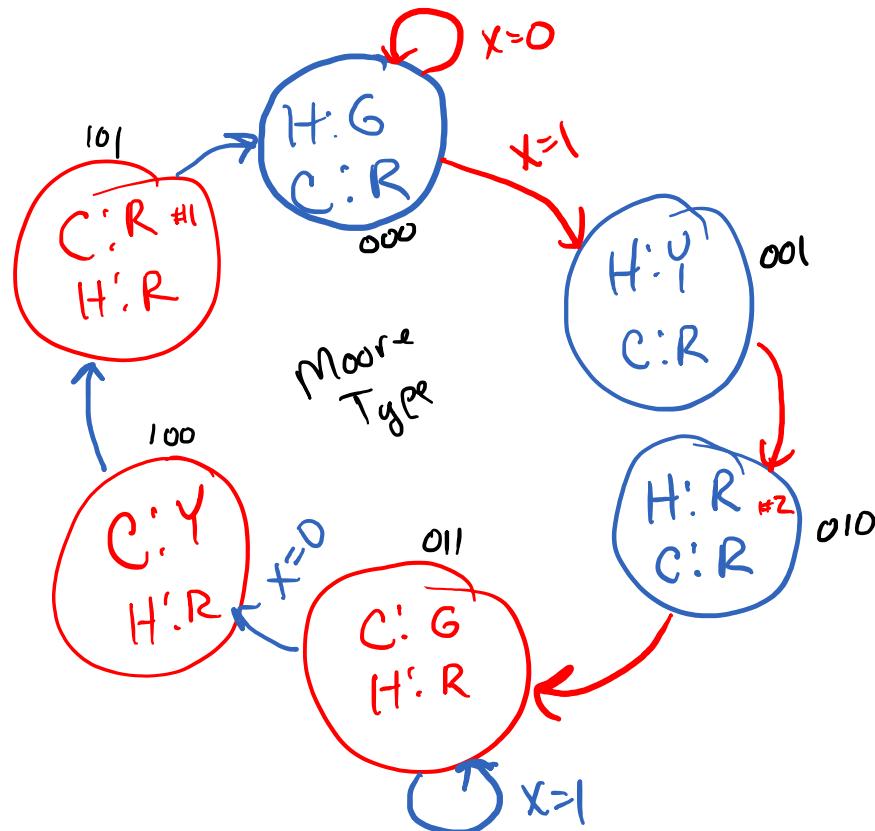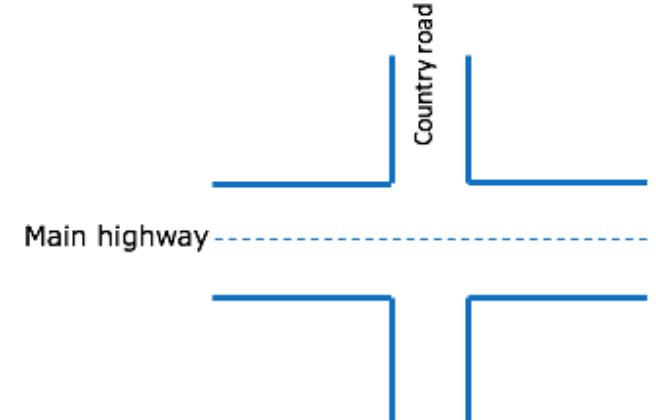

Mealy Type

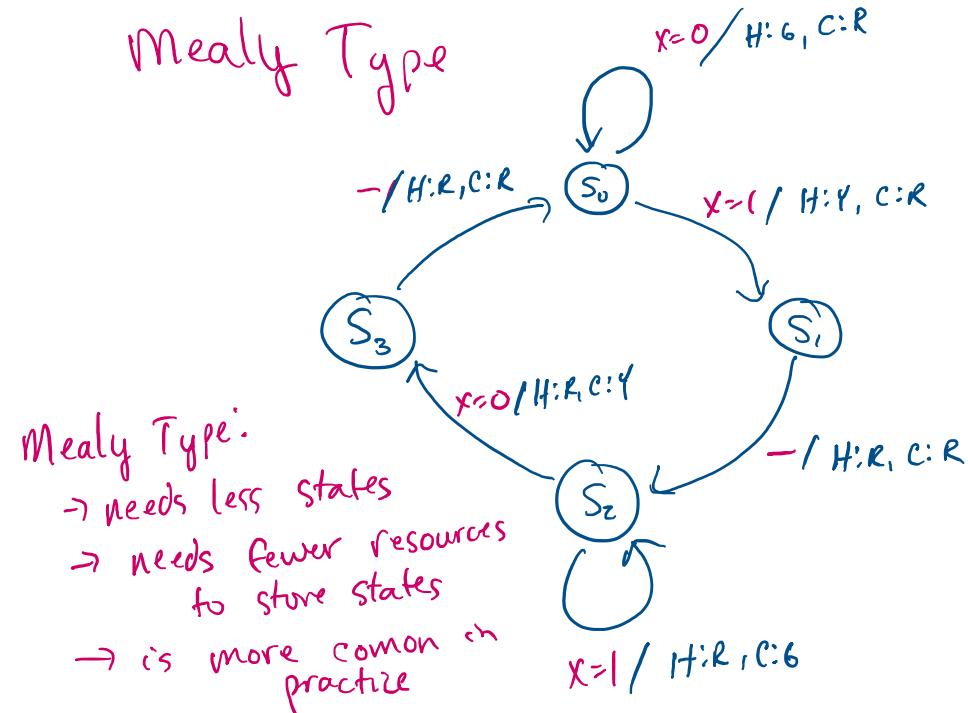


Mealy Type:

- needs less states
- needs fewer resources to store states
- is more common in practice


State Transition Encoding

<u>State</u>	<u>X</u>	<u>Next State</u>
0 0 (S_0)	0	00 (S_0)
0 0 (S_d)	1	01 (S_1)
0 1	0	10 (S_2)
0 1	1	10 (S_2)
1 0	0	11 (S_3)
1 0	1	10 (S_2)
1 1	0	00 (S_0)
1 1	1	00 (S_0)

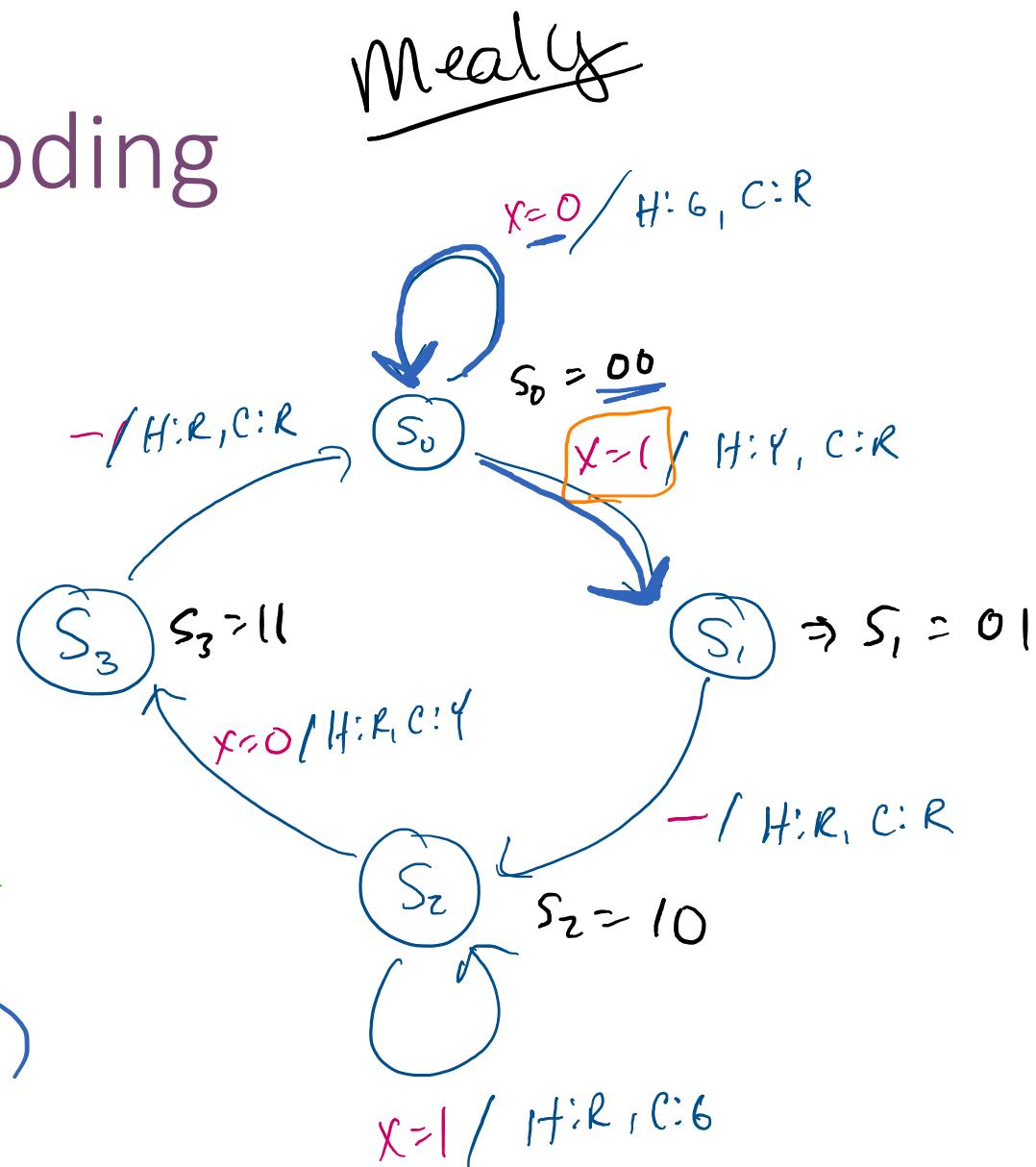

State Machine Encoding

	<u>State</u>	<u>X</u>	<u>Next State</u>
0	00	0	00
1	00	1	01
2	→ 01	0	10
3	→ 01	1	00
4	→ 10	0	11
5	→ 10	1	10
6	11	0	00
7	11	1	00

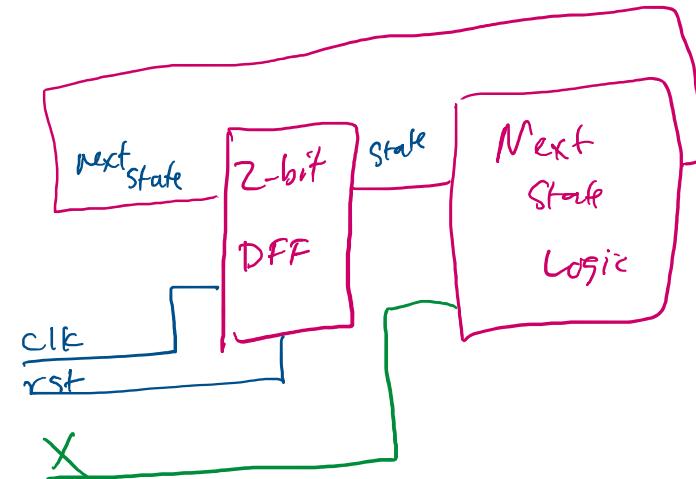

$$\text{Next State}[1] =$$

$$(\overline{\text{state}[1]} \oplus \text{state}[0] \oplus \overline{X}) \mid$$

$$(\overline{\text{state}[1]} \oplus \text{state}[0] \oplus X) \mid$$

$$(\text{state}[1] \oplus \overline{\text{state}[0]} \oplus \overline{X}) \mid$$

$$(\text{state}[1] \oplus \overline{\text{state}[0]} \oplus X)$$


$$\text{Next State}[0] =$$

$$(\overline{\text{state}[1]} \oplus \text{state}[0] \oplus X) \mid$$


$$(\text{state}[1] \oplus \overline{\text{state}[0]} \oplus \overline{X}) \mid$$

Output Logic (Highway)

	<u>State</u>	<u>X</u>	<u>H:R</u>	<u>H:Y</u>	<u>H:G</u>
0	00	0	0	0	1
1	00	1	0	1	0
2	01	0	1	0	0
3	01	1	1	0	0
4	10	0	1	0	0
5	10	1	1	0	0
6	11	0	1	0	0
7	11	1	1	0	0

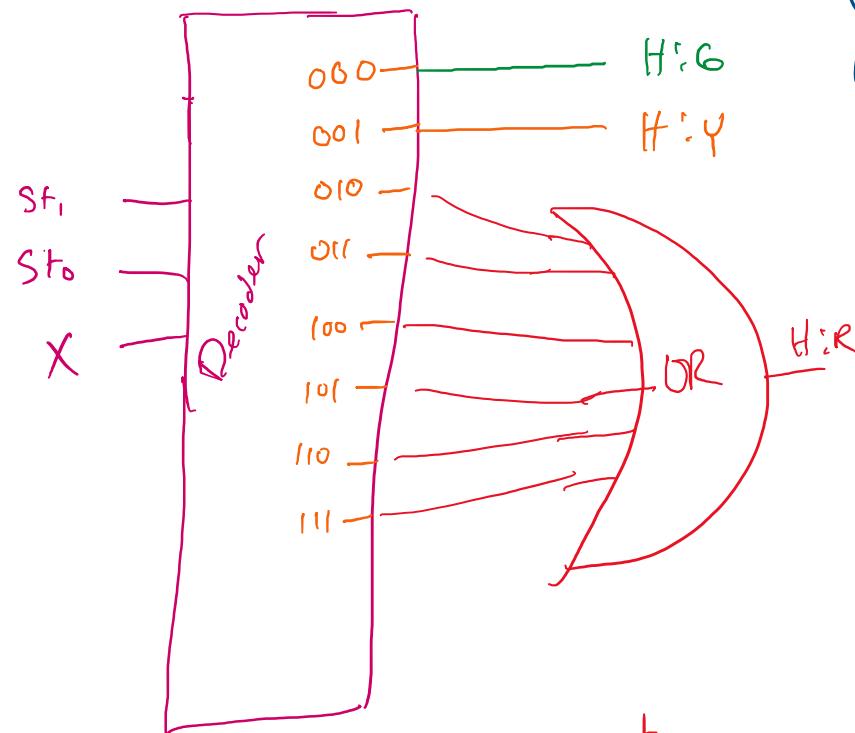


* Simpler methods exist

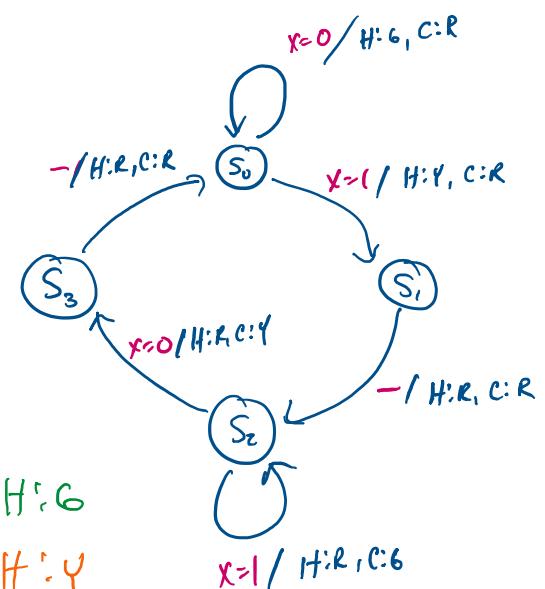



Output Logic (Country Road)

	<u>State</u>	<u>X</u>	C:R	C:Y	C:6
0	00	0	1	0	0
1	00	1	1	0	0
2	01	0	1	0	0
3	01	1	1	0	0
4	10	0	0	1	0
5	10	1	0	0	1
6	11	0	1	0	0
7	11	1	1	0	0

* Simpler methods exist

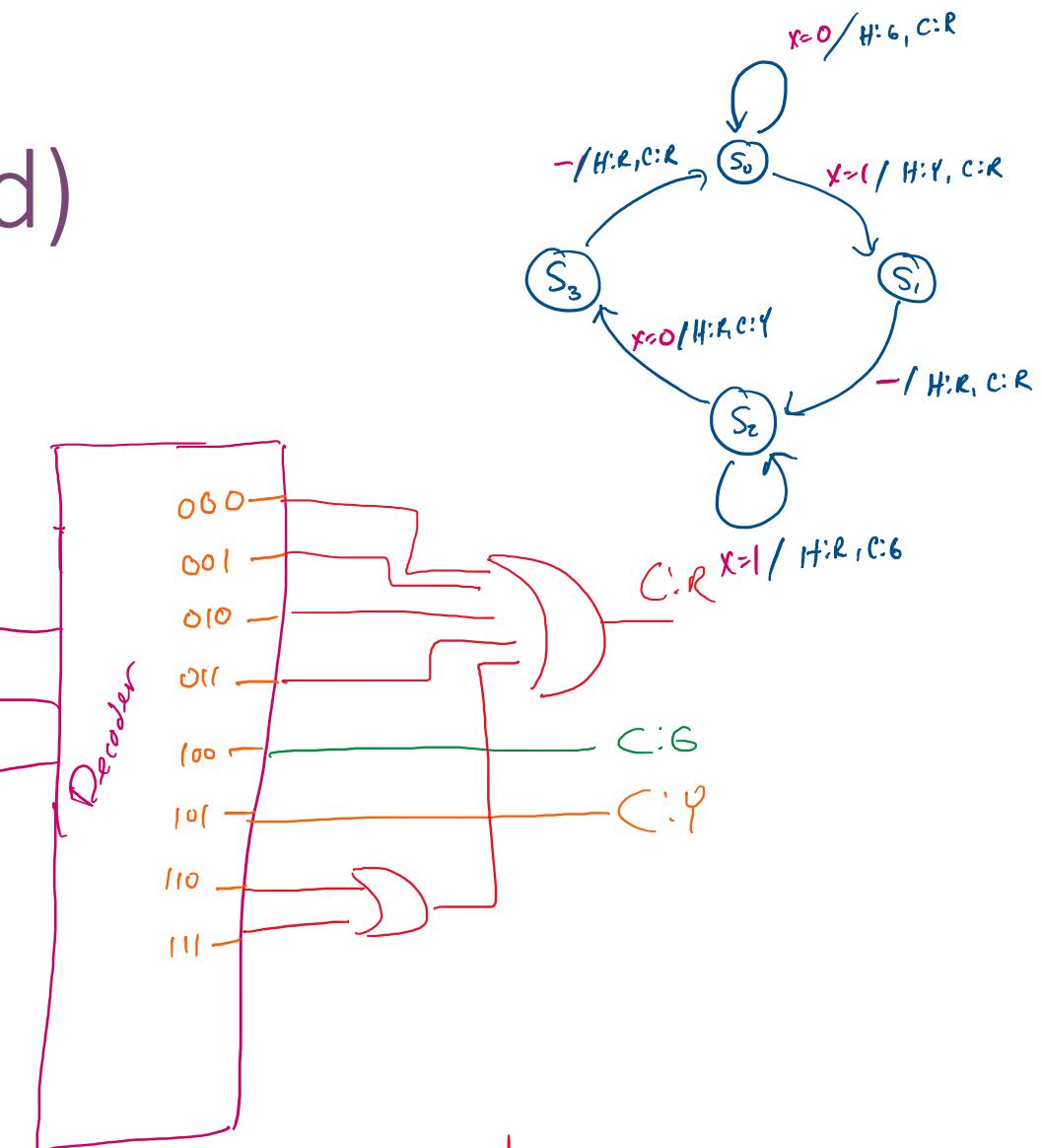


State Machines in Verilog

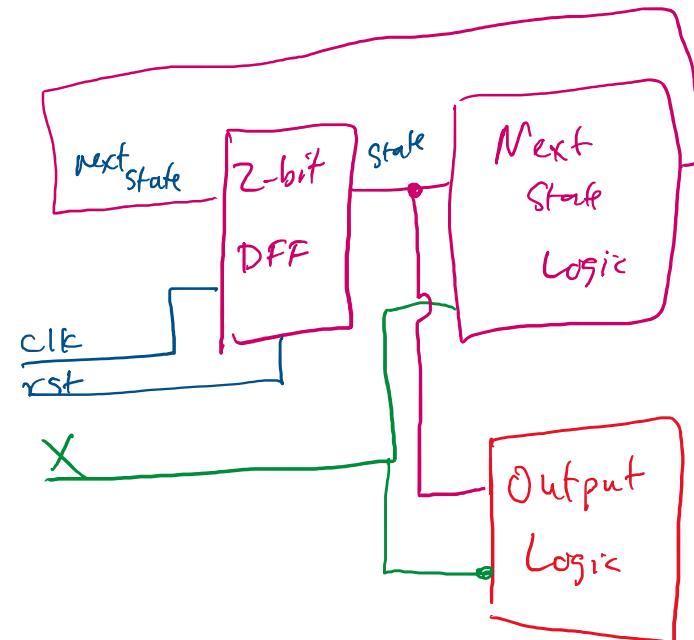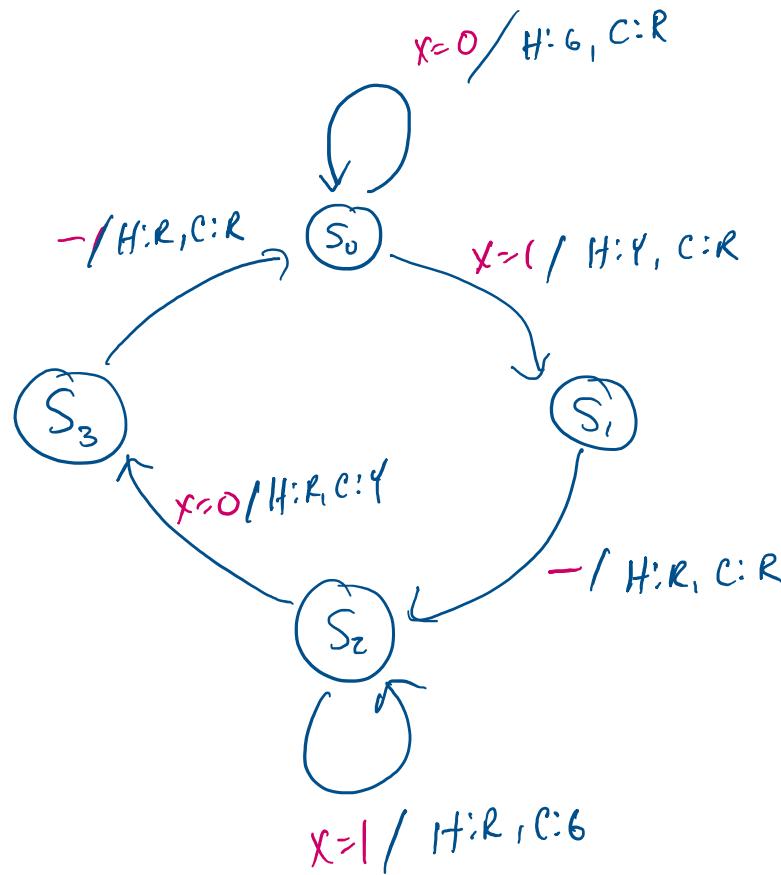


State Machine to Verilog

- Define states?

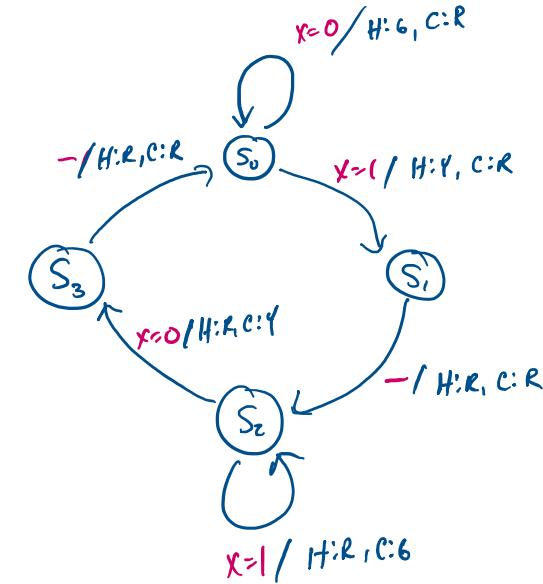

State Machine to Verilog


- Define states?

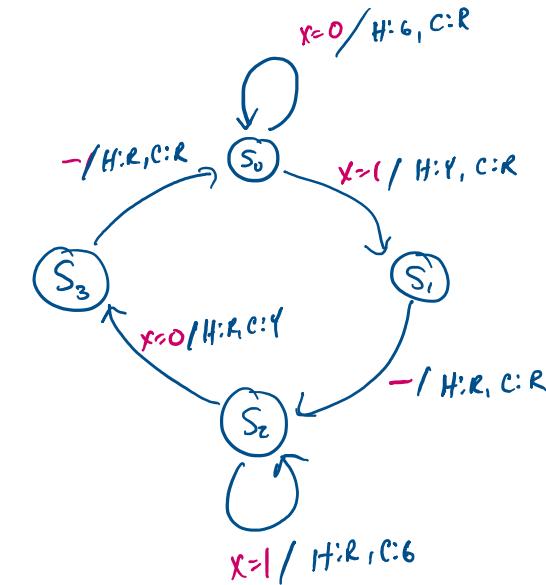

```
enum { ST_0, ST_1, ST_2, ST_3 } state, nextState;
```

State Machine to Verilog

- Build State Machine?

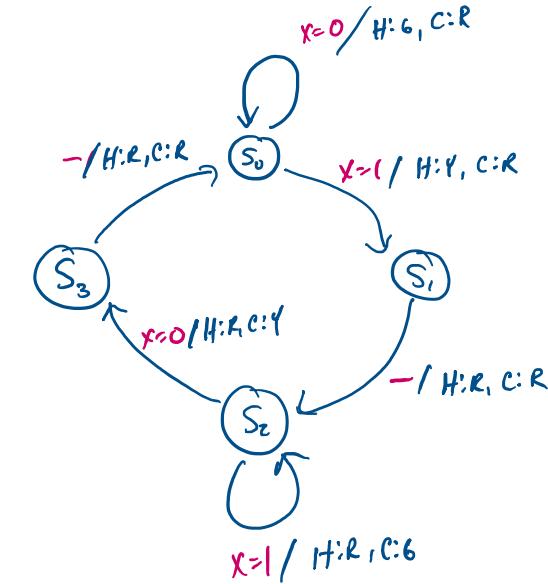


State Machine to Verilog

- Build State Machine?

```
always_ff @ (posedge clk) begin
    if (rst) state <= ST_0;
    else state <= nextState;
end
```


- What is nextState?

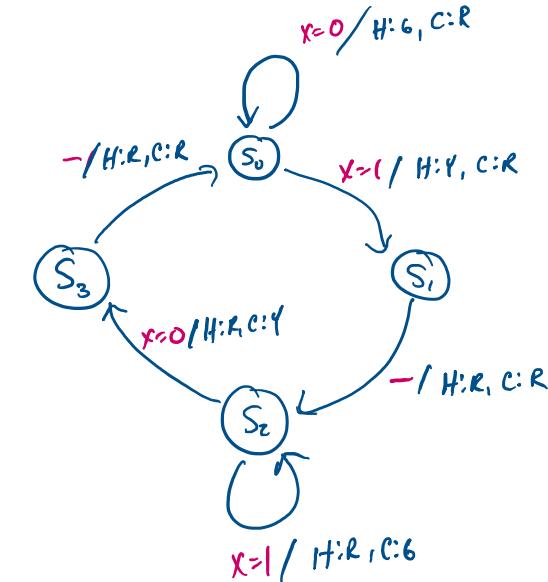

State Machine to Verilog

```
always_ff @ (posedge clk) begin
    if (rst) state <= ST_0;
    else state <= nextState;
end

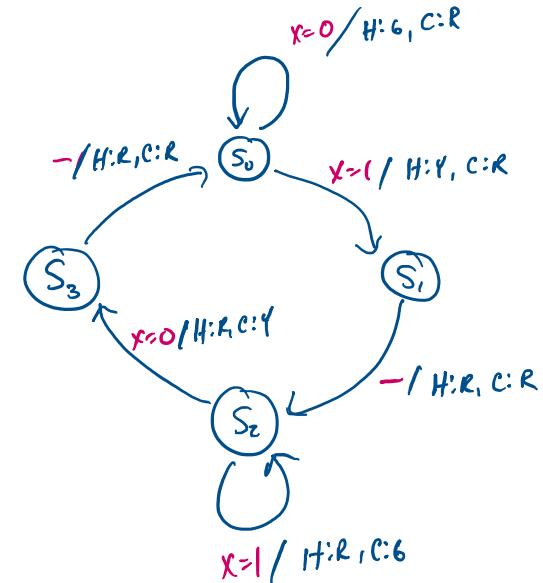
always_comb begin
    nextState = state; //default
    case(state)
        ST_0: nextState = ST_1; //goto state 1
        ST_1: nextState = ST_2;
        ST_2: nextState = ST_3;
        ST_3: nextState = ST_0; //loop
        default: nextState = ST_0; //just in case
    endcase
end
```



State Machine to Verilog

- What is this missing?

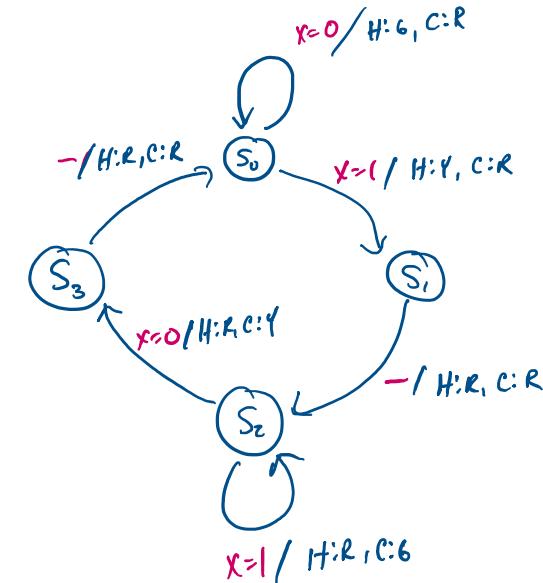
```
always_comb begin
    nextState = state; //default
    case(state)
        ST_0:
            nextState = ST_1;
        ST_1:
            nextState = ST_2;
        ST_2:
            nextState = ST_3;
        // ST_3 and default cases
    endcase
end
```



State Machine to Verilog

- What is this missing? **Guards**

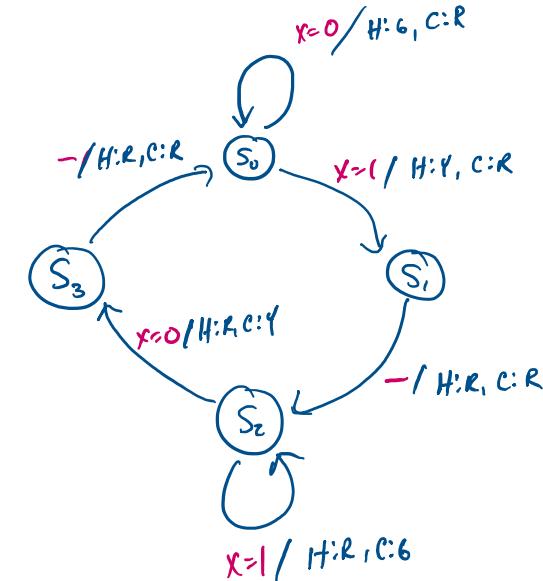
```
always_comb begin
    nextState = state; //default
    case(state)
        ST_0:
            if (x) nextState = ST_1;
        ST_1:
            nextState = ST_2;
        ST_2:
            if (~x) nextState = ST_3;
        // ST_3 and default cases
    endcase
end
```



State Machine to Verilog


- What else is this missing?
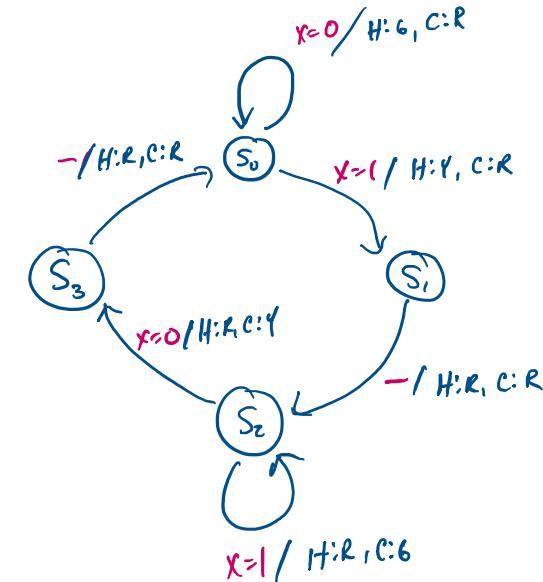
```
always_comb begin
    nextState = state; //default
    case(state)
        ST_0:
            if (X) nextState = ST_1;
            // ST_1-3 and default cases
    endcase
end
```



Outputs

```
always_comb begin
    nextState = state; //default
    Hryg = {0,0,1}; Cryg={1,0,0};
    case(state)
        ST_0: begin
            if (X) begin
                nextState = ST_1;
                Hryg = {0,1,0};
                Cryg = {1,0,0}; //optional
            end else begin
                nextState = ST_0; //optional
                Hryg = {0,0,1}; //optional
                Cryg = {1,0,0}; //optional
            end
        end
        // ST_1-3 and default cases
    endcase
end
```

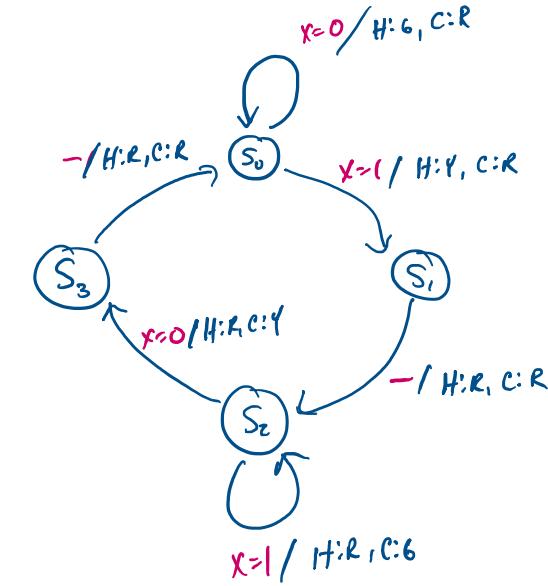

```

module traffic(
    input clk,
    input rst,
    input x,
    output logic [2:0] Hryg, //red-yellow-green
    output logic [2:0] Cryg //red-yellow-green
);

enum { ST_0, ST_1, ST_2, ST_3 } state, nextState;

always_ff @(posedge clk) begin
    if (rst) state <= ST_0;
    else      state <= nextState;
end

always_comb begin
    nextState = state; //default
    Hryg = 3'b001; Cryg = 3'b100;

    case (state)
        ST_0: begin
            if (x) begin
                nextState = ST_1;
                Hryg = 3'b010;
                Cryg = 3'b100; //opt
            end else begin //opt
                nextState = ST_0; //opt
                Hryg = 3'b001; //opt
                Cryg = 3'b100; //opt
            end
        end
    end

```

```

        ST_1: begin
            nextState = ST_2;
            Hryg = 3'b100;
            Cryg = 3'b100; //opt
        end


        ST_2: begin
            if (x) begin
                nextState = ST_2;
                Hryg = 3'b100;
                Cryg = 3'b001;
            end else begin
                nextState = ST_3;
                Hryg = 3'b100;
                Cryg = 3'b010;
            end
        end

        ST_3: begin
            nextState = ST_0;
            Hryg = 3'b100;
            Cryg = 3'b100; //opt
        end
    endcase
end

endmodule

```

Testbenches for State Machines

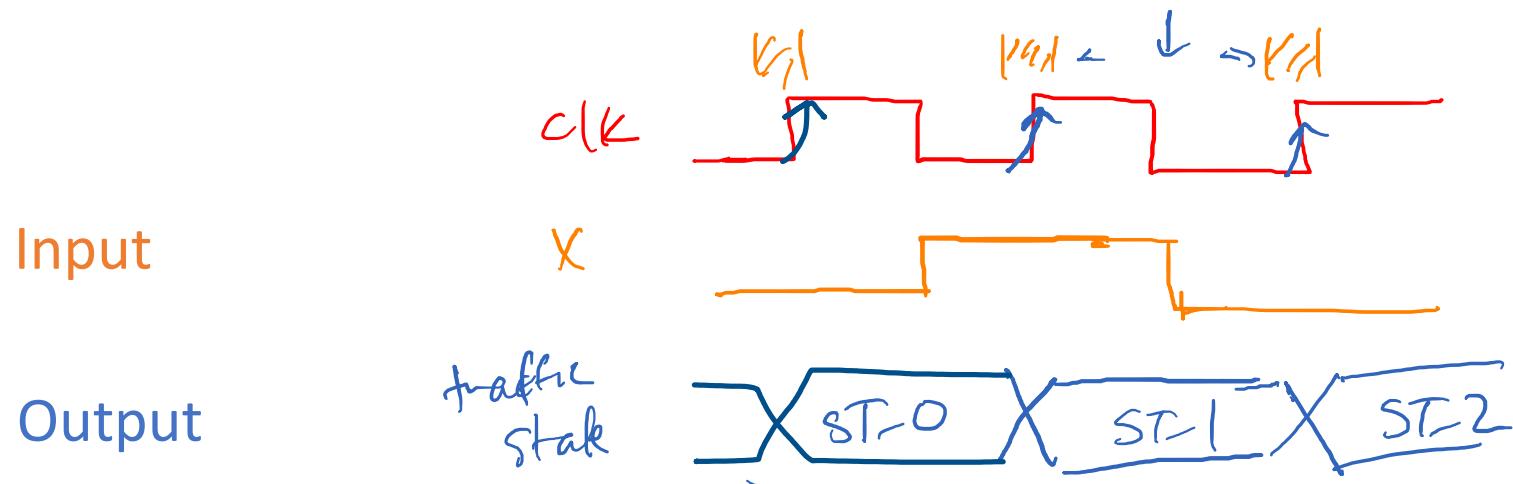

- Outputs change @posedge clk
- Change Inputs @negedge clk

```

`timescale 1ns / 1ps

module traffic_tb();

logic clk;
logic rst;
logic x;
wire [2:0] Hryg;
wire [2:0] Cryg;

traffic t0( .clk, .rst, .x, .Hryg, .Cryg);

always #10 clk = ~clk; //auto-update clock

initial begin
    clk = 0; rst = 1; x=0;
    @(negedge clk); //advance 1 cycle
    @(negedge clk);
    rst = 0;

```

```

@(negedge clk);
@(negedge clk);

x = 1;
@(negedge clk);
@(negedge clk);
@(negedge clk);

x = 0;
@(negedge clk);
@(negedge clk);
@(negedge clk);

$finish;
end
endmodule

```

```

`timescale 1ns / 1ps

module traffic_tb();

logic clk; ↗
logic rst;
logic x;
wire [2:0] Hryg; ↗
wire [2:0] Cryg;

traffic t0( .clk, .rst, .x, .Hryg, .Cryg);
outputs
always #10 clk = ~clk;

initial begin
    ↗ clk = 0; rst = 1; x=0; ↗
    @ (negedge clk); ↗ 2 cycles
    @ (negedge clk); ↗
    rst = 0; ↗ reset off

```

testbench: negedge
FPGA code: posedge

```


@ (negedge clk);
@ (negedge clk);

x = 1; ↗
@ (negedge clk);
@ (negedge clk);
@ (negedge clk);



x = 0; ↗
@ (negedge clk);
@ (negedge clk);
@ (negedge clk);

$finish;
end
endmodule


```

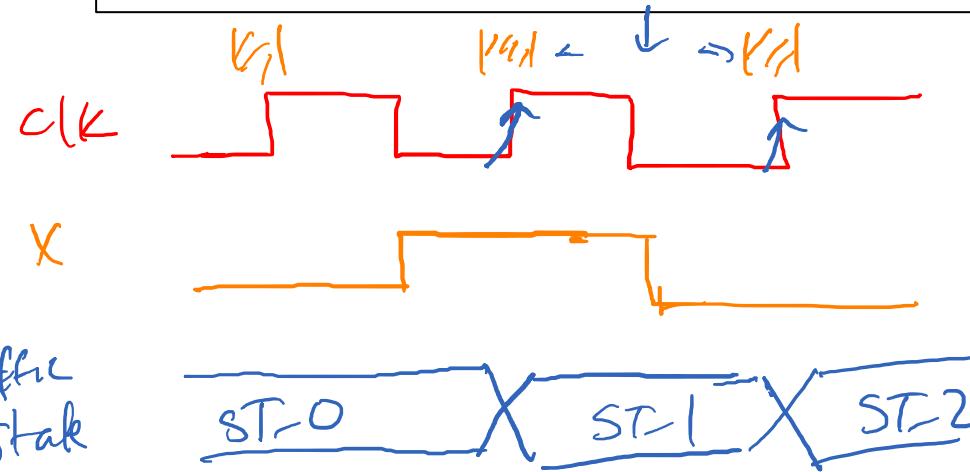

State Machine in Logic

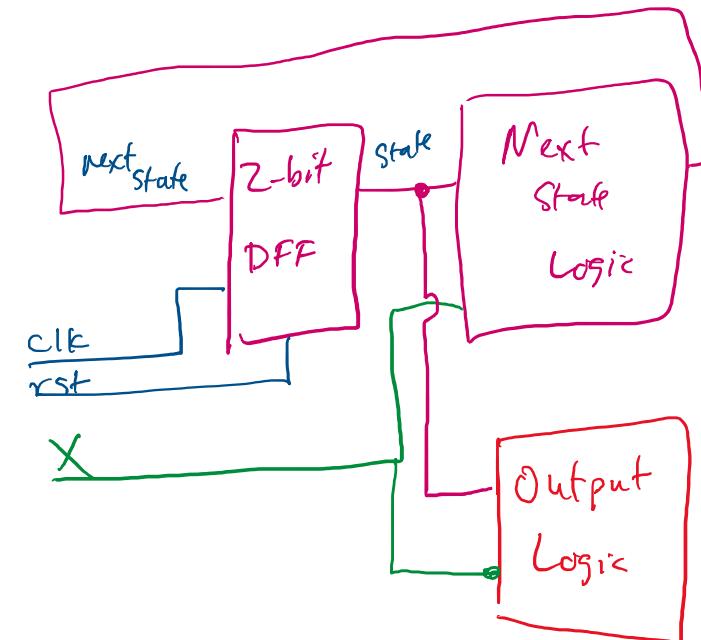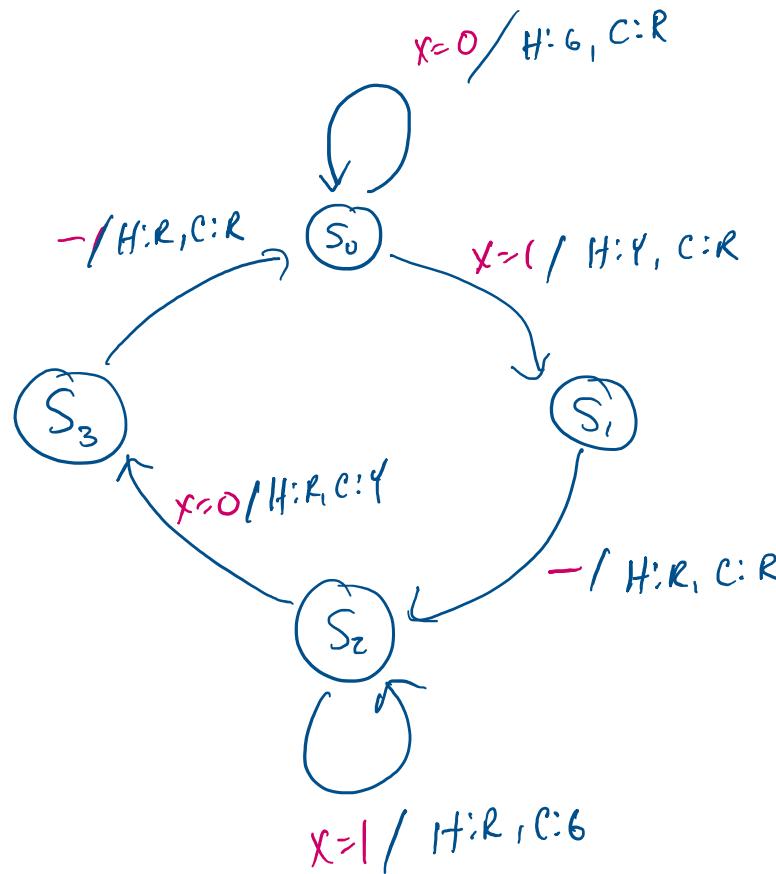

Circuit Structure for FSMs

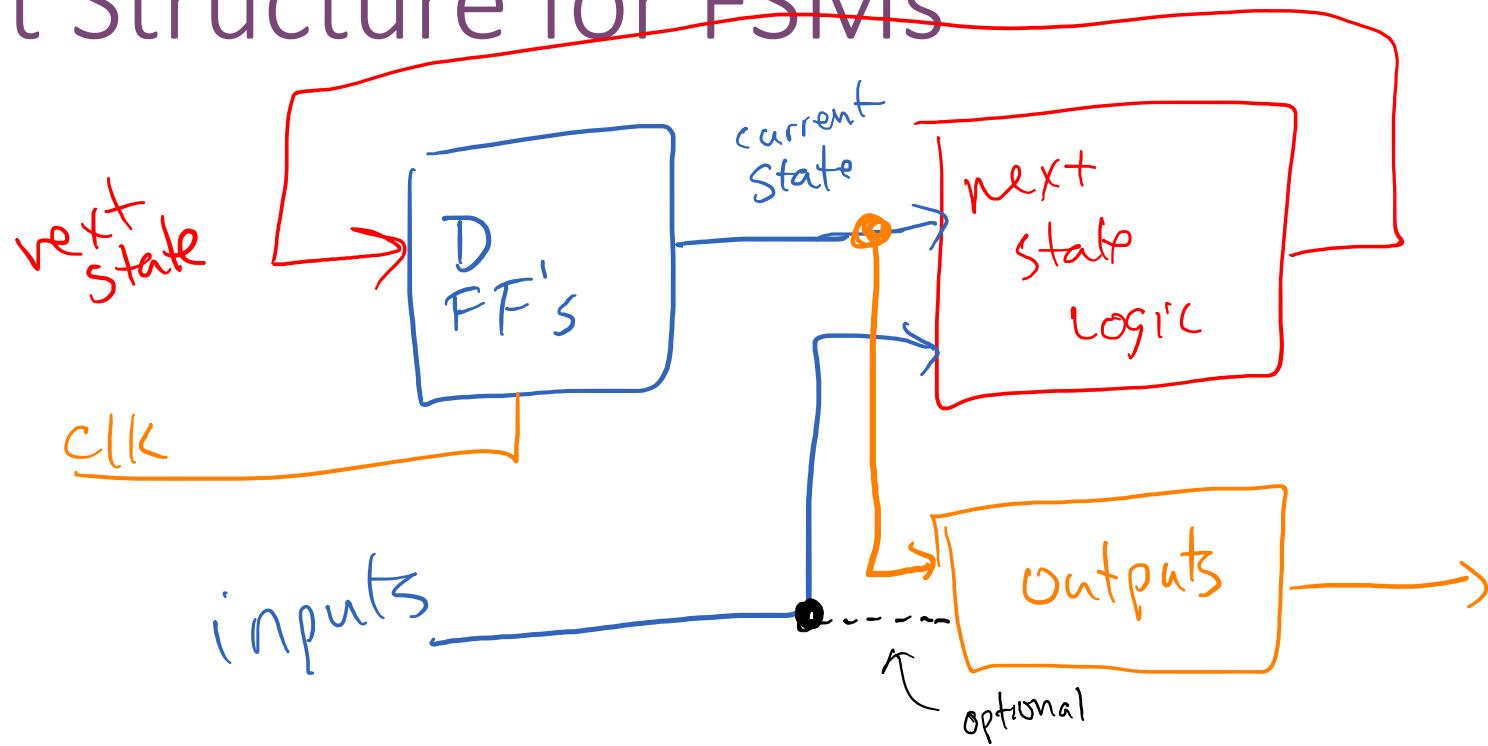

Moore Machine: outputs are a function of current state

Mealy Machine: outputs are a function of current state + inputs

Your Turn

- Build a digital safe / keypad lock
- The user must enter the digits 5 – 4 – 3 in that order to unlock the door. Any other inputs result in a locked door.
- Once unlocked, the door remains unlocked until E key pressed. *Ignore all other keys while unlocked.*



should unlock : 5 - 5 - 4 - 3, 5 - 4 - 5 - 4 - 3

- Draw the state machine!

Lock State Machine


- Recall: 5 - 4 - 3
- E: relock



Lock State Machine




- Recall: 5 - 4 - 3
 - E: relock

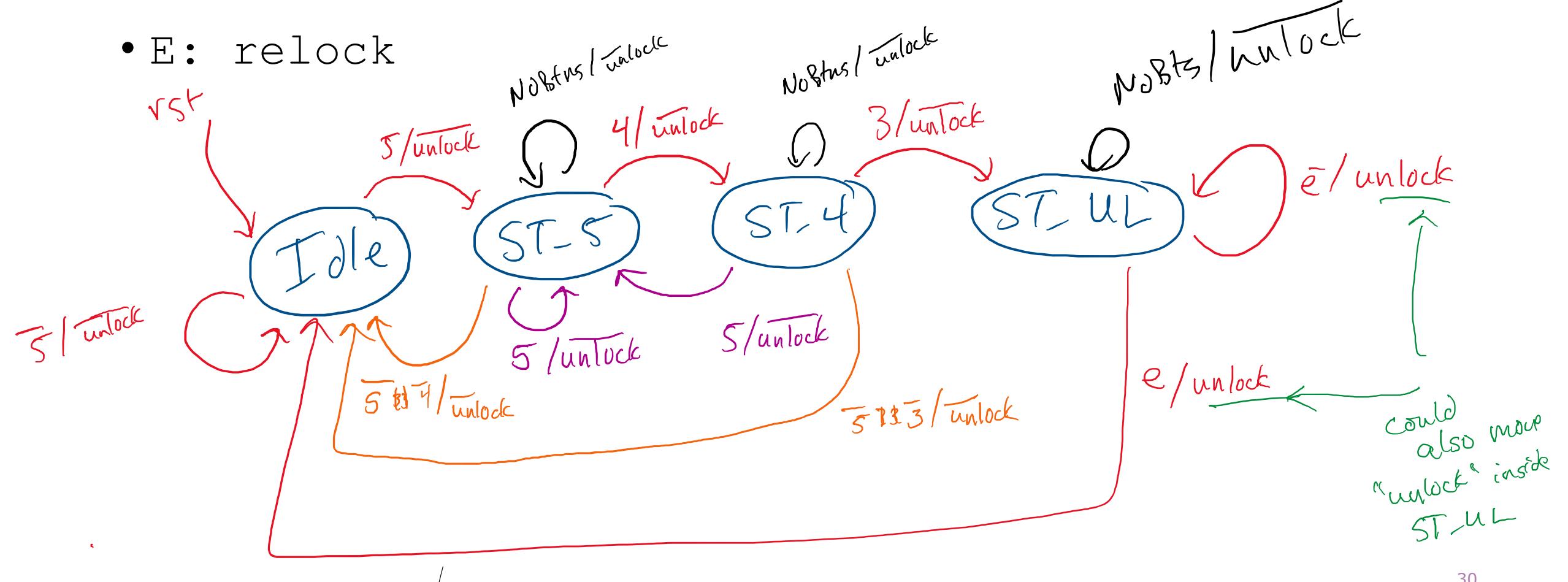


State Machine in Verilog
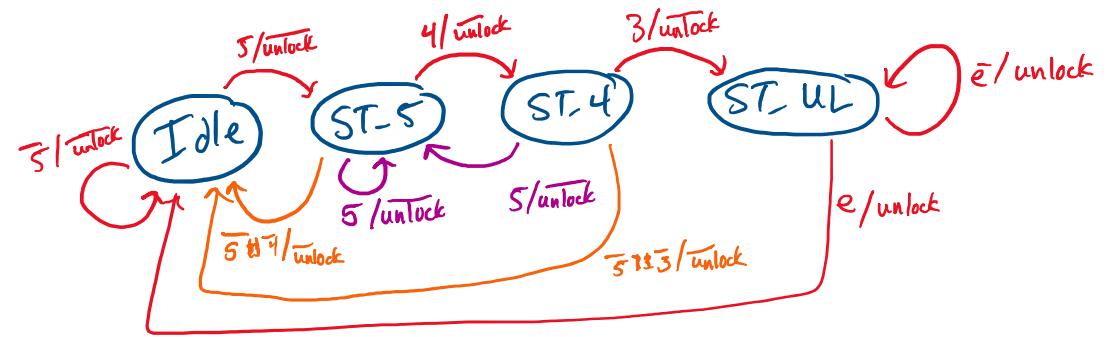
```
module Lock(  
    input clk, rst,  
    input [9:0] num,  
    input e, //relock  
    output unlock  
) ;
```



State Machine in Verilog

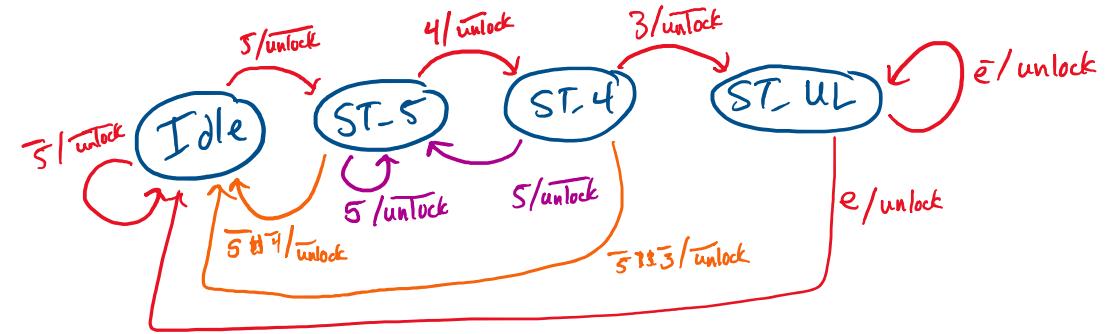

```
module Lock(
    input clk, rst,
    input [9:0] num,
    input e, //relock
    output unlock
);
```


```
enum {ST_IDLE, ST_5, ST_4, ST_UL } state, next_state;

//seq logic
always_ff @(posedge clk) begin
    if (rst) state <= ST_IDLE;
    else      state <= next_state;
end
```

State Machine in Verilog


```
//comb logic block  
always_comb begin
```

```
end
```

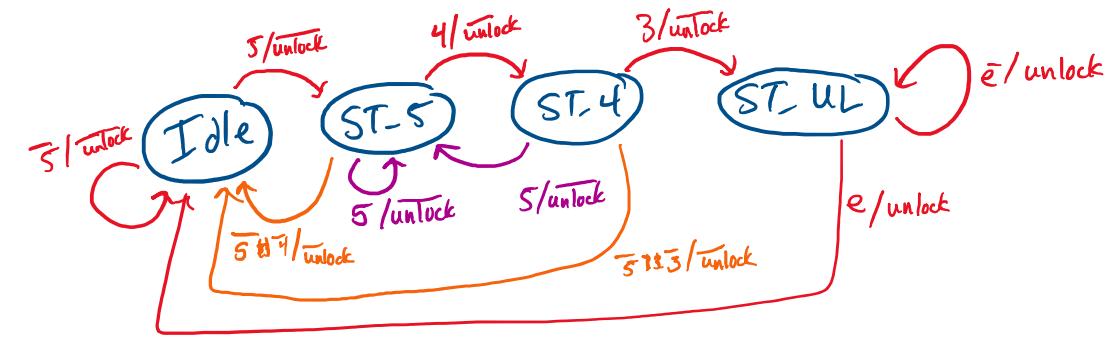


State Machine in Verilog
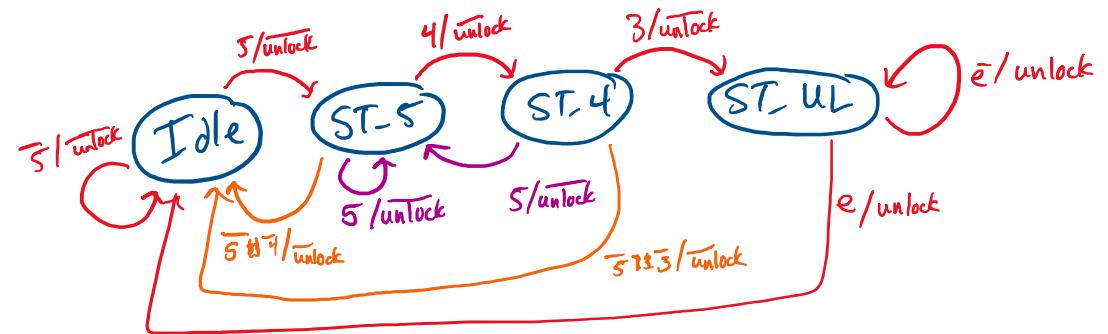
```
//comb logic block
always_comb begin
    next_state = state; //default
    unlock = 1'h0; //default
    case (state)
        ST_IDLE:
            if (num[5]) next_state = ST_5;
        ST_5:
            if (num[4]) next_state = ST_4;
        ST_4:
            if (num[3]) next_state = ST_UL;
        ST_UL: if (e)
            next_state = ST_IDLE;
    endcase
end
```



State Machine in Verilog

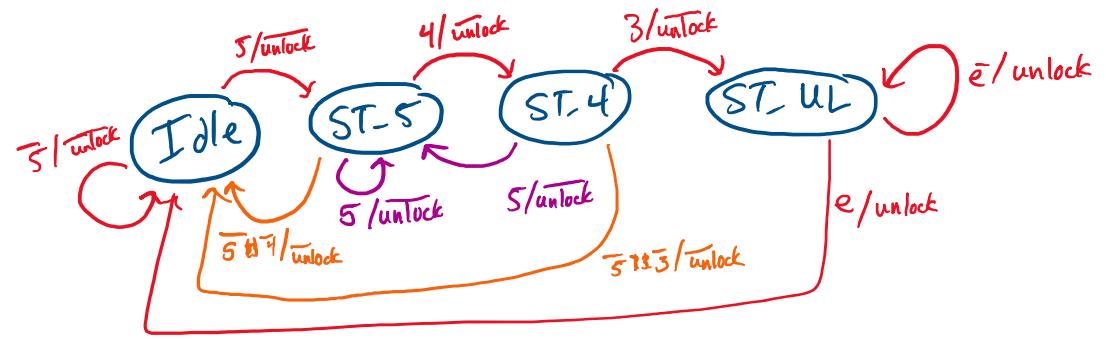
```
case (state)
    ST_IDLE:
        if (num[5])
            next_state = ST_5;
    ST_5: begin
        if (num[4])
            next_state = ST_4;
    end
    ST_4: begin
        if (num[3])
            next_state = ST_UL;
```



```
end
ST_UL: begin
    if (e)
        next_state = ST_IDLE;
end
endcase
```

State Machine in Verilog


```
case (state)
    ST_IDLE:
        if (num[5])
            next_state = ST_5;
    ST_5: begin
        if (num[4])
            next_state = ST_4;
        else if (num[5])
            next_state = ST_5;
        else if ((|num) | e) //other btns
            next_state = ST_IDLE;
    end
    ST_4: begin
        if (num[3])
            next_state = ST_UL;
```

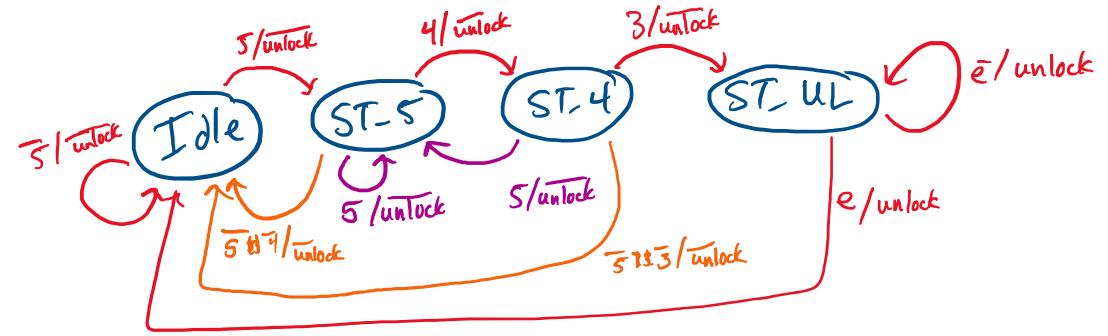

```
        else if (num[5])
            next_state = ST_5;
        else if ( (|num) | e) // other btns
            next_state = ST_IDLE;
    end
    ST_UL: begin
        unlock = 1'h1;
        if (e)
            next_state = ST_IDLE;
    end
endcase
```

State Machine in Verilog

```
case (state)
    ST_IDLE:
        if (num[5])
            next_state = ST_5;
    ST_5: begin
        if (num[4])
            next_state = ST_4;
        else if (num[5])
            next_state = ST_5;
        else if ( (|num) | e ) //other btns
            next_state = ST_IDLE;
    end
    ST_4: begin
        if (num[3]) unlock=1'h1;
            unlock = 1'h1;
            next_state = ST_UL;
    end
endcase
```

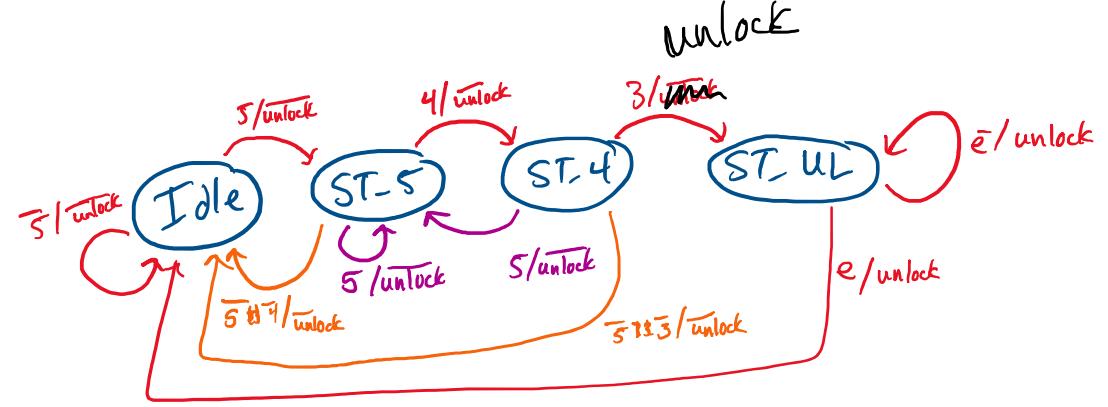


```
else if (num[5])
    next_state = ST_5;
else if ( (|num) | e ) //other btns
    next_state = ST_IDLE;
end
ST_UL: begin
    unlock = 1'h1;
    if (e)
        next_state = ST_IDLE;
    end
endcase
```

Timing

Flip-Flop Timing



- What's the delay for this Latch?
- Assume 5ps/ gate
- What about a Flip-Flop?

worst-case
delay
 $= 20\text{ps}$

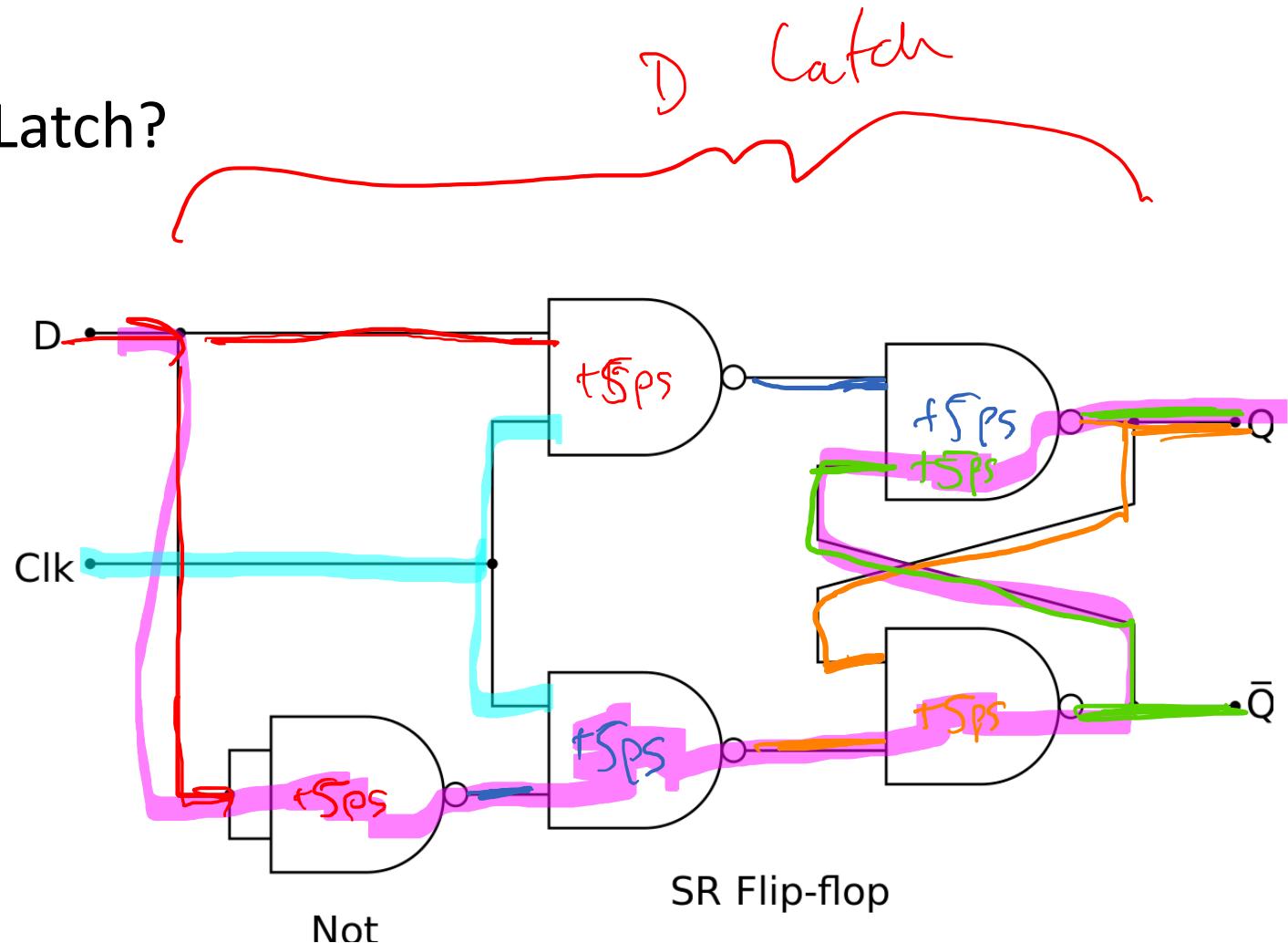



Flip-Flop Timing

- Assume 5ps/ Gate

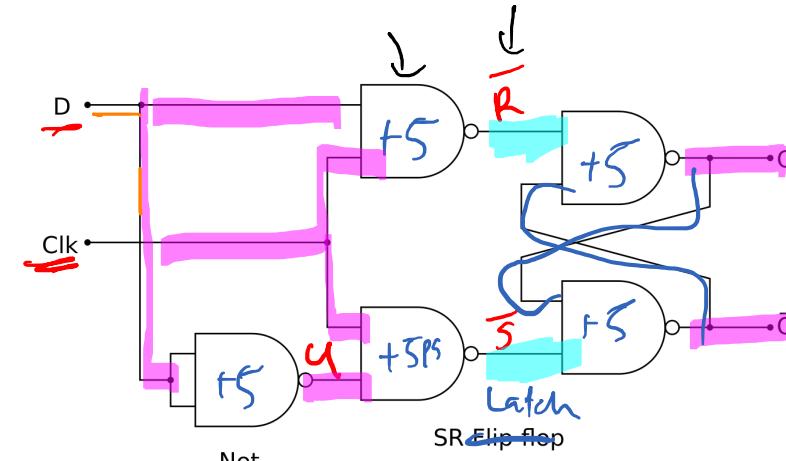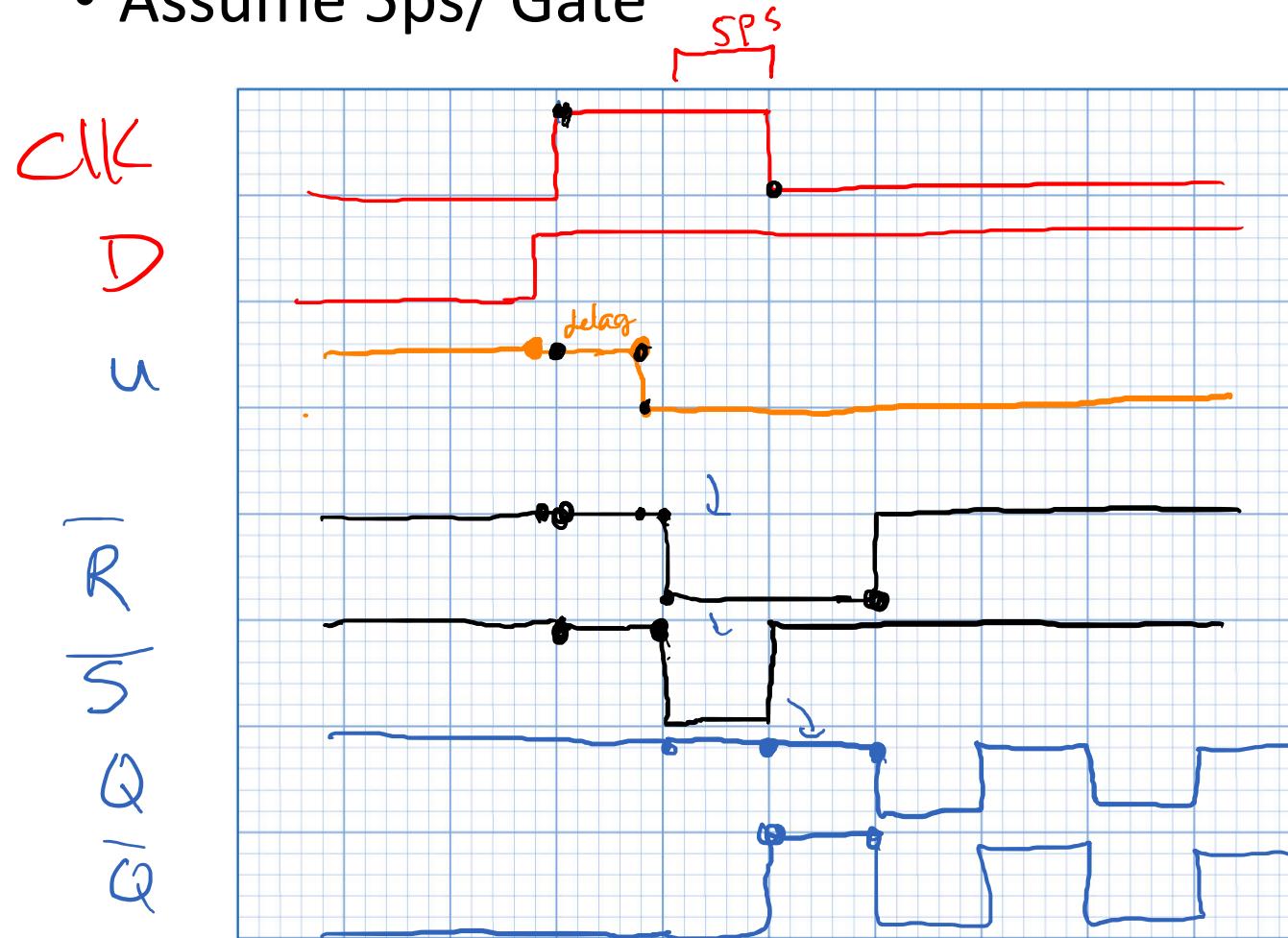


Flip-Flop Timing


- Assume 5ps/ Gate

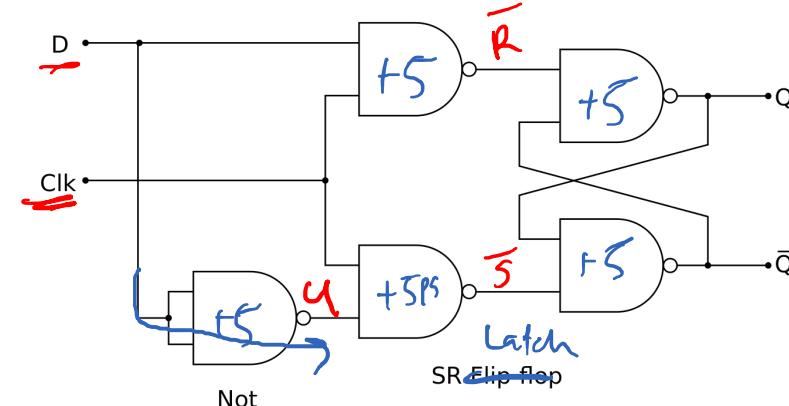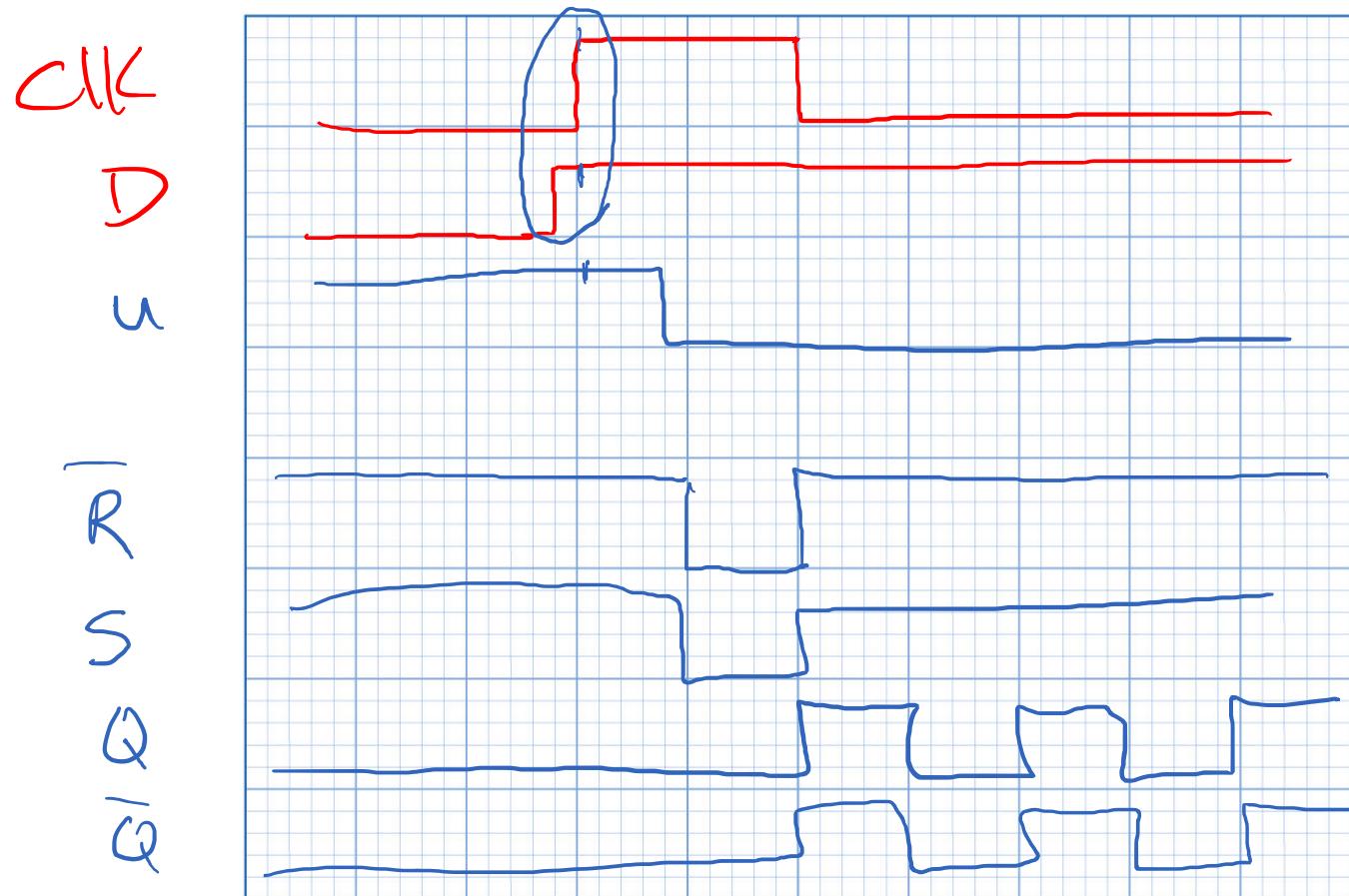

Glitch

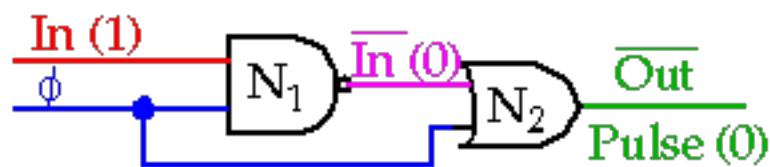

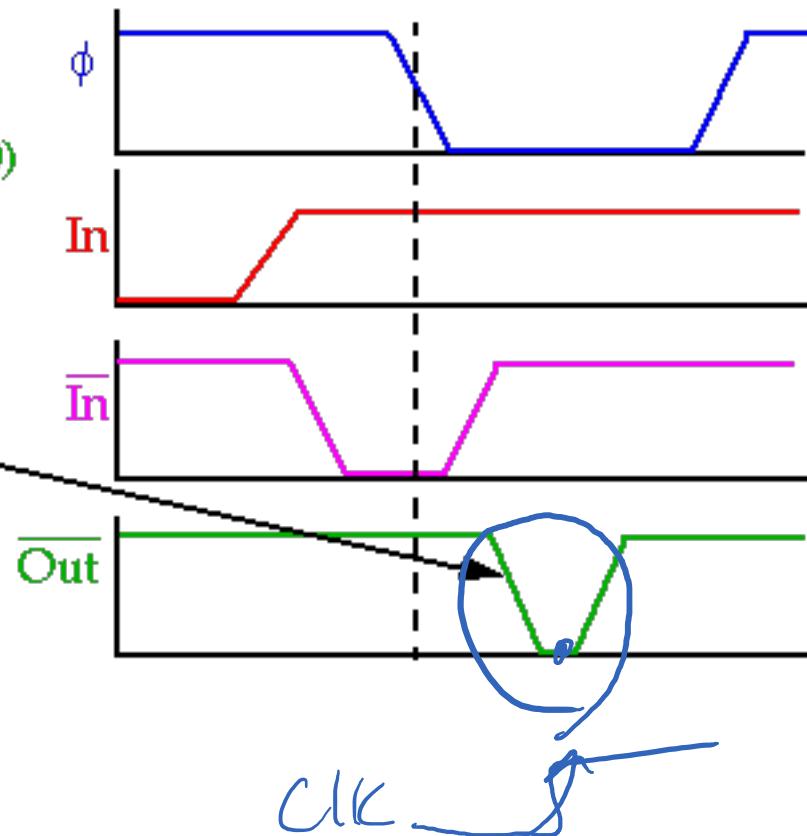Results in a short low-going pulse at the output of N_2 with length approximately equal to the propagation delay through N_1 .




Setup and Hold Time


- **Setup Time**: minimum time the inputs to a flip-flop must be stable before the clock edge
- **Hold Time**: minimum time the inputs to a flip-flop must be stable after the clock edge

Setup Time


time →

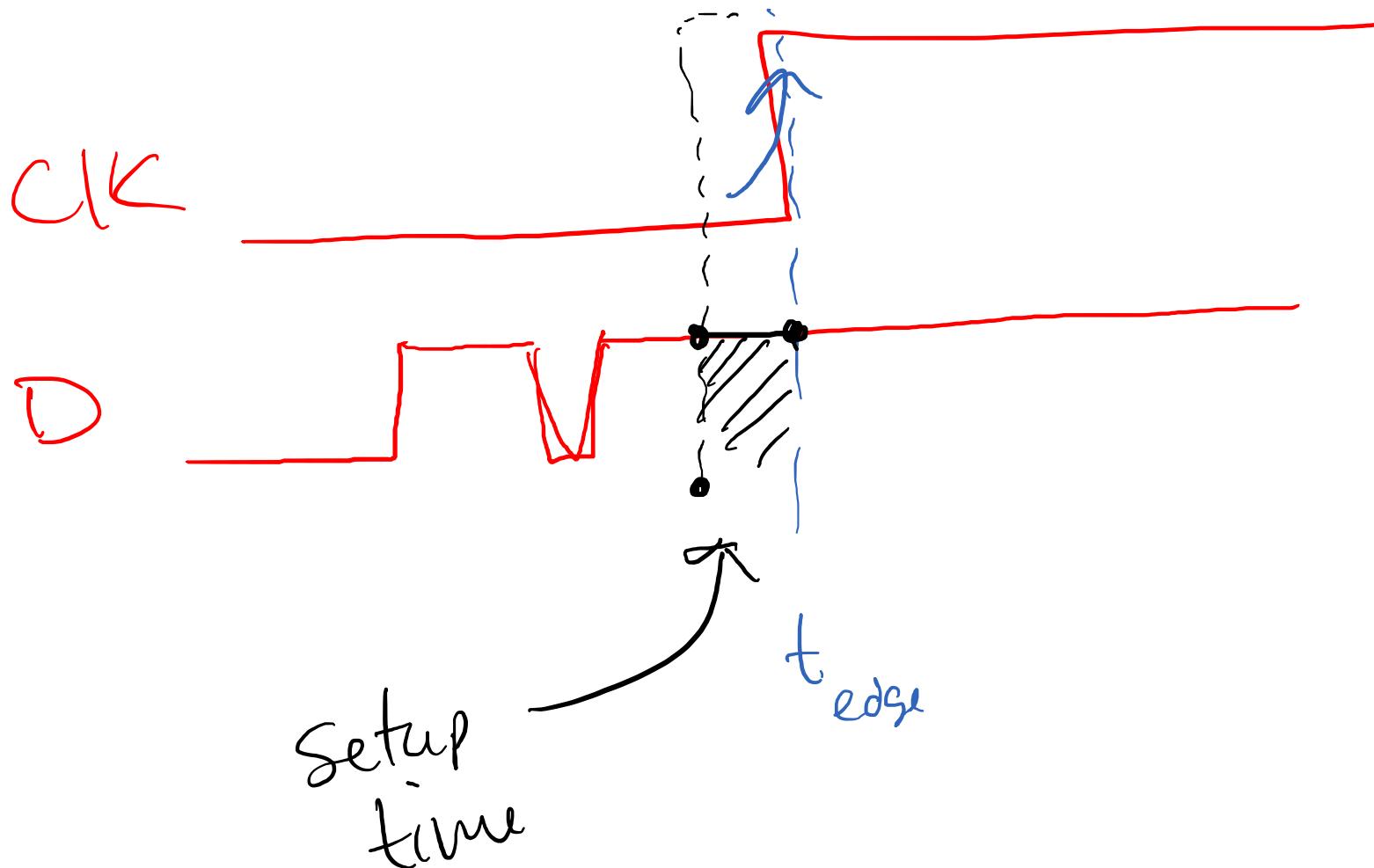


Hold Time

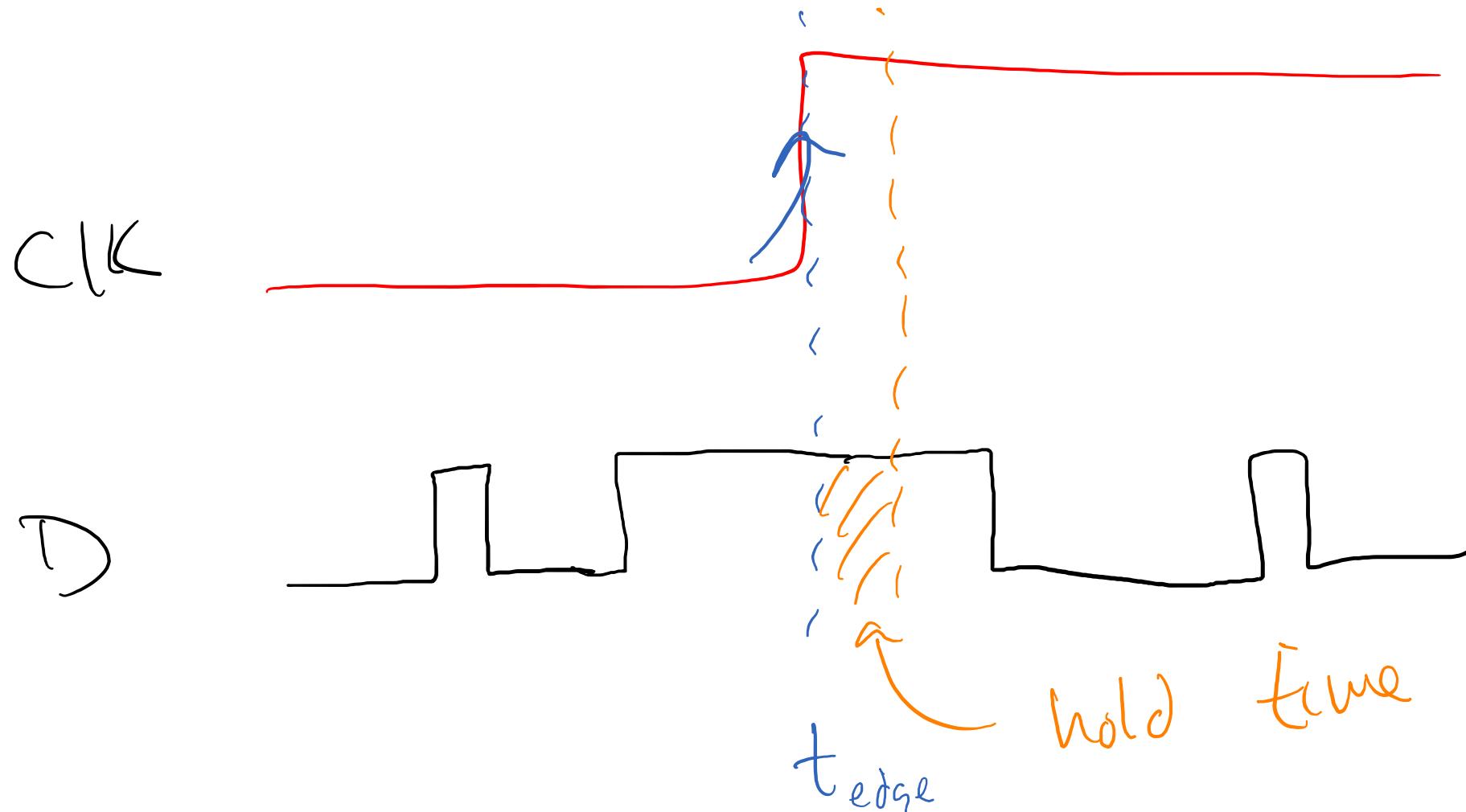

Setup/Hold Time

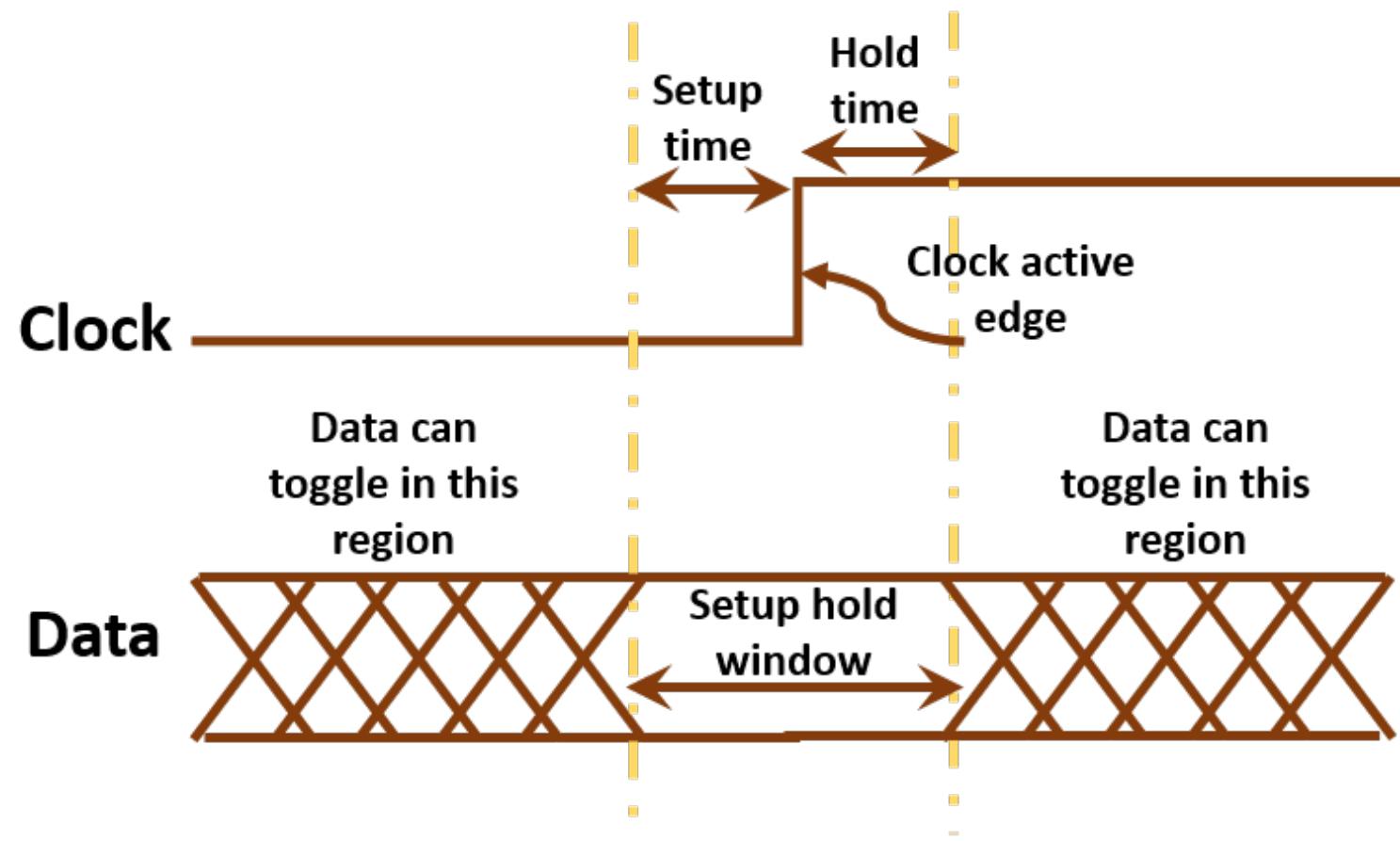


Inter Flip-Flop Timing



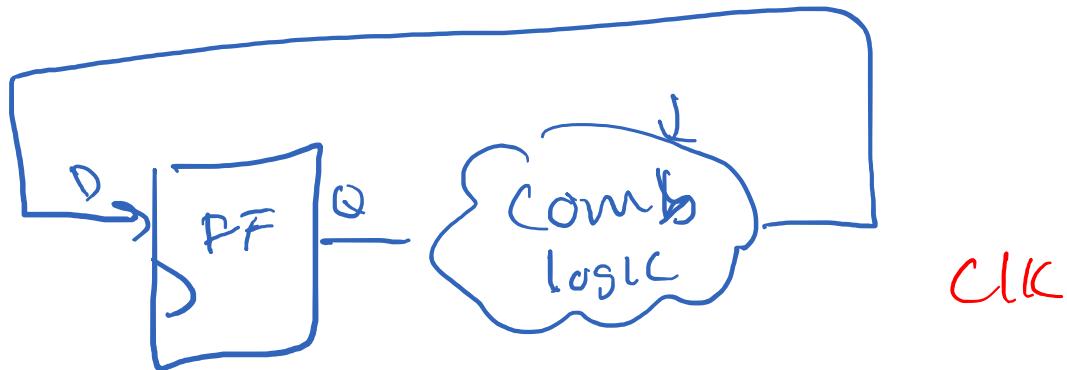


~~St~~
State

next
state

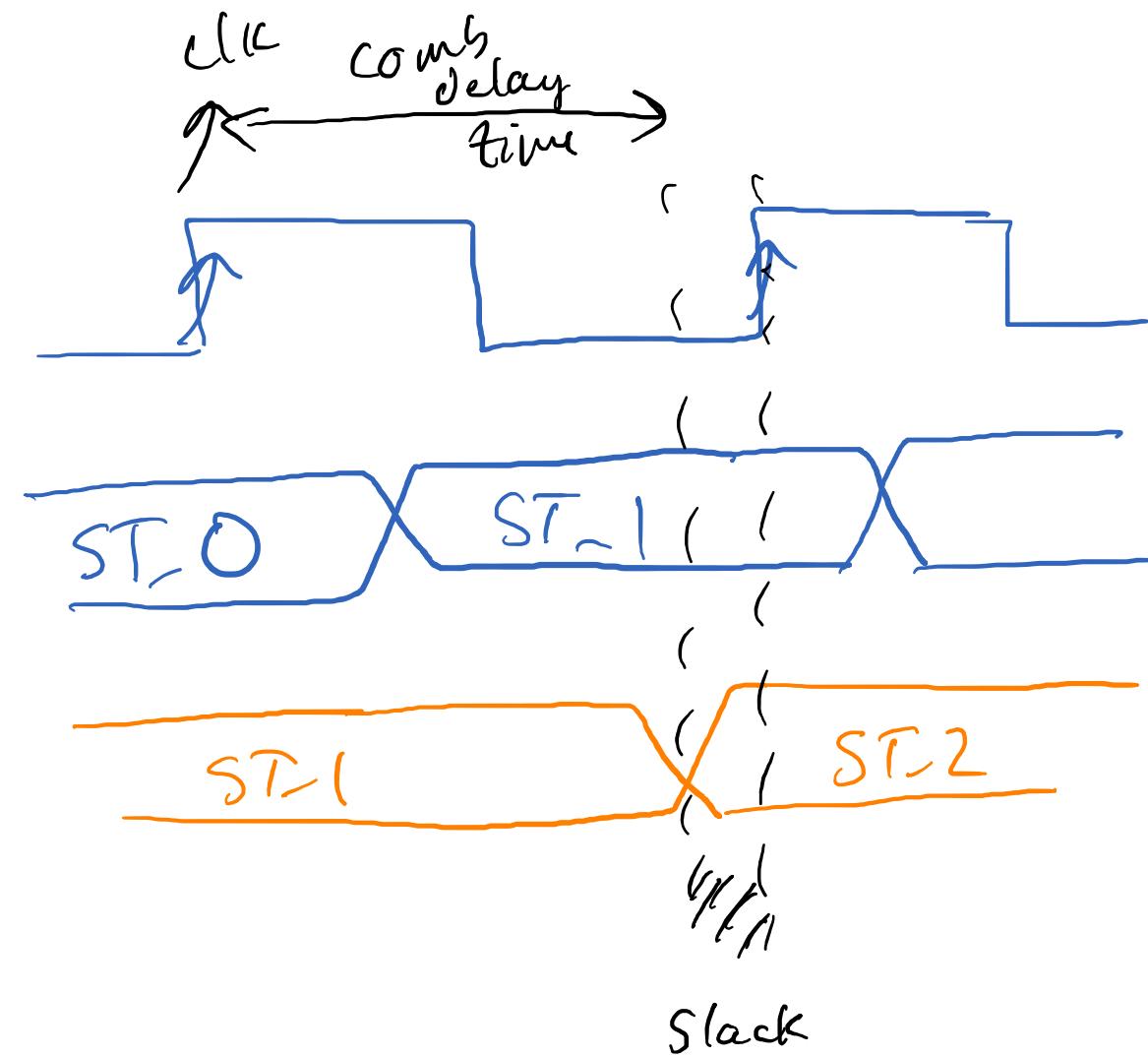


Inter Flip-Flop Timing

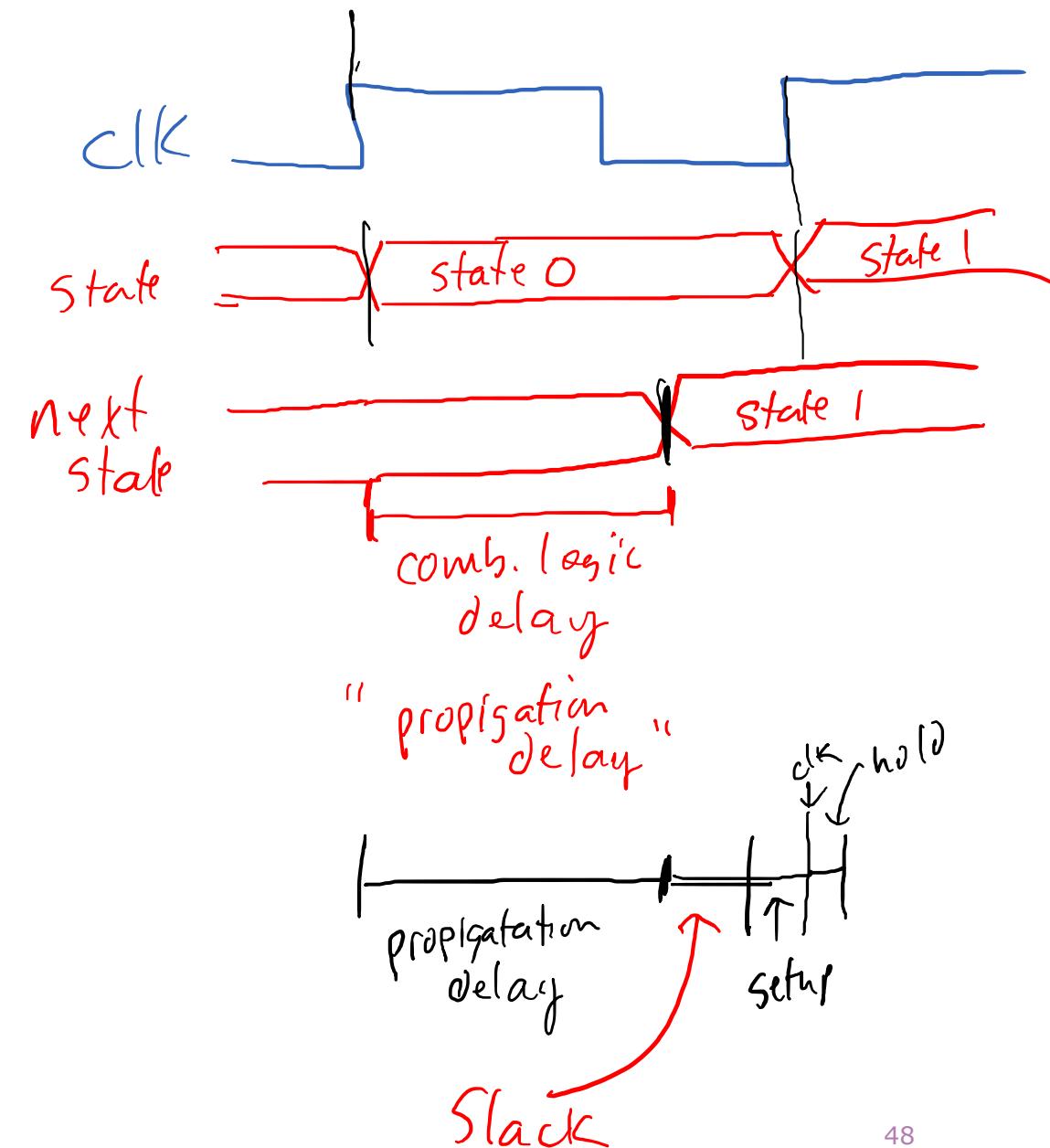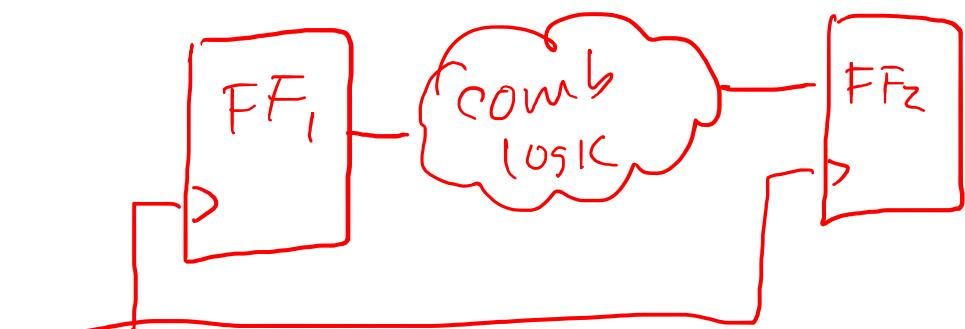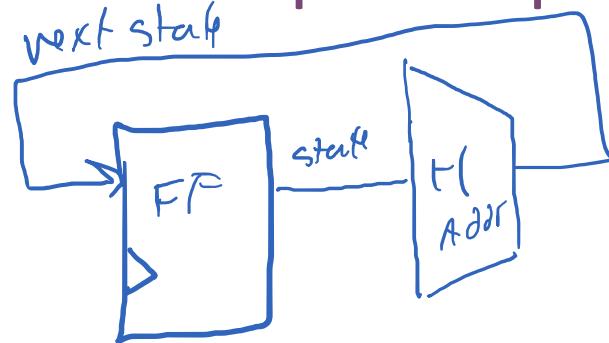

Inter Flip-Flop Timing

Register to register timing:

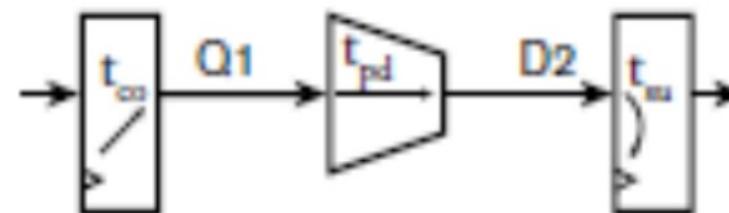- output of a register $Q1$
- some combinational circuit
- input to the next register $D2$




Delays:


- t_{co} , clock to output delay,
- t_{pd} , propagation delay in combinational circuit
- t_c , clock period

Timing requirement:

$$t_{co} + t_{pd} + t_{su} < t_c$$

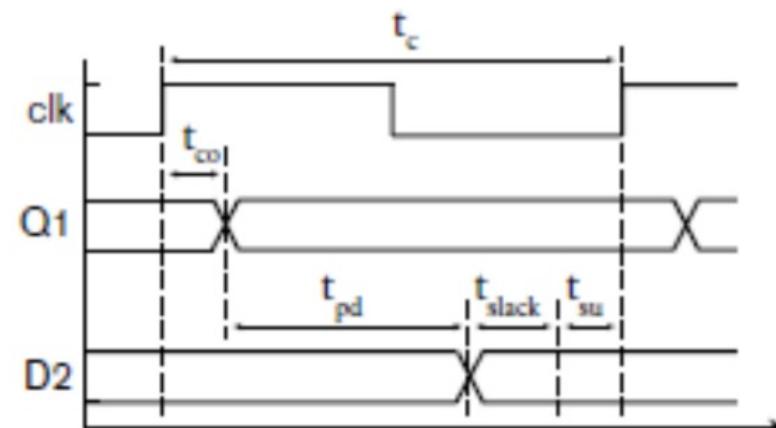

Inter Flip-Flop Timing

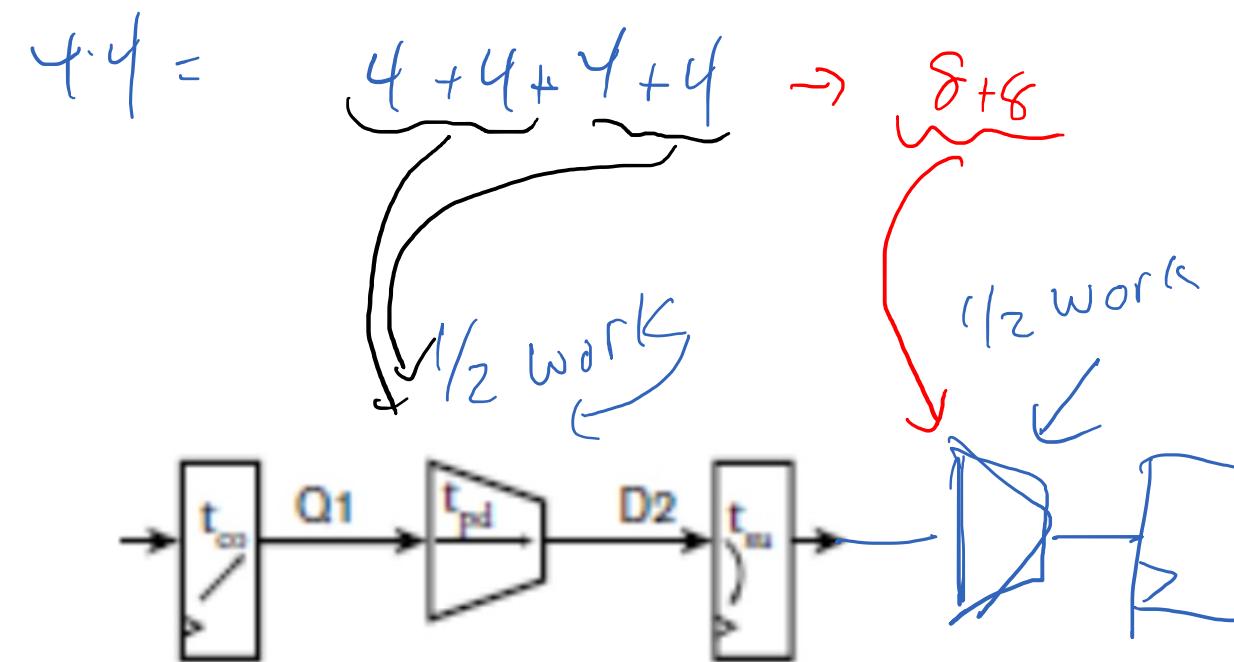

Register to register timing:


- output of a register Q_1
- some combinational circuit
- input to the next register D_2

Delays:



- t_{co} , clock to output delay,
- t_{pd} , propagation delay in combinational circuit
- t_c , clock period

Timing requirement:

$$t_{co} + t_{pd} + t_{su} < t_c$$

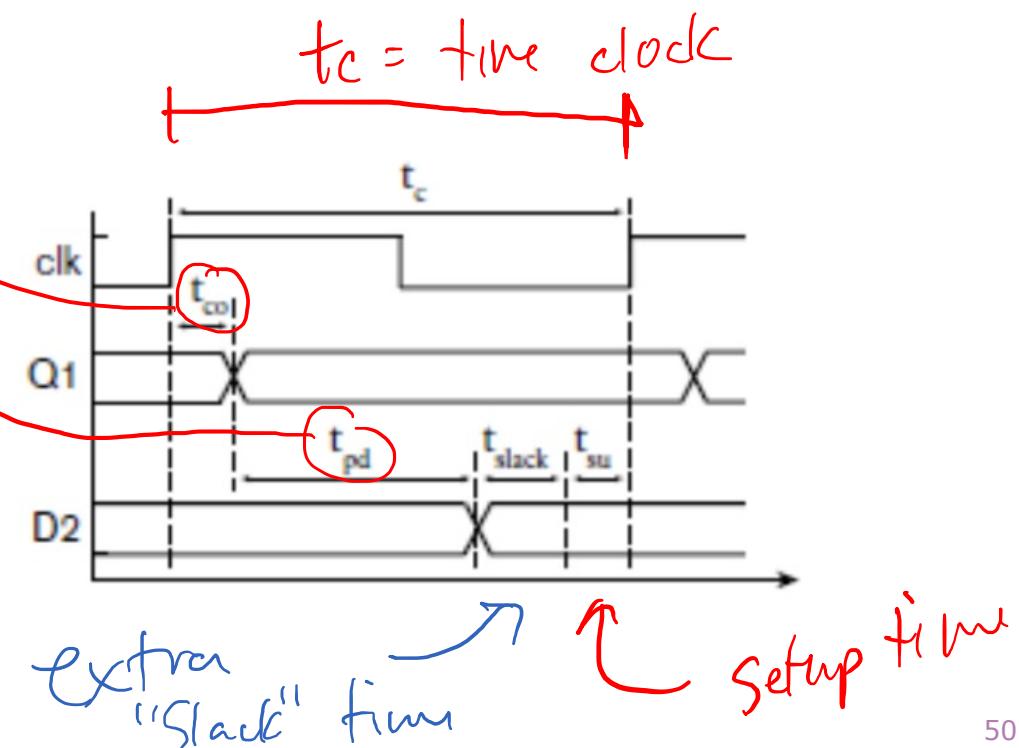

Slack

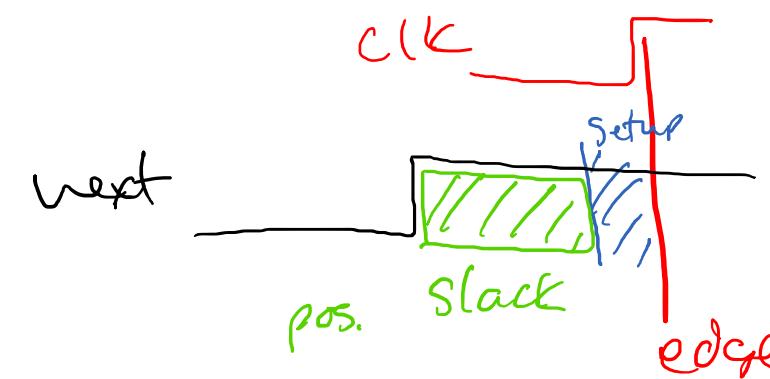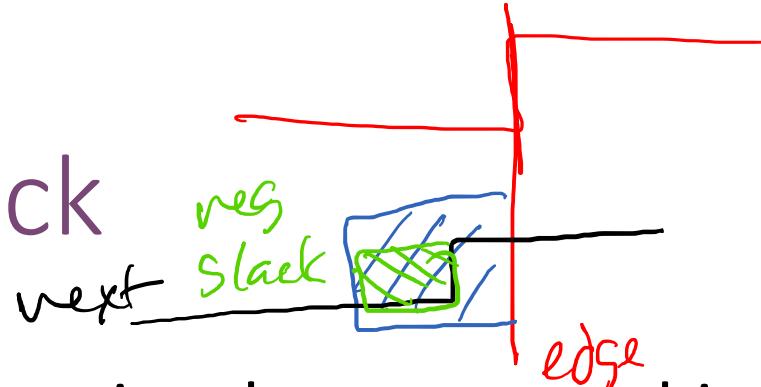

- Extra time between combinational propagation delay and setup time
- Time between stable input to Flip-Flop and next clock edge

- Vivado:
 - WNS: Worst-case Negative Slack



- If this number is <0, your circuit will (probably) not work