

ENGR 210 / CSCI B441  
“Digital Design”

# Tri-State Logic

## FPGAs

Andrew Lukefahr

Course Website

[fangs-bootcamp.github.io](https://fangs-bootcamp.github.io)

Write that down!

# Announcements

- Elevator Controller: You should be done
- UART: Should be starting

Always specify  
defaults for  
**always\_comb!**

**BLOCKING (=) FOR**  
**`always_comb`**

**NON-BLOCKING (<=) for**  
**`always_ff`**

# UART RX/TX LEDs on Basys3

- A word of **caution**:
- The Basys3's **RX + TX LEDs are backwards** from what you expect.
- They are the USB adaptor chip's RX+TX, not the FPGAs.

# Stack with RAMs

push( 4'b 0001)

$head = 00$ ,  $input = 0001$ ,  $Rd\overline{Wr} = 0$ ,  $memEn = 1$

$head \leftarrow head + 1$

push( 4'b 0010)


$head =$

$head = 01$ ,  $input = 0010$ ,  $Rd\overline{Wr} = 0$ ,  $memEn = 1$

$head \leftarrow head + 1$

push( 4'b 0100)


push( 4'b 1000)

 

$head \rightarrow 100$
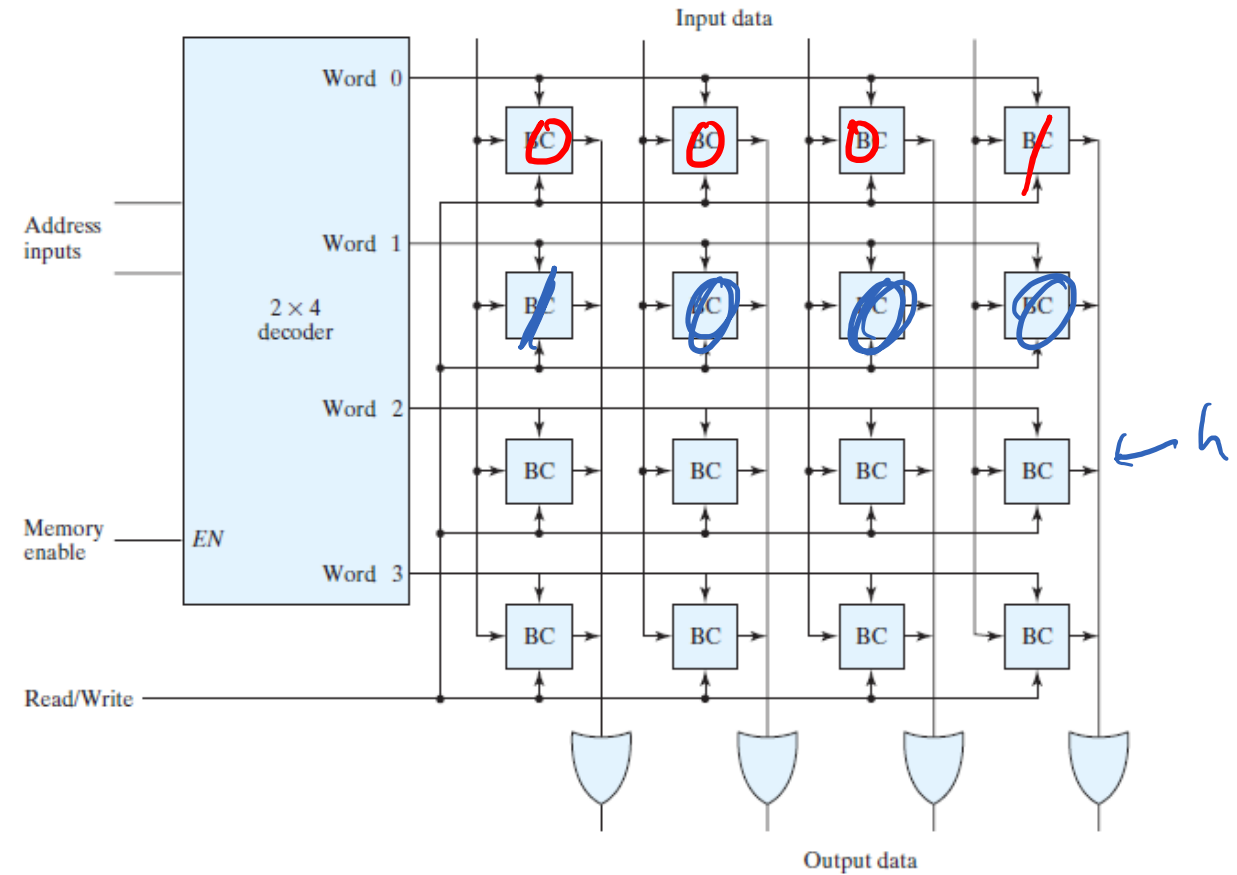
# push/pop with RAMs

push( 4'b 0001) ✓  
push( 4'b 0010) ✓  
push( 4'b 0100) ✓  
pop() ⇒ 0100  
pop() ⇒ 0010  
push( 4'b 1000) ✓  
push( 4'b 0011)  
pop()  
pop()  
push( 4'b 0110)  
pop()






# Busses

- Boolean Logic is bi-state:
  - 1: logical true
  - 0: logical false
  - X: The simulation tools don't know if it's 1 or 0
- So you can't do things like this:
 
# Question: Then how does I2C work?

- I2C: **Inter - Integrated Circuit Communication**



- Clearly multiple “drivers” for 1 wire?

# Answer: A “Tri-State” Bus

- “Tri-State” signals:
  - 1: this is logical true
  - 0: this is logical false
  - X: The simulation tools don’t know if it’s 1 or 0
  - Z: this is “high impedance”
- Z: High Impedance
  - Stop driving a logical value
  - Pretend I’m not connected


# Tri-State logic

```
wire enable;  
wire enabled_output = 'h0;  
wire tri;  
assign tri = (enable ? enabled_output : 'hZ);
```

# Tri-State Bus



# Problems with Tri-State Logic

- What if two signals “drive” at once?

 


Solution: Don't Do That!

# Review: RAM

  



# Look-Up Table (LUT)

 


- DON'T compute a Boolean equation
- DO pre-compute all solutions in a table
- DO look up the Boolean result in the table

- Examples:

$$s = a \wedge b;$$

$$c = a \& b;$$

 


<u>a</u>	<u>b</u>	<u>Sum</u>	<u>carry</u>
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

# RAM to LUT


- Can I use a RAM to build a Half-Adder LUT?

$$s = a \oplus b;$$




$$c = a \& b;$$

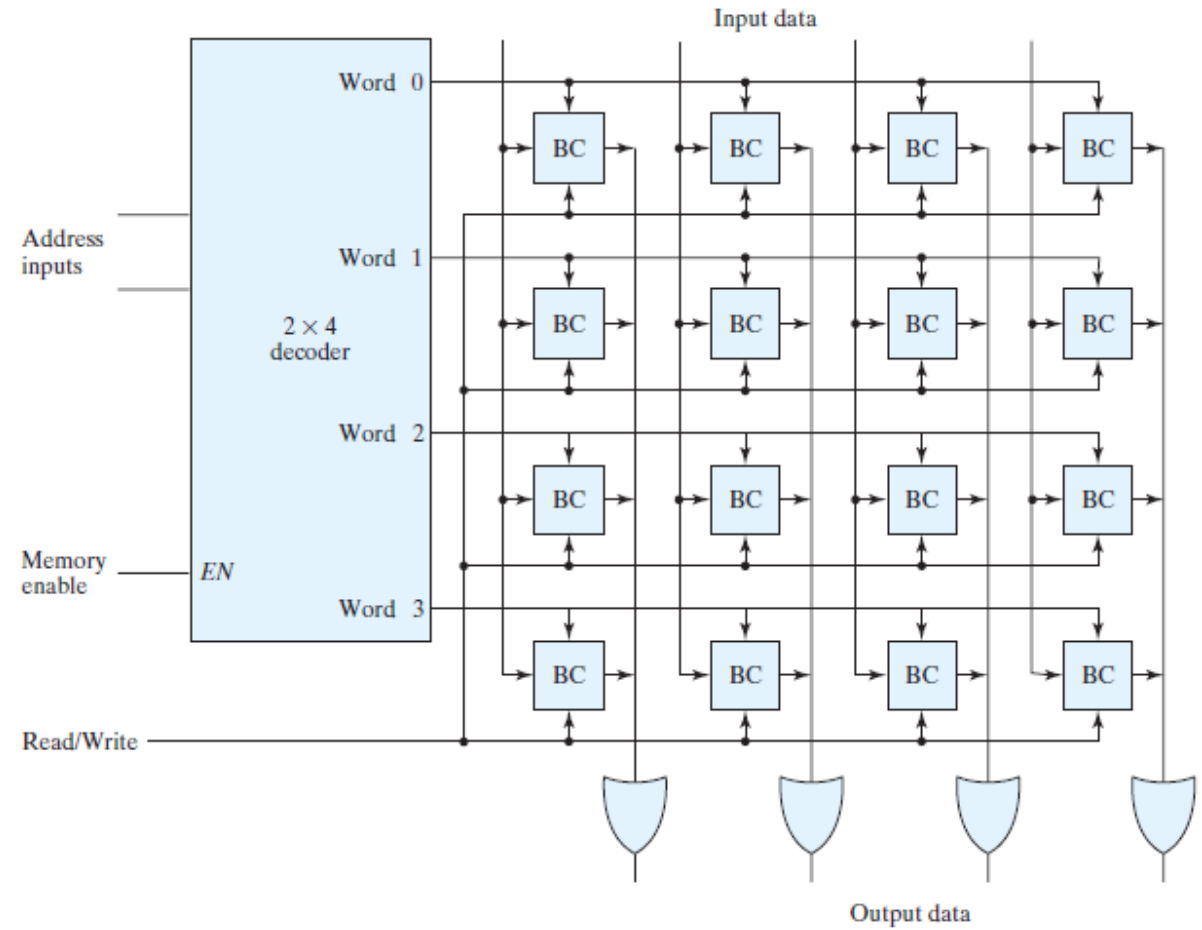




# Full-Adder LUT

 

Input			Output	
A	B	Cin	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

   

# N-input, M-output LUT

   


# LUT size

1 output

~~3 in~~


- Why not a 1000-input, 100-output LUT?

 

- 3 inputs  $\Rightarrow 2^3$  rows = 8 rows  $\leftarrow 3_{in}, 1_{out}$
- 4 inputs  $\Rightarrow 2^4$  rows = 16 rows  $\leftarrow 4_{in}, 1_{out}$
- 5 inputs  $\Rightarrow 2^5$  rows = 32 rows
- ...
- 64 inputs  $\Rightarrow 2^{64}$  rows =  $1.85 \times 10^{19}$  rows

- LUT input size does not scale well.

2 output

 

$$8 \cdot 2 = 16$$


$$16 \cdot 2 = 32$$

$$32 \cdot 2 = 64$$

...

# Divide and Conquer with LUTs


- 3-Bit Full Adder

 

a n n

# Sequential Logic

 - Problem: How do we handle sequential logic?
  - LUTs cannot contain state
- Solution: Add a Flip-Flop



# Basic Logic Element (BLE)

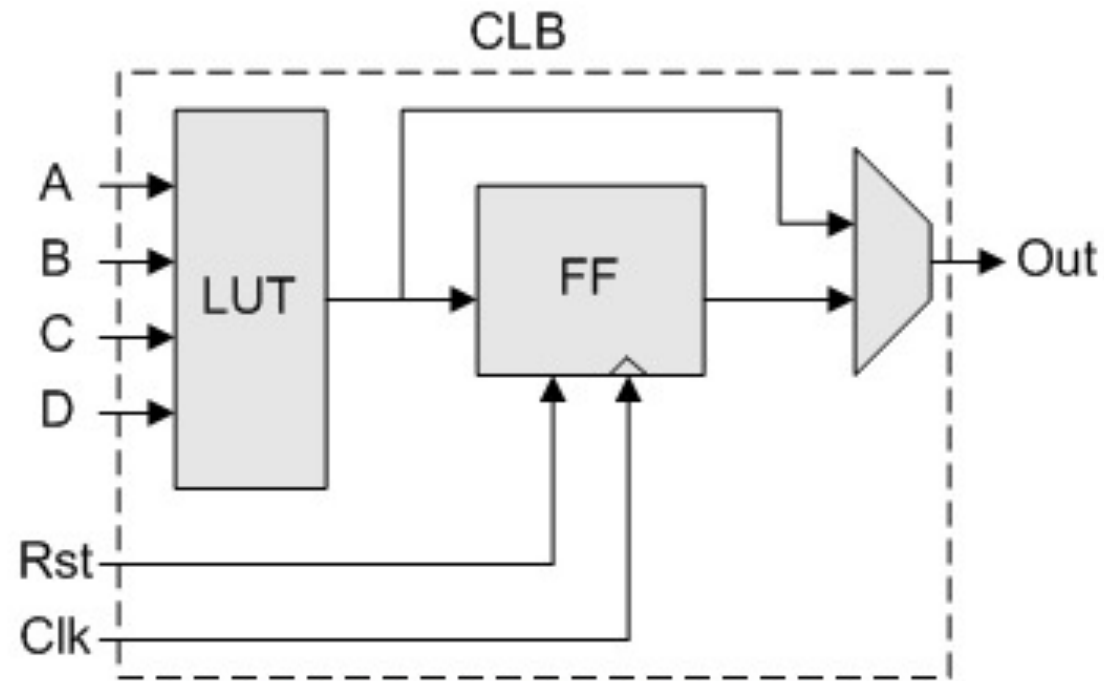


Fig.4 Example of Configurable Logic Cell.



# Basic Logic Element (BLE)

- What if I only want to store a value?

A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1


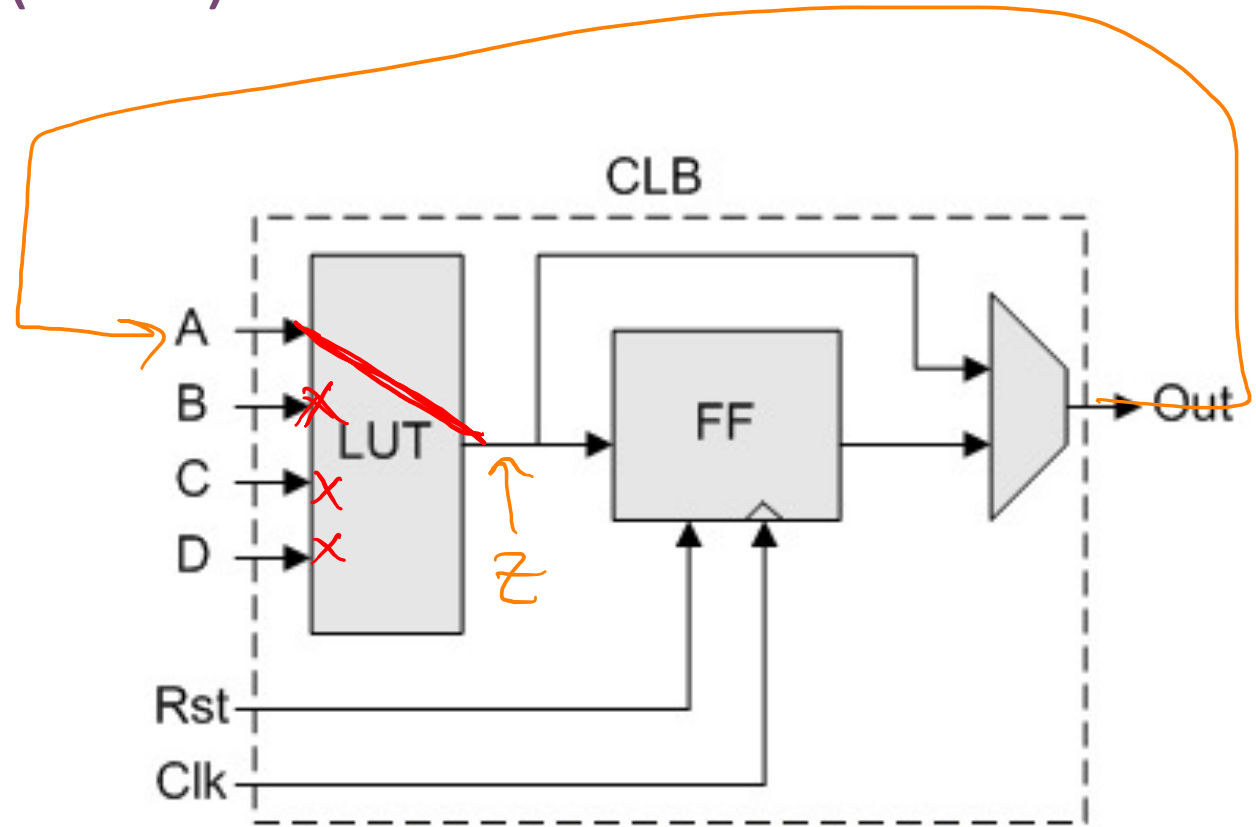



Fig.4 Example of Configurable Logic Cell.

6 input, 4 output CLB


## Improved BLE

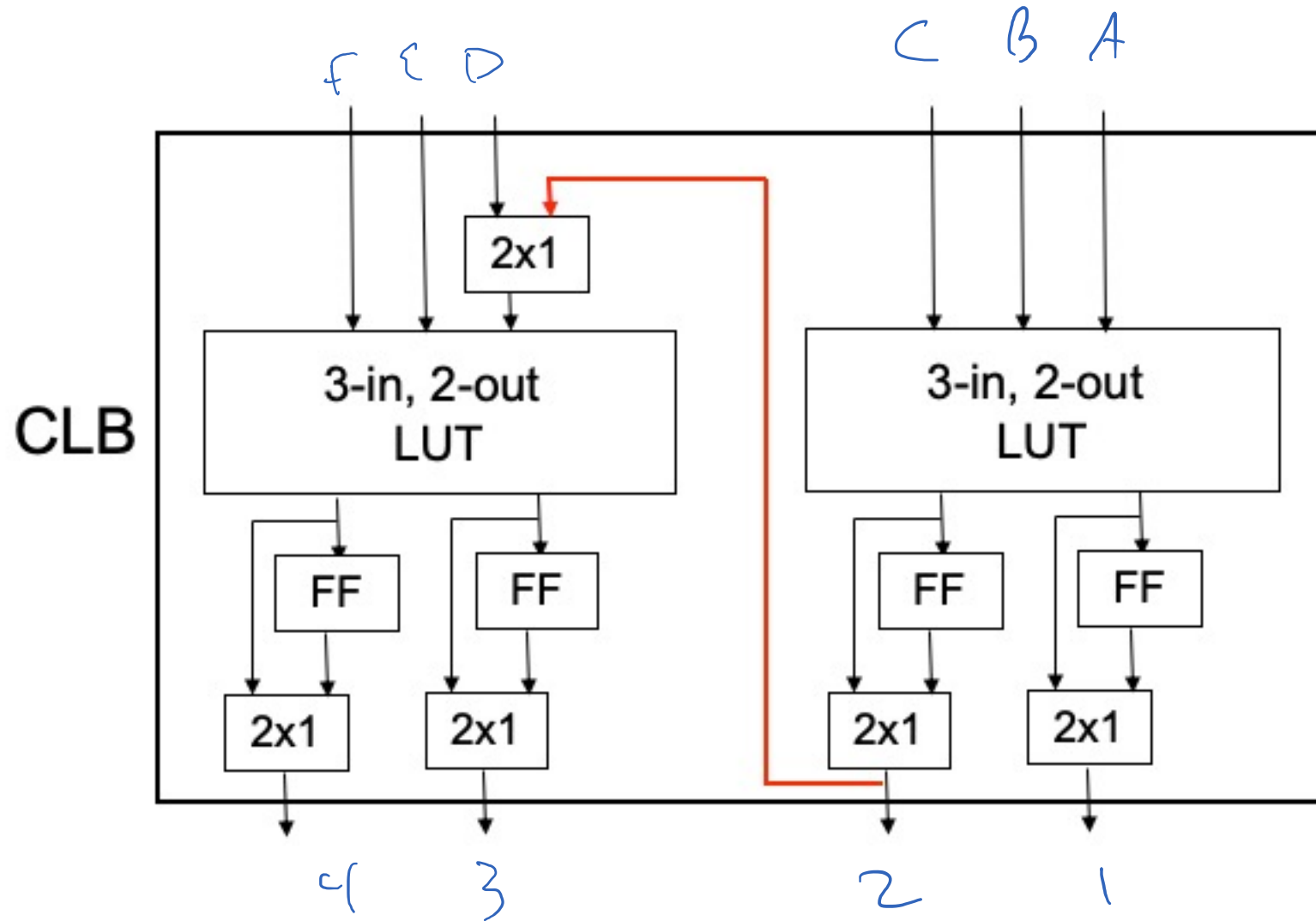


## 2-Bit Ripple-Carry w/ BLE

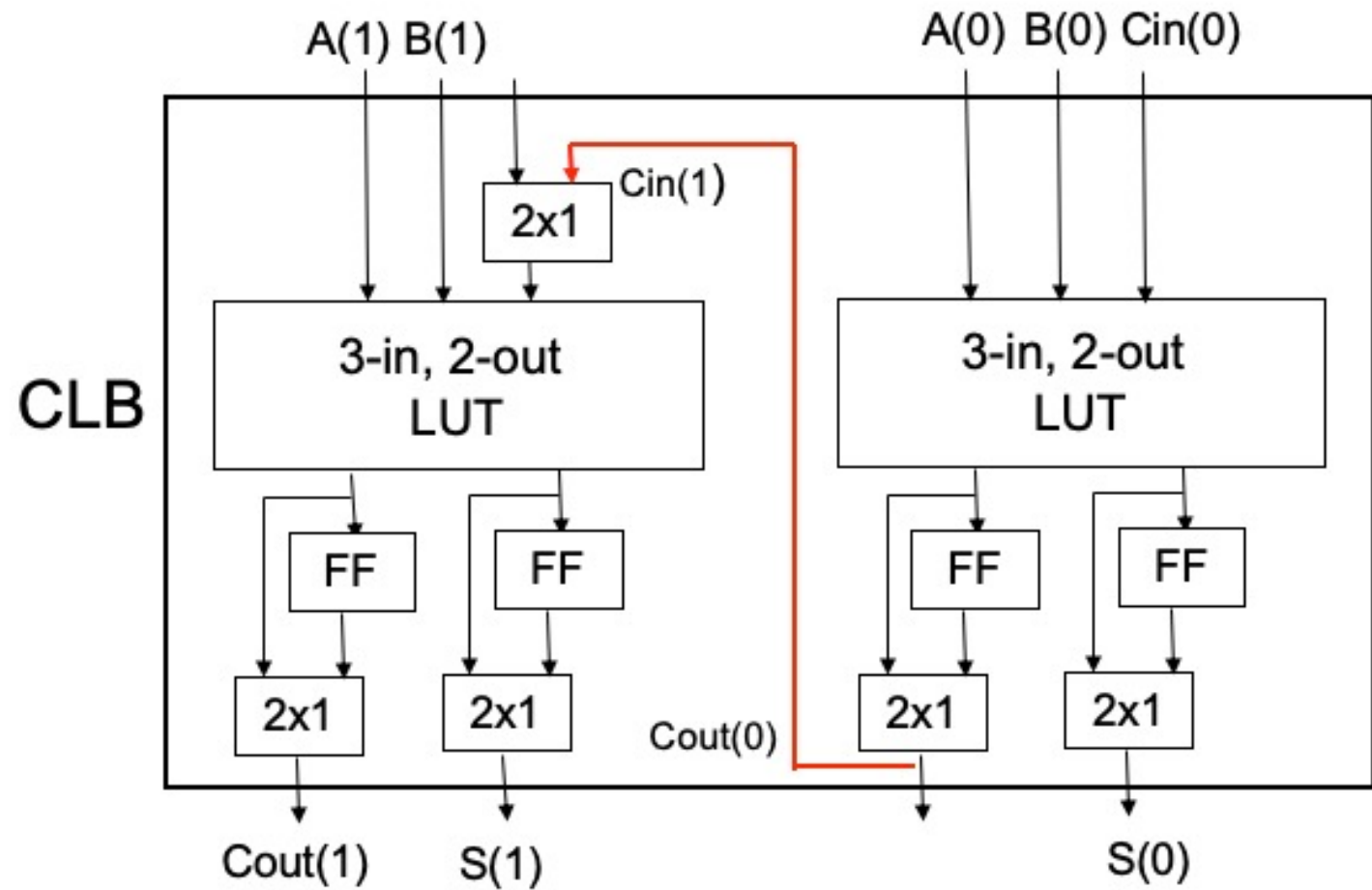

# Realistic BLE: Xilinx

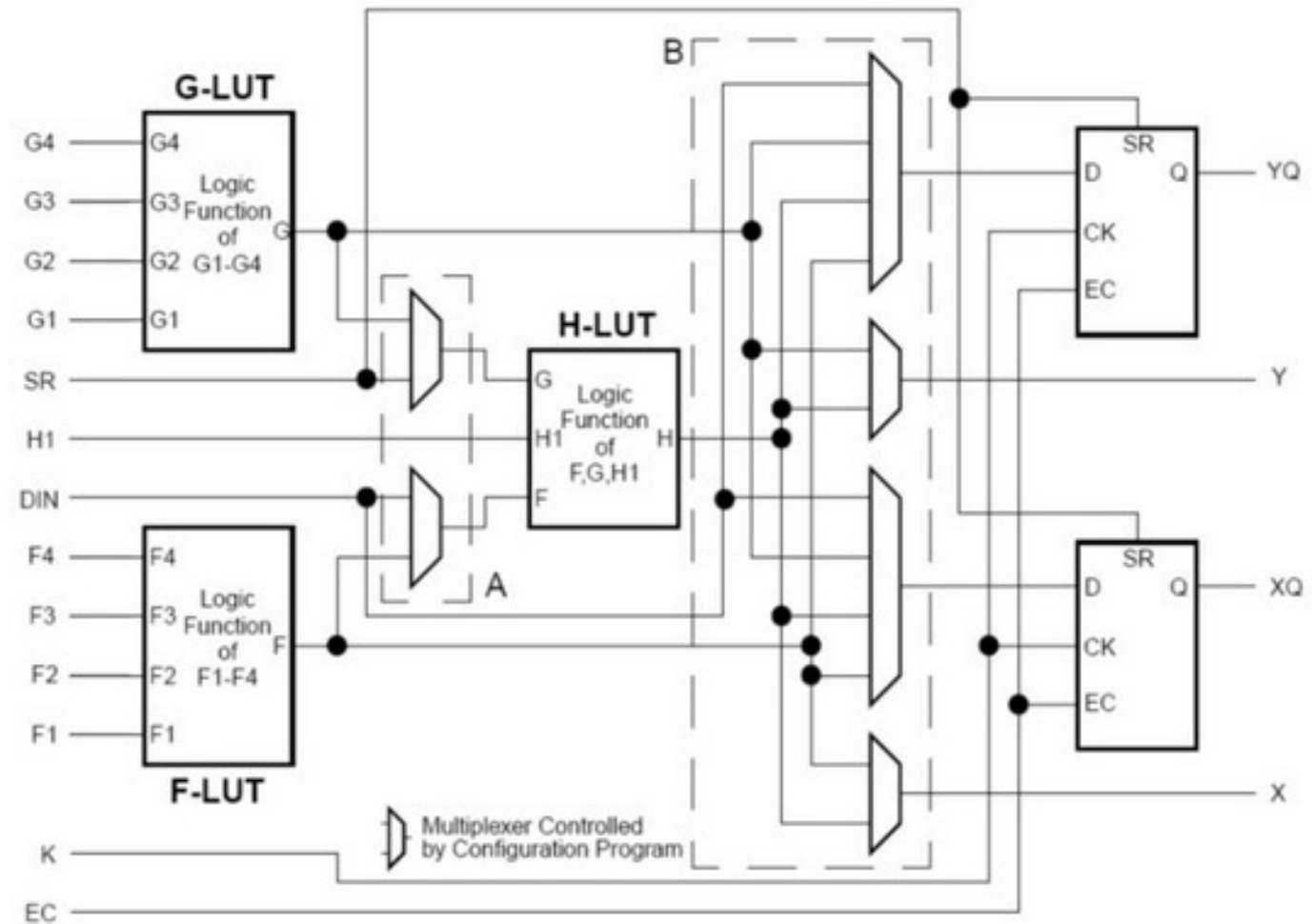


# CLBs: Configurable Logic Block

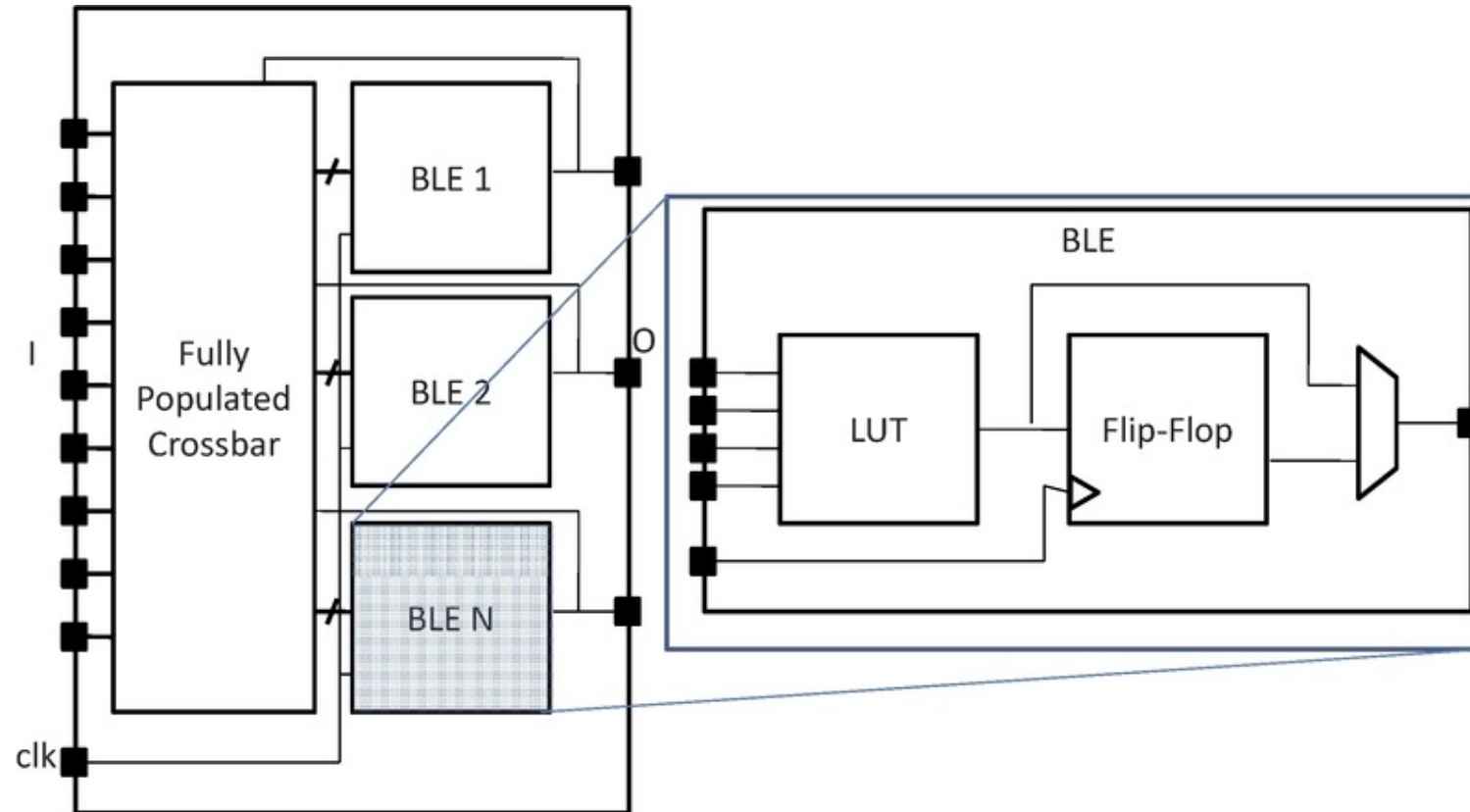

 
# Connecting CLBs

- Q: How do CLBs talk to each other?
- A: Put wires everywhere!



 
# Connecting CLBs

- Q: How do CLBs talk to each other?
- A: Put wires everywhere (ok, almost everywhere)!



 
# How to connect CLBs to wires?

- “Connection box”
  - Device that allows inputs and outputs of CLB to connect to different wires






# Connection Box Flexibility

 


*\*Dots represent **possible** connections*

# How to connect wires to each other?

 

 
# Switch Box


- Connects horizontal and vertical routing channels




# Switch Box Connections

 

 - Programmable connections between inputs and outputs





*Wilton*

 


*\*Not all possible connections shown*

# Switch Box Connections

  

# FPGA “Fabric”


- 2D array of CLBs + interconnects

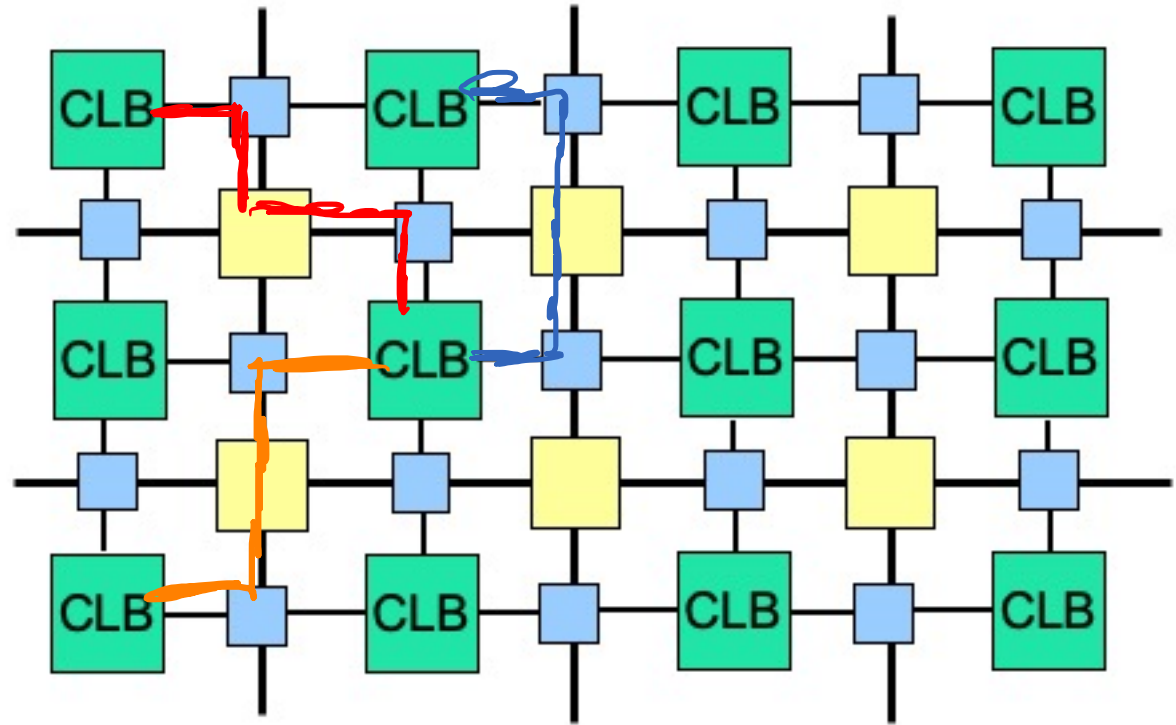

- Am I missing anything?

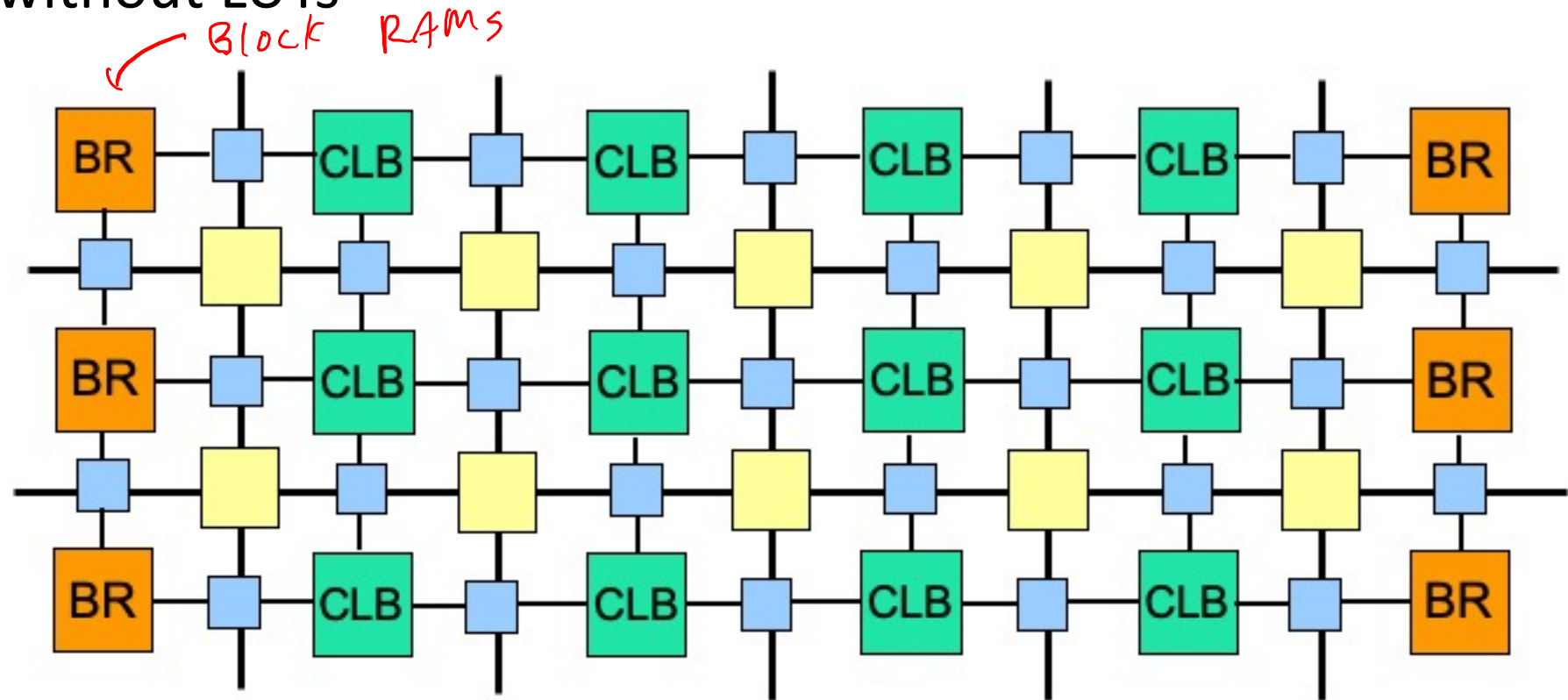
# Block RAM

- Special blocks of just RAM
- Big CLBs without LUTs



DSPs → Digital Signal Processor → dedicated math units

multiply

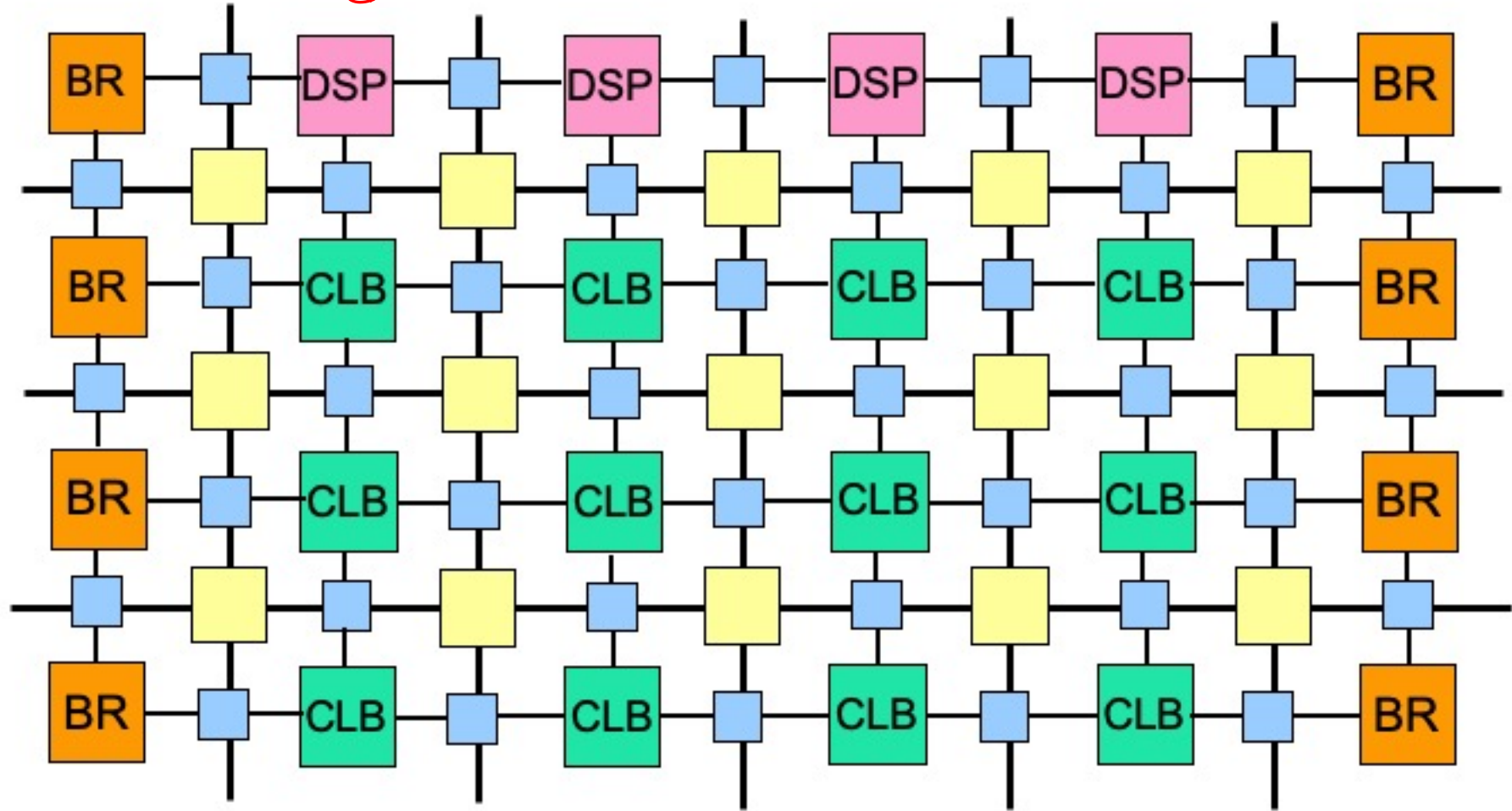



# Input/Output (IO)

