

Memory II

Andrew Lukefahr

Always specify
defaults for
always_comb!

BLOCKING (=) FOR
`always_comb`

NON-BLOCKING (<=) for
`always_ff`

UART RX/TX LEDs on Basys3


- A word of **caution**:
- The Basys3's **RX + TX LEDs are backwards** from what you expect.
- They are the USB adaptor chip's RX+TX, not the FPGAs.

ROM vs RAM

- ROM – Read-Only Memory
 - Input: address
 - Output: fixed value
- RAM – Random-Access Memory
 - Read/Write version of a ROM

ROM in Verilog
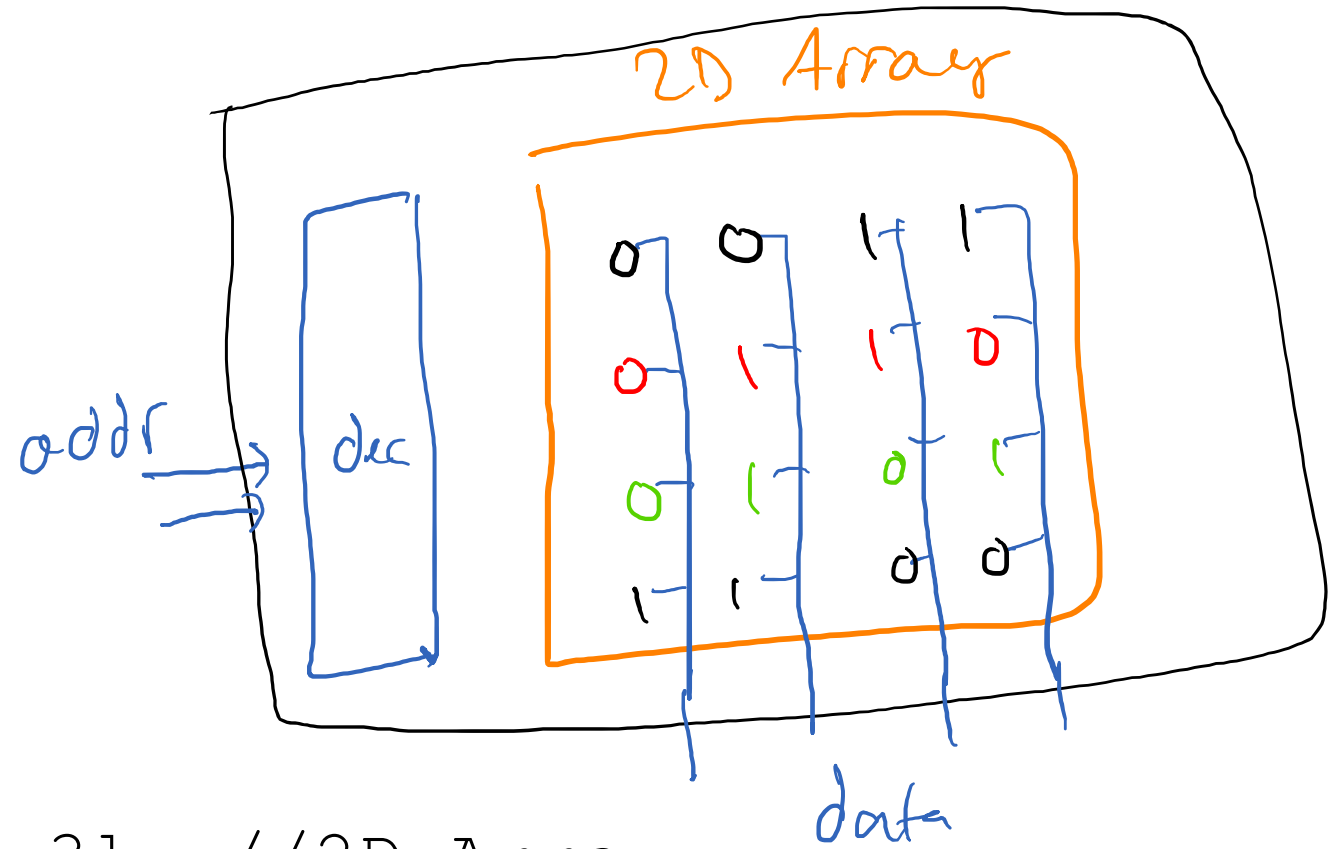
```
module ROM (  
    input [1:0] addr,  
    output [3:0] data  
)  
    logic [3:0] array [0:3]; //2D Array  
    assign array = { 4'b0011, 4'b0110, 4'b0101, 4'b1100 }  
    assign data = array[addr]; ← select a row for output  
endmodule
```



Flip-Flop RAM in Verilog

```
module RAM (  
    input      clk,  
    input [1:0] addr,  
    input      set,  
    input [3:0] set_data,  
    output [3:0] read_data  
)  
    logic [3:0] array [0:3]; //2D Array  
    always_ff @(posedge clk) begin  
        if (set) array[addr] <= set_data;  
    end  
    assign read_data = array[addr];  
endmodule
```


Stacks

- First-In-Last-Out data structure

- Defines two operations:

- `push(x)`: adds an element to the end of the stack
- `X = pop()`: returns most recently-added element from the stack


`push(1)`
`push(2)`
`pop()` → 2

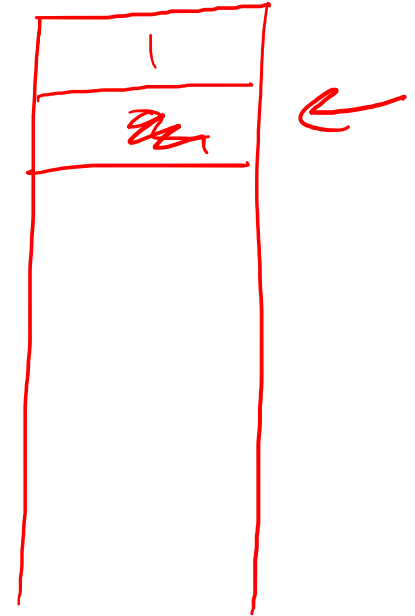


Stacks

- In C/C++:
 - Can grow to (near) arbitrary sizes
 - Implemented with linked lists
 - `malloc()` allows more memory for bigger stacks
- In Hardware:
 - Don't have `malloc()`
 - Can't get "more gates"
 - Fixed size!

Stacks

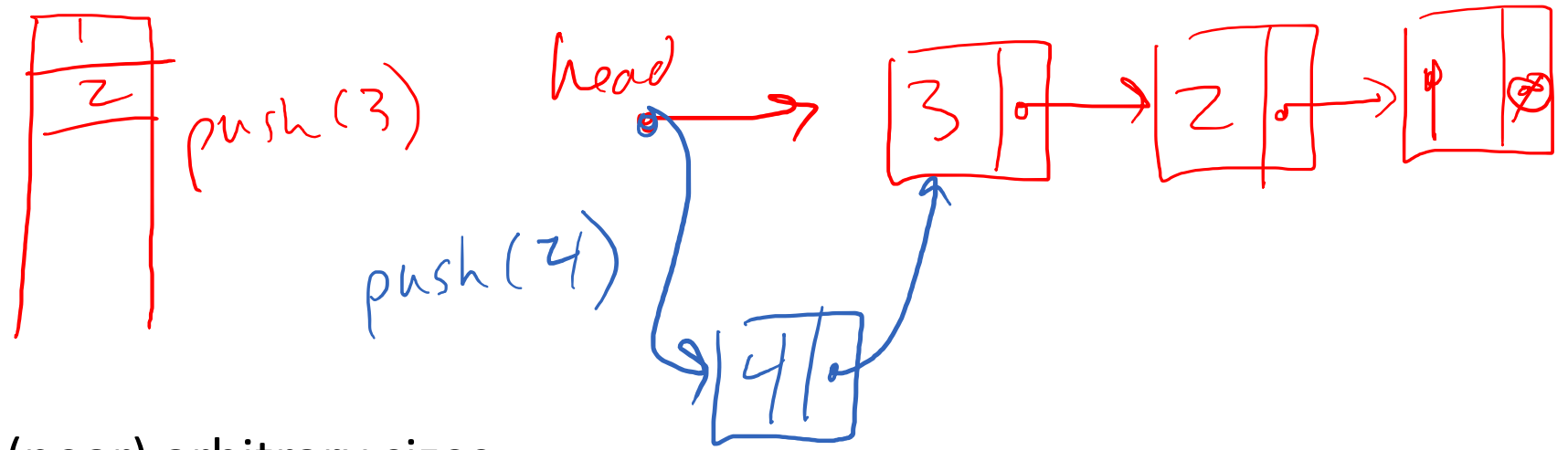


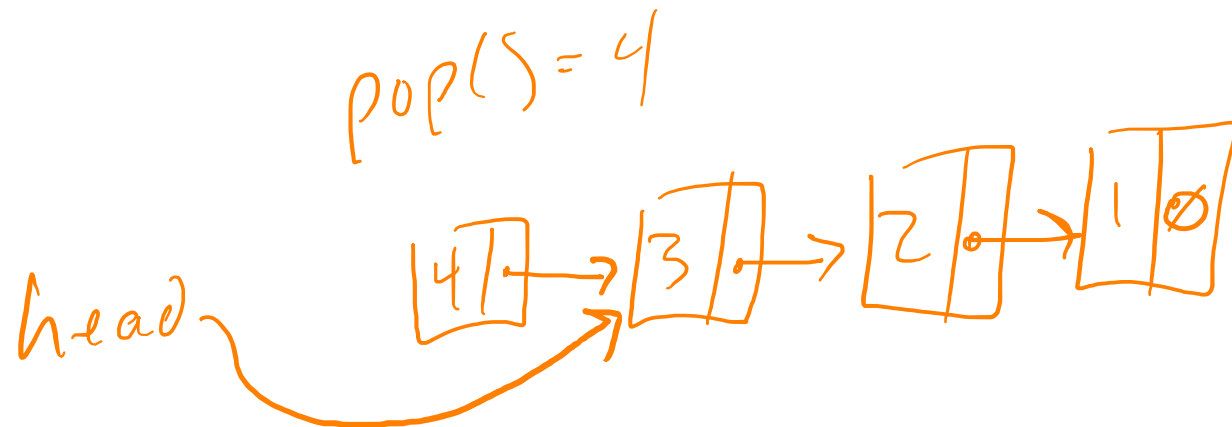- In C/C++:
 - Can grow to (near) arbitrary sizes
 - Implemented with linked lists
 - `malloc()` allows more memory for bigger stacks
- In Hardware:
 - Don't have `malloc()`
 - Can't get "more gates"
 - Fixed size!



Fixed-Size Stacks

- Use an array as a fixed-size stack

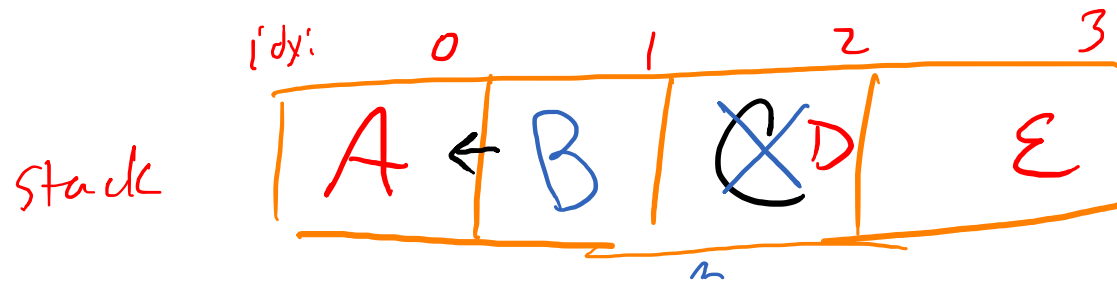

head = NULL or

head = 2



push(A)
push(B)
push(C)
pop()
push(D)
push(E)

Python Example

```
PUSH [1, 0, 0, 0] 1
PUSH [1, 2, 0, 0] 2
PUSH [1, 2, 3, 0] 3
POP: 3
POP [1, 2, 3, 0] 2
POP: 2
POP [1, 2, 3, 0] 1
POP: 1
POP [1, 2, 3, 0] 0
```

```
RAM = [ 0, 0, 0, 0]
head = 0

def push(x):
    global RAM, head
    RAM[head]=x
    head += 1
def pop():
    global RAM, head
    head -= 1
    return RAM[head]

push(1)
print ("PUSH ", RAM, " ", head)
push(2)
print ("PUSH ", RAM, " ", head)
push(3)
print ("PUSH ", RAM, " ", head)

print ('POP: ', pop())
print ("POP ", RAM, " ", head)
print ('POP: ', pop())
print ("POP ", RAM, " ", head)
print ('POP: ', pop())
print ("POP ", RAM, " ", head)
```

```

RAM = [ 0, 0, 0, 0]
head = 0

def push(x):
    global RAM, head
    RAM[head]=x
    head += 1
def pop():
    global RAM, head
    head -= 1
    return RAM[head]

push(1); push(2); push(3)
pop(); pop()
push(4)

print (RAM, " ", head)

```

```


PUSH [1, 0, 0, 0] 1
PUSH [1, 2, 0, 0] 2
PUSH [1, 2, 3, 0] 3
POP: 3
POP [1, 2, 3, 0] 2
POP: 2
POP [1, 2, 3, 0] 1
PUSH [1, 4, 3, 0] 2

```

The stack values: [1, 4]


Fixed-Size Stack in Hardware

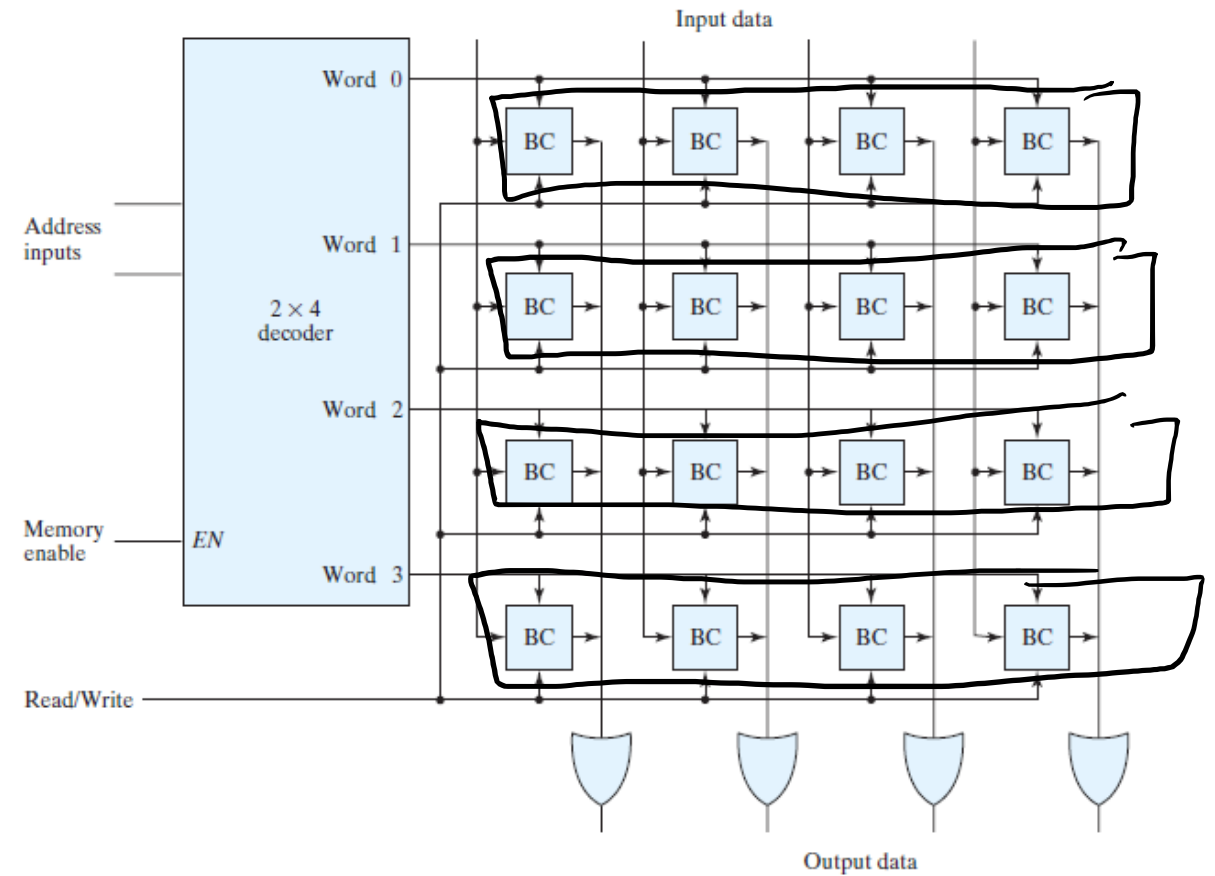- We can use a RAM block as a stack
- Just need to add head index




Stack with RAMs

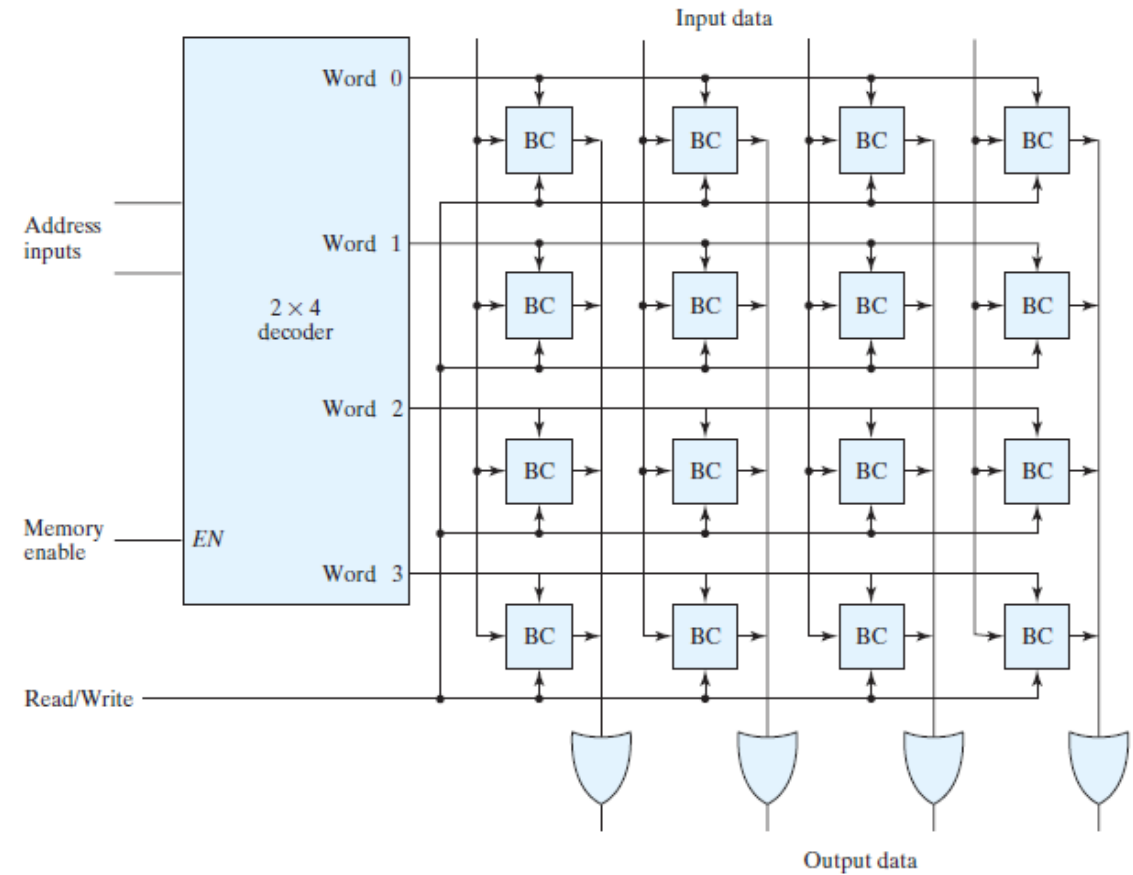- Given: RAM array (shown)
- Make: 4-element 4-bit **Stack**
 - Recall: First-In-Last-Out
- Tip: Use a state machine!



Stack with RAMs

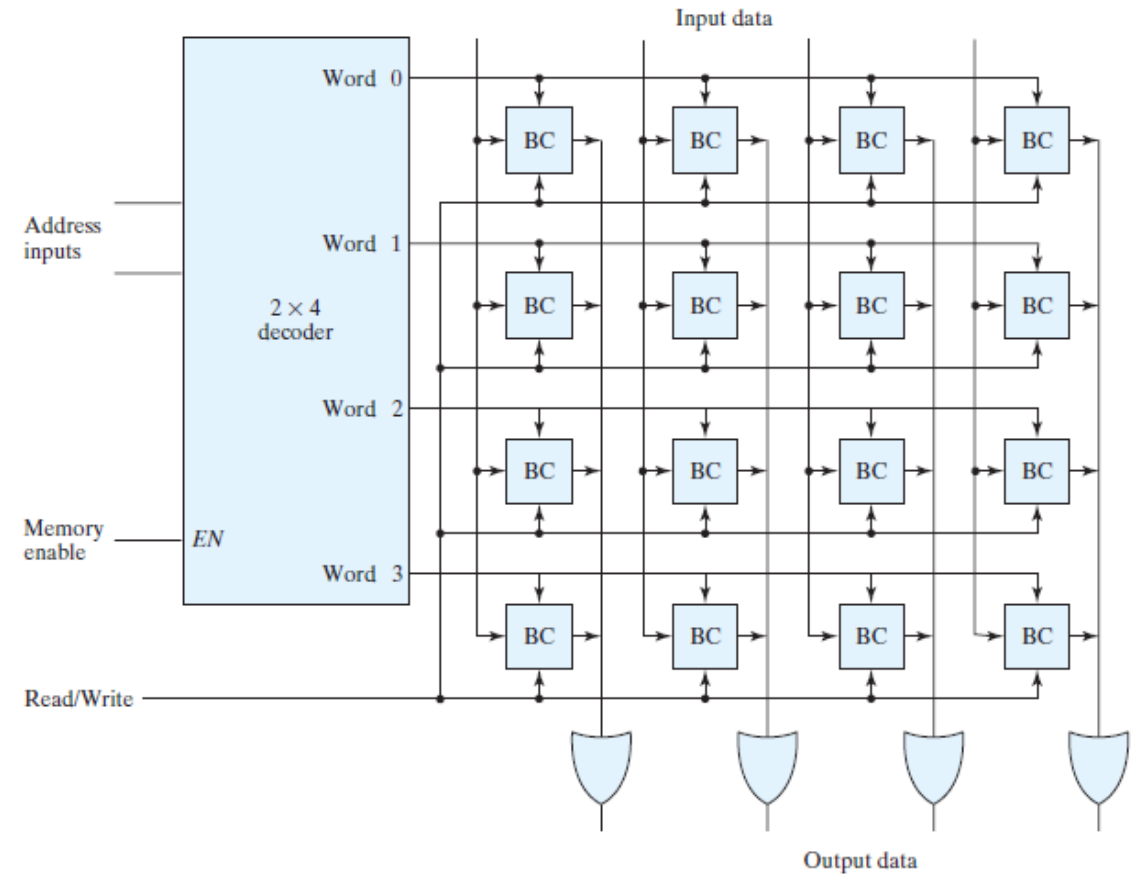- Two stack “functions”
 - push:
 - Adds element to stack
 - `push(4'b XXXX)`
 - pop:
 - Removes element from stack
 - `4'bXXXX = pop()`




Stack with RAMs

push (4'b 0001)

push (4'b 0010)

push (4'b 0100)

push (4'b 1000)

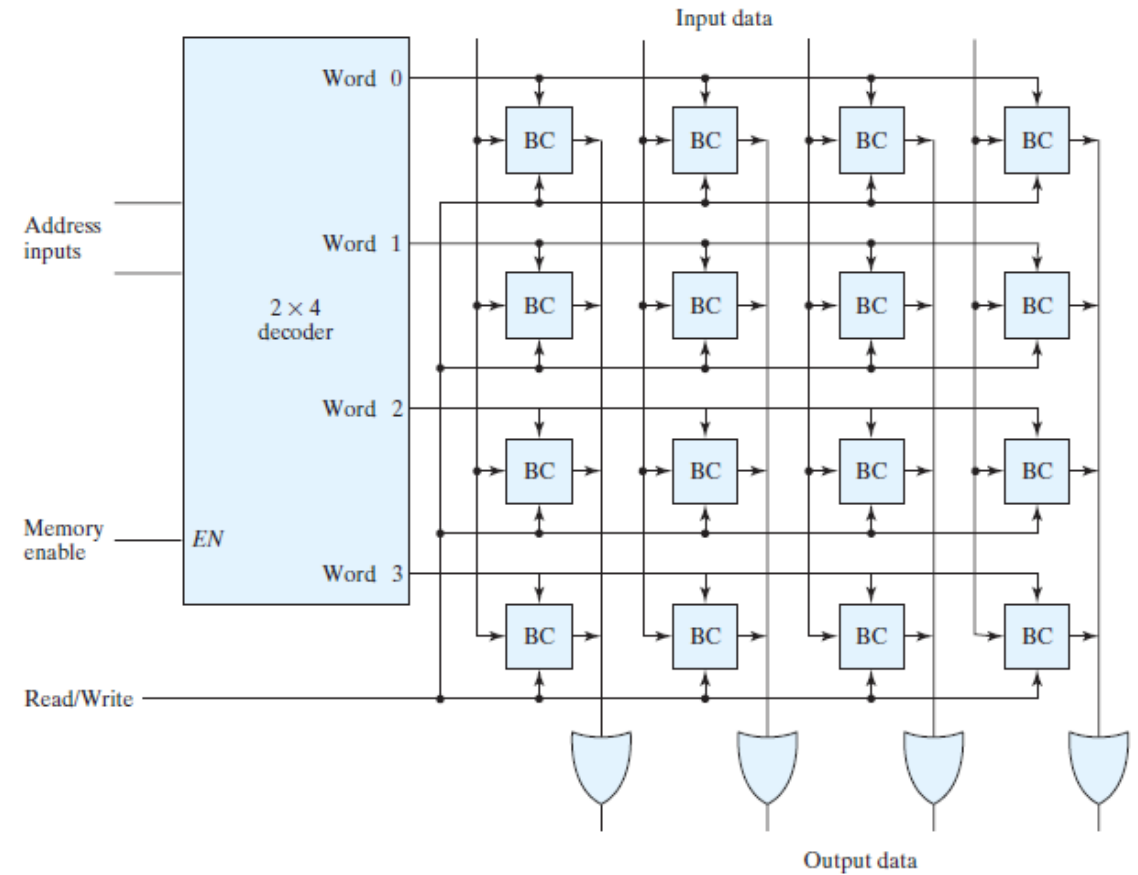

Stack with RAMs

push(4'b 0001)

$head = 00$, $input = 0001$, $Rd\overline{Wr} = 0$, $memEn = 1$

$head \leftarrow head + 1$

push(4'b 0010)


$head =$

$head = 01$, $input = 0010$, $Rd\overline{Wr} = 0$, $memEn = 1$

$head \leftarrow head + 1$

push(4'b 0100)


push(4'b 1000)

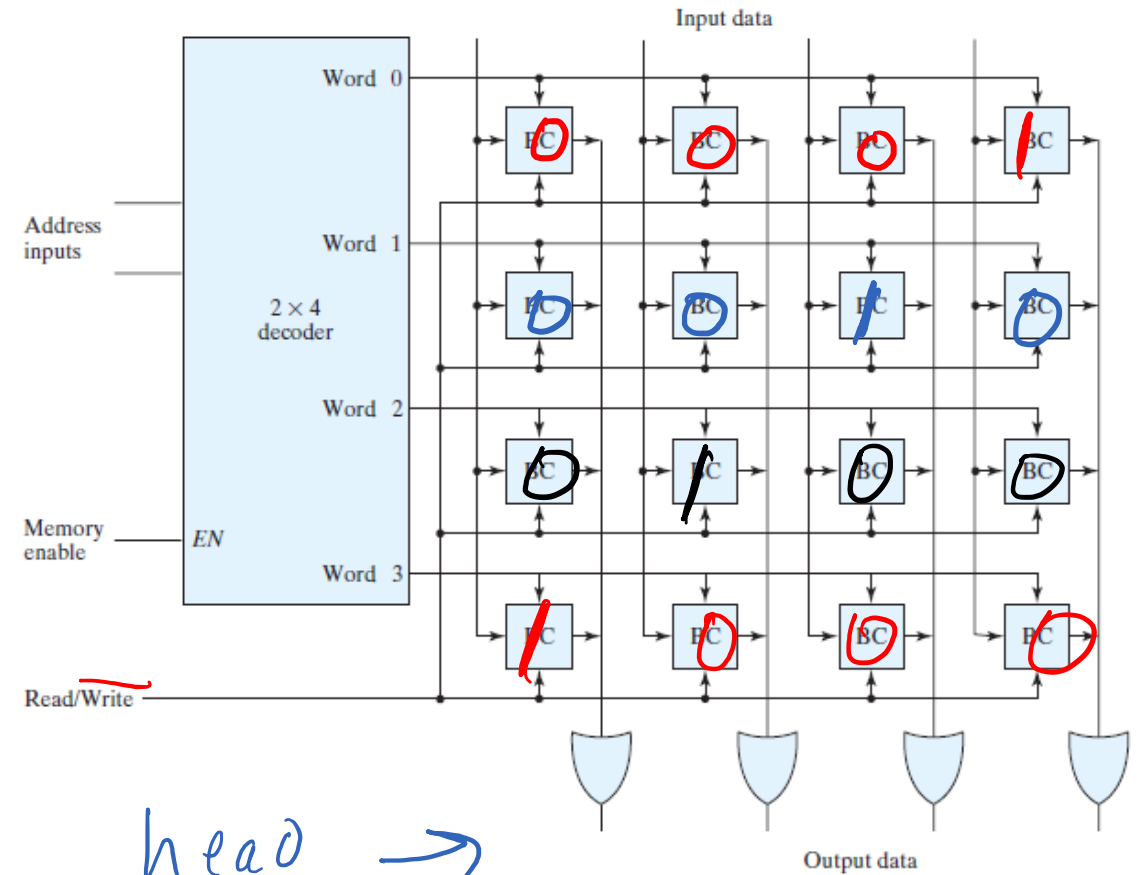

$head \rightarrow$
100


push/pop with RAMs
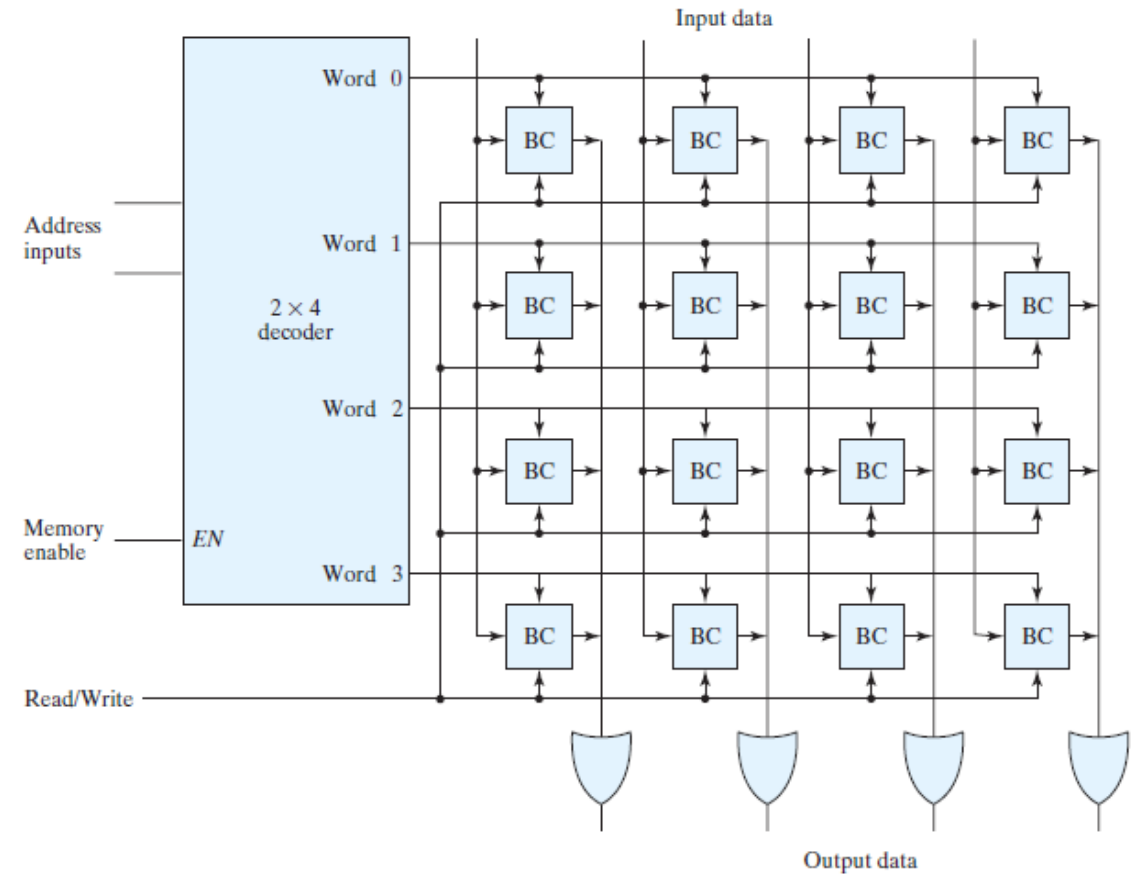
```
push( 4'b 0001)
push( 4'b 0010)
push( 4'b 0100)
    pop()
    pop()
push( 4'b 1000)
push( 4'b 0011)
    pop()
    pop()
push( 4'b 0110)
    pop()
```



push/pop with RAMs

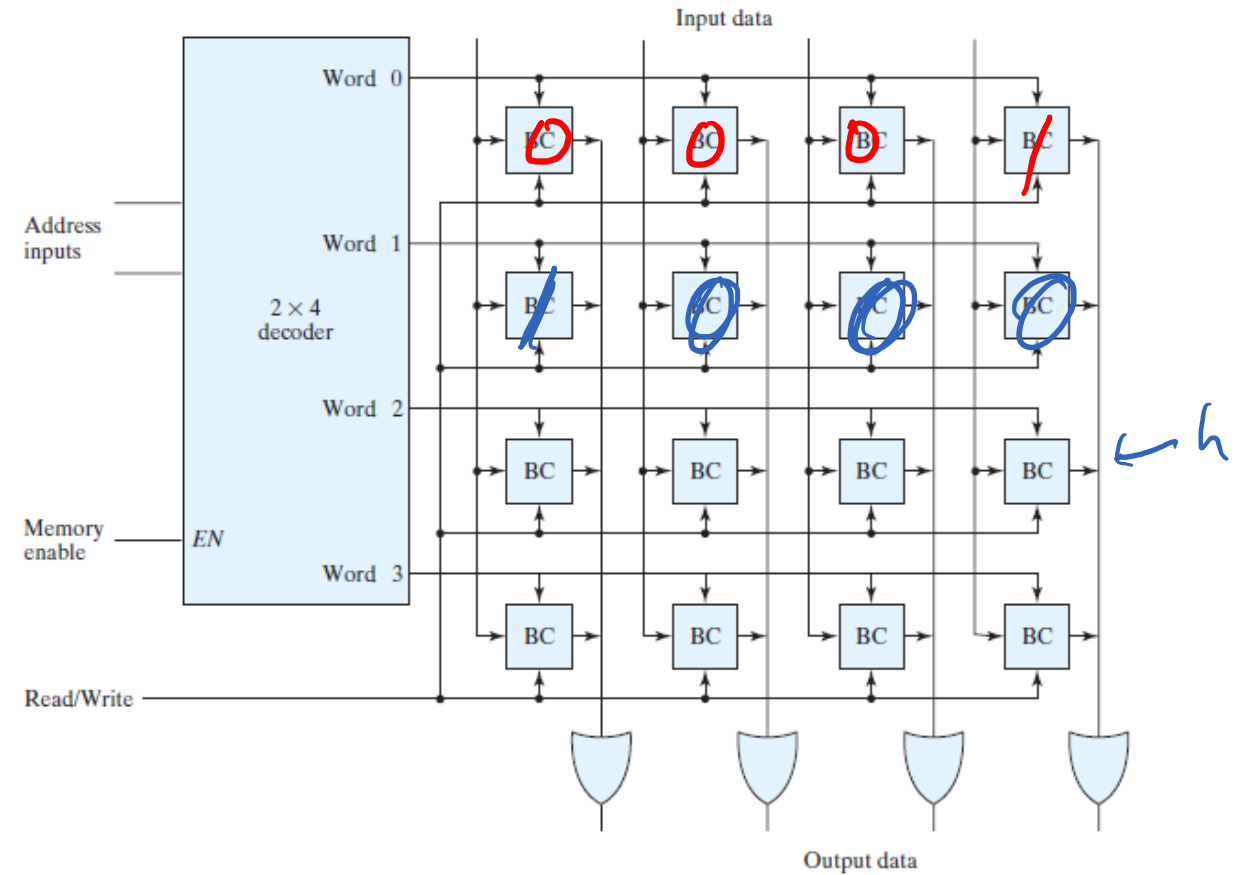push(4'b 0001) ✓
push(4'b 0010) ✓
push(4'b 0100) ✓
pop() ⇒ 0100
pop() ⇒ 0010
push(4'b 1000) ✓
push(4'b 0011)
pop()
pop()
push(4'b 0110)
pop()



Stack Logic

- Inputs: push_req, [3:0] push_data
- Inputs To RAM: addr, set, [3:0] set_data

```
module RAM (  
    input      clk,  
    input [1:0] addr,  
    input      set,  
    input [3:0] set_data,  
    output [3:0] read_data  
)
```

Push State Machine

assign pop_data =

always_ff (@ posedge clk) begin
 if (rst) ...
 else begin

end
end


```
module RAM (  
    input      clk,  
    input [1:0] addr,  
    input      set,  
    input [3:0] set_data,  
    output [3:0] read_data  
)
```

Pop Logic

- Inputs: pop_req
- Outputs: [3:0] pop_data
- Inputs To RAM: addr, set
- From RAM: [3:0] read_data

```
module RAM (  
    input      clk,  
    input [1:0] addr,  
    input      set,  
    input [3:0] set_data,  
    output [3:0] read_data  
)
```

Stack State Machine

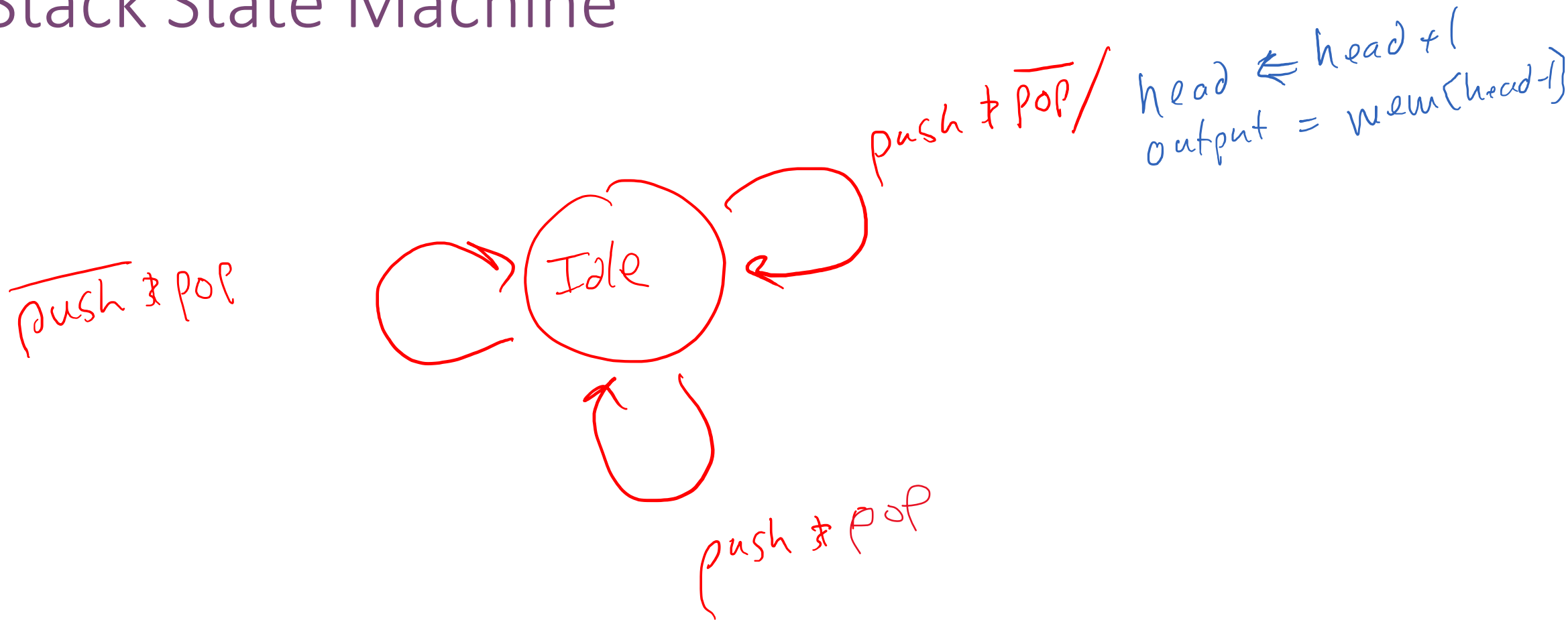

Error cases not shown.

Challenge: Push+Pop Together

- This needs to be a “replace” in the RAM.

0	0	0	1
0	0	1	0

pop() + push(0100)

⇒

0	0	0	1
0	1	0	0

Challenge: Push+Pop Error Logic

- What happens if the RAM is empty? Or Full?

0	0	0	1
0	0	1	0
0	1	0	0
1	0	0	0

push \rightarrow fail

pop \rightarrow succeed

push + pop \rightarrow Succeed

push \rightarrow succeed

pop \rightarrow fail

push + pop \rightarrow

push-err = 0
pop-err = 1

Next Time

- FPGA Structures