

# Encoders / Decoders

Andrew Lukefahr

# Last Time


- Boolean Logic / Schematic / Truth Tables

- Verilog
  - Submodules

- Verilog
  - Testbenches
 
## Review: Logic

- Draw this circuit:  $co = ((a \& b) \mid (a \wedge b)) \& ci;$



# Review: Submodules

- `modules` are basic building block in Verilog
- Group modules together to form more complex structure

# Review: Submodules

```

module FullAddr (
    input a,b,ci,
    output s, co
);

    s = a ^ b ^ ci;
    co = a & b | ( a ^ b) & ci;

endmodule

```

```

module TwoBitAddr(
    input a0, a1, b0, b1, ci,
    output s0, s1, co
);

```

//code me!

wire R; // carry

FullAddr add0 ( .a(a0), .b(b0), .ci(ci),  
 .s(s0), .co(R) );

FullAddr add1 ( .a(a1), .b(b1), .ci(R),  
 .s(s1), .co(co) );  
endmodule

$$\begin{array}{r}
 \begin{array}{cc}
 a_1 & a_0 \\
 + & b_1 & b_0 \\
 + & & c_{in} \\
 \hline
 C_{out} & s_1 & s_0
 \end{array}
 \qquad
 \begin{array}{r}
 1 \\
 + 1 \\
 + 1 \\
 \hline
 0
 \end{array}
 \end{array}$$

# Review: Submodules

```
module FullAddr (  
    input a,b,ci,  
    output s, co  
);  
  
    s = a ^ b ^ ci;  
    co = a & b | ( a ^ b) & ci;  
  
endmodule
```

```
module TwoBitAddr(  
    input a0, a1, b0, b1, ci,  
    output s0, s1, co  
);
```

```
    wire r; //caRry ?
```

```
    FullAddr fa0 (.a(a0), .b(b0), .ci(ci), .s(s0), .co(r) );  
    FullAddr fa1 (.a(a1), .b(b1), .ci(r) , .s(s1), .co(co) );
```


```
endmodule
```

# Review: Submodules

Two Bit Addr

Full Addr
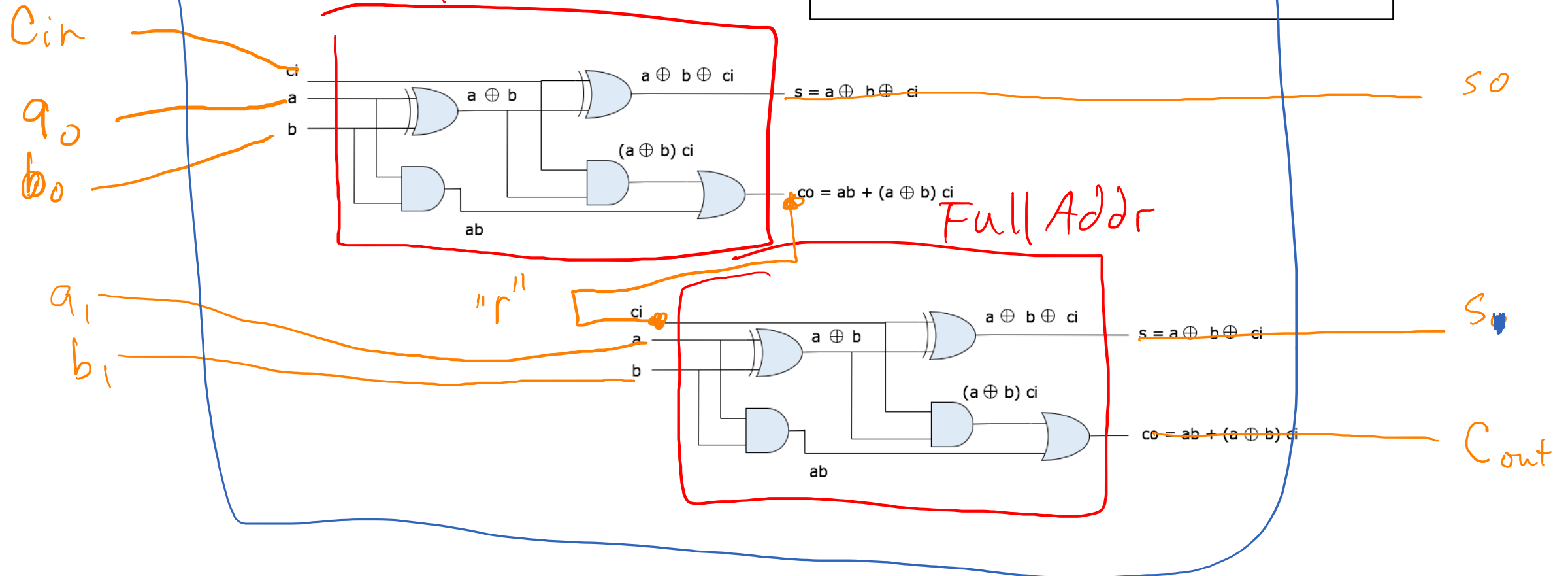
```
module TwoBitAddr(  
    input a0, a1, b0, b1, ci,  
    output s0, s1, co  
);  
    wire r; //carry ?  
    FullAddr fa0 (a0, b0, ci, s0, r);  
    FullAddr fa1 (a1, b1, r, s1, co);  
endmodule
```



# Verilog Testbenches

- Synthesize-able vs. Simulate-able
- Synthesis: Real circuit on real hardware
  - Only “synthesizable” Verilog allowed
- Simulation: Test our design with software simulations
  - “Non-synthesizable” Verilog allowed (System Verilog)
  - Often simulation-only commands start with a dollar sign (\$)




# TestBenches

- Another Verilog module to drive and monitor our “Synthesizable” module
 
# TestBenches

- Another Verilog module to drive and monitor our “Synthesizable” module



## “initial” statement

0  
for (int i = 0; i < 10; ++i) {  
}

- Simulation only!
- Starts at simulation time 0, executes exactly once, and then does nothing.
- Group multiple statements with `begin` and `end`.
  - `begin/end` are the ‘{’ and ‘}’ of Verilog.

```
initial  
begin  
    a = 1;  
    b = 0;  
end
```

timescale 1ns / 1ps ←

## Delayed execution

# 10.0005 ← appear  
# 10.0001 ← the same

- If a delay #<delay> is seen before a statement, the statement is executed <delay> time units after the previous statement.

```
initial  
begin  
  (0 ns) #10 a = 1; // executes at 10 time units  
          #25 b = 0; // executes at 35 time units  
end
```

- We can use this to test different inputs over time on our circuits

# \$monitor

- `$monitor` prints a new line every time it's output changes
- C printf-like format

- `$monitor($time,`  
    `"K= %b, P= %b, S= %b, A= %b\n",`  
    `K,P,S,A) ;`

*%b = binary*

*%h = hex*

*%d = decimal*

## Example Output:

```
0   K= 0, P= 0, S= 0, A= 0
5   K= 1, P= 0, S= 0, A= 0
10  K= 1, P= 1, S= 0, A= 1
```

# Testing a Full Adder

```
`timescale 1ns / 1ps
```

```
/// initialize FullAddr
```

```
initial  
begin
```

```
//$monitor optional
```

```
✓ #1 //wait 1ns
```

```
✓ a = 1; b = 0; ci = 0;
```

```
#0.001 // 1ps
```

```
assert( s == 1) else $fatal(1, "s");
```

```
assert( co == 0) else $fatal(1, "co");
```

```
#1 //wait 1ns
```

```
a = 1; b = 1; ci = 0;
```

```
#0.001 // 1ps
```

```
assert( s == 0) else $fatal(1, "s");
```

```
assert( co == 1) else $fatal(1, "co");
```

```
$finish;
```

```
end
```

```
module FullAddr (  
    input a,b,ci,  
    output s, co  
);  
  
    s = a ^ b ^ ci;  
    co = a & b | ( a ^ b) & ci;  
  
endmodule
```

Handwritten addition:  
1  
+ 0  
+ 0  
---  
0 1

Handwritten addition:  
1  
+ 1  
+ 0  
---  
1 0

Handwritten notes:  
return  
print

# Testing a Full Adder

```
`timescale 1ns / 1ps

/// initialize FullAddr

initial
begin

    //$monitor optional

    #1 //wait 1ns
    a = 1; b = 0; ci = 0;
    #0.001 // 1ps
    assert( s == 1) else $fatal(1, "s");
    assert( co == 0) else $fatal(1, "co");

    #1 //wait 1ns
    a = 1; b = 1; ci = 0;
    #0.001 // 1ps
    assert( s == 0) else $fatal(1, "s");
    assert( co == 1) else $fatal(1, "co");

    $finish;
end
```

```
module FullAddr (
    input a,b,ci,
    output s, co
);

    s = a ^ b ^ ci;
    co = a & b | ( a ^ b) & ci;

endmodule
```

# Tasks in Verilog

- A task in a Verilog simulation behaves similarly to a C function call.

↓

```
task taskName;  
    input localVariable1;  
    input localVariable2;  
  
    #1 //1 ns delay  
    globalVariable1 = localVariable1;  
    #1 // 1ns delay  
    assert( globalVariable2 == localVariable2)  
        else $fatal(1, "failed!");  
  
endtask
```

inputs

what to do

what to check



# Tasks in Testing

```
module FullAddr (
    input a,b,ci,
    output s, co
);
    s = a ^ b ^ ci;
    co = a & b | ( a ^ b ) & ci;
endmodule
```

```
`timescale 1ns / 1ps
```

```
// declare a,b,ci, s, & co
```

```
FullAddr fa0 (.a(a), .b(b), .ci(ci), .s(s), .co(co));
```

✓ task TestOne; //set module signals to T(est) values  
 input aT, bT, ciT, sT, coT;

```
#1
```

→ a = aT; b = bT; ci = ciT;

```
#1
```

```
assert( s == sT ) else $fatal(1, "s failed");
```

```
assert( co == coT ) else $fatal(1, "co failed");
```

```
endtask
```

```
initial
```

```
begin
```

```
TestOne(.aT(1), .bT(0), .ciT(1), .sT(1), .coT(0)); ✓
```

```
TestOne(.aT(1), .bT(1), .ciT(0), .sT(0), .coT(1));
```

```
$finish;
```

```
end
```

a=1 b=0 cin=1 s=1 co=0  
 a=1 b=1 cin=0 s=0 ~~co=1~~

```

      1
    + 0
    + 1
  -----
    10
  
```

# Tasks in Testing

```

/// module definition
// declare a0,a1,b0,b1,ci, s0,s1,& co

TwoBitAdder tba0 (a0,a1,b0,b1,ci,s0,s1,co);

task TestTwo;

```

```

module TwoBitAddr(
    input a0, a1, b0, b1, ci,
    output s0, s1, co
);
    wire r;
    FullAddr fa0 (a0,b0,ci,s0,r);
    FullAddr fa1 (a1,b1,r,s1,co);
endmodule

```

*input  $a_1^T, a_0^T, b_1^T, b_0^T, cin^T, cout^T, s_1^T, s_0^T$ ;*

*#1*

*$a_1 = a_1^T; a_0 = a_0^T; b_1 = b_1^T; b_0 = b_0^T; cin = cin^T$ ;*

*#1*

*assert(  $co == co^T$  ) else \$fatal(1, "cout failed\n");*  
*assert( ( $s_0 == s_0^T$ ) && ( $s_1 == s_1^T$ ) ) else \$fatal(1, "sum failed\n");*

```

endtask

initial begin
    a1 a0 b1 b0 ci cout s1 s0
    TestTwo( 0,0,0,0,0, 0,0,0); // a=00 + b=00 + ci=0 => s=00 co=0
    TestTwo( 0,0,0,0,1, 0,0,1); // a=00 + b=00 + ci=1 => s=01 co=0
    //more tests + $finish
end

```

# Tasks in Testing

```
/// module definition
// declare a0,a1,b0,b1,ci, s0,s1,& co

TwoBitAdder tba0 (a0,a1,b0,b1,ci,s0,s1,co);

task TestTwo;
    input a1T, a0T, b1T, b0T, ciT;
    input coT, s0T, s1T;

    #1
    a0 = a0T; a1 = a1T; b0 = b0T; b1=b1T, ci = ciT;
    #1
    assert( (s0 == s0T) && (s1 == s1T)) else $fatal(1, "s failed");
    assert( co == coT) else $fatal(1, "co failed");
endtask

initial begin
    TestTwo( 0,0,0,0,0, 0,0,0); // 00 + 00 + 0 = 000
    TestTwo( 0,0,0,0,1, 0,0,1); // 00 + 00 + 1 = 001
    //more tests + $finish
end
```

```
module TwoBitAddr(
    input a0, a1, b0, b1, ci,
    output s0, s1, co
);
    wire r;
    FullAddr fa0 (a0,b0,ci,s0,r);
    FullAddr fa1 (a1,b1,r,s1,co);
endmodule
```


# Tasks in Testing

- `tasks` are very useful for quickly testing Verilog code
- Call a `task` to quickly change + check things
- A `task` can call another `task`
- There is a `function` in Verilog.
- We don't use it.


# Topic Change: Encoders / Decoders

# Encoding/Decoding


- Using 1 switch at a time

 

# Encoding

 


# Encoding

 


 
# Encoders

- Have: 4 input wires
- Want: Encoded data to 2 output wires



<u>Inputs</u>				<u>Outputs</u>		
<u>a</u>	<u>b</u>	<u>c</u>	<u>d</u>	<u>e<sub>1</sub></u>	<u>e<sub>0</sub></u>	<u>dec</u>
1	0	0	0	0	0	0
0	1	0	0	0	1	1
0	0	1	0	1	0	2
0	0	0	1	1	1	3

$$e_1 = c \vee d;$$


$$e_0 = b \vee d;$$

# Encoders

- Have: 4 input wires
- Want: Encoded data to 2 output wires

<u>inputs</u>				<u>outputs</u>	
<u>a</u>	<u>b</u>	<u>c</u>	<u>d</u>	<u>e<sub>1</sub></u>	<u>e<sub>0</sub></u>
<u>0</u>	<u>0</u>	<u>0</u>	<u>1</u>	<u>0</u>	<u>0</u>
<u>0</u>	<u>0</u>	<u>1</u>	<u>0</u>	<u>0</u>	<u>1</u>
<u>0</u>	<u>1</u>	<u>0</u>	<u>0</u>	<u>1</u>	<u>0</u>
<u>1</u>	<u>0</u>	<u>0</u>	<u>0</u>	<u>1</u>	<u>1</u>

$$e_1 = a \vee b;$$
$$e_0 = a \vee c;$$

 

# Encoder in Verilog

$$e_1 = c / d;$$
$$e_0 = b / d;$$

```
module encoder (  
    input a,b,c,d,  
    output e1, e0  
);
```

```
    assign e1 = c / d;
```

```
    assign e0 = b / d;
```

```
endmodule
```

# Encoder in Verilog

```
module encoder (  
    input a,b,c,d,  
    output e1, e0  
);  
  
    assign e0 = c | d;  
    assign e1 = b | d;  
  
endmodule
```

# Encoder w/Valid

- How would you add a valid output signal?

```
module encoder_valid (
    input a,b,c,d,
    output e1, e0,
    output valid
);
```

//code me!

$encoder\ enc0(.a(a), .b(b), .c(c), .d(d), .e1(e1), .e0(e0))$

$assign\ valid = a | b | c | d;$

endmodule

<u>a</u>	<u>b</u>	<u>c</u>	<u>d</u>	<u>Valid</u>
1	0	0	0	1
0	1	0	0	1
0	0	1	0	1
0	0	0	1	1
0	0	0	0	0

```
module encoder (
    input a,b,c,d,
    output e1, e0
);

    assign e0 = a | c; c | d
    assign e1 = b | a; b | d

endmodule
```

# Encoder w/Valid

- How would you add a  
valid output signal?



```
module encoder_valid (  
    input a,b,c,d,  
    output e1, e0,  
    output valid  
);
```

```
    encoder e0 (.a(a),.b(b),.c(c), .d(d), .e1(e1), .e0(e0) );  
    assign valid = a | b | c | d; // e0|e1|d
```

```
endmodule
```

```
module encoder (  
    input a,b,c,d,  
    output e1, e0  
);  
  
    assign e0 = a | c;  
    assign e1 = b | a;  
  
endmodule
```


# Decoding

  

# Decoders

- Have: 2-bit encoded data
- Want: 4 wires

Decode

 

$e_1$	$e_0$
0	0
0	1
1	0
1	1

$w$	$x$	$y$	$z$
0	0	0	1
0	0	1	0
0	1	0	0
1	0	0	0

$$Z = \neg e_1 \wedge \neg e_0$$

$$= (\neg(e_1 \vee e_0))$$

$$Y = \neg e_1 \wedge e_0$$

$$X = e_1 \wedge \neg e_0$$

$$W = e_1 \wedge e_0$$



# Decoders

- Have: 2-bit encoded data
- Want: 4 wires

# Decoders

- Have: 2-bit encoded data
- Want: 4 wires


$e_1$	$e_0$	$w$	$x$	$y$	$z$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

$$z = \bar{e}_1 \bar{e}_0$$

$$y = \bar{e}_1 e_0$$

$$x = e_1 \bar{e}_0$$

$$w = e_1 e_0$$

 

# Decoder Verilog

```
module decoder (  
    input e1, e0,  
    output w,x,y,z  
);  
  
    assign w = ~e1 & ~e0;  
    assign x = ~e1 & e0;  
    assign y = e1 & ~e0;  
    assign z = e1 & e0;  
  
endmodule
```


# Encoders / Decoders

- Encoder:
  - Takes  $2^n$  single-bit signals, emits an  $n$ -bit encoded signal
- Decoder:
  - Takes an  $n$ -bit encoded signal, emits  $2^n$  single-bit signals

# Bigger Encoders

- What would a 8-to-3 *encoder* look like?
- Write the Truth Table & Boolean Equation

# 8-3 Encoder

 

hierarchically

$d_0$	$d_1$	$d_2$	$d_3$	$d_4$	$d_5$	$d_6$	$d_7$	$e_2$	$e_1$	$e_0$
							1	0	0	0
						1		0	0	1
					1			0	1	0
				1				0	1	1
			1					1	0	0
		1						1	0	1
	1							1	1	0
1								1	1	1

$$e_2 = d_0 | d_1 | d_2 | d_3 ;$$

$$e_1 = d_4 | d_5 | d_6 | d_7 ;$$

$$e_0 = d_0 | d_2 | d_4 | d_6$$

# Next Time

- Multiplexer
- Demultiplexer
- Adders
- ALUs