

Tri-State Logic

FPGAs

Andrew Lukefahr

Always specify
defaults for
always_comb!

BLOCKING (=) FOR
`always_comb`

NON-BLOCKING (<=) for
`always_ff`

UART RX/TX LEDs on Basys3

- A word of **caution**:
- The Basys3's **RX + TX LEDs are backwards** from what you expect.
- They are the USB adaptor chip's RX+TX, not the FPGAs.

Stack with RAMs

push(4'b 0001)

$head = 00$, $input = 0001$, $Rd\overline{Wr} = 0$, $memEn = 1$

$head \leftarrow head + 1$

push(4'b 0010)


$head =$

$head = 01$, $input = 0010$, $Rd\overline{Wr} = 0$, $memEn = 1$

$head \leftarrow head + 1$

push(4'b 0100)


push(4'b 1000)

 

$head \rightarrow 100$

push/pop with RAMs

 push(4'b 0001) ✓
push(4'b 0010) ✓
push(4'b 0100) ✓
pop() ⇒ 0100
pop() ⇒ 0010
push(4'b 1000) ✓
push(4'b 0011)
pop()
pop()
push(4'b 0110)
pop()




Busses

- Boolean Logic is bi-state:
 - 1: logical true
 - 0: logical false
 - X: The simulation tools don't know if it's 1 or 0
- So you can't do things like this:


Busses

 - Boolean Logic is bi-state:
 - 1: logical true
 - 0: logical false
- X: The simulation tools don't know if it's 1 or 0
- So you can't do things like this:



 Question: Then how does I2C work?

- I2C: **Inter - Integrated Circuit Communication**



- Clearly multiple “drivers” for 1 wire?


Answer: A “Tri-State” Bus

- “Tri-State” signals:
 - 1: this is logical true
 - 0: this is logical false
 - X: The simulation tools don’t know if it’s 1 or 0
 - Z: this is “high impedance”
- Z: High Impedance
 - Stop driving a logical value
 - Pretend I’m not connected

Tri-State logic


```
wire enable;  
wire enabled_output = 'h0;  
wire tri;  
assign tri = (enable ? enabled_output : 'hZ);
```

Tri-State logic

 


Tri-State Bus

Tri-State Bus

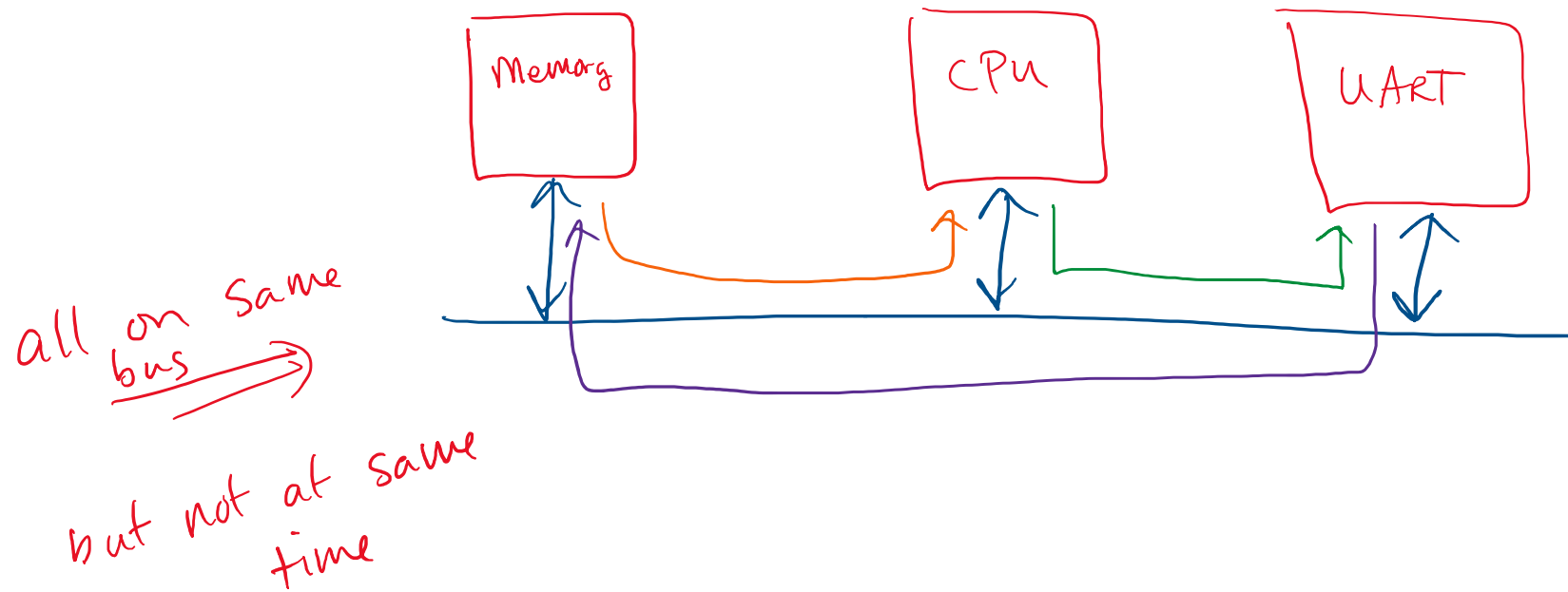



Problems with Tri-State Logic

- What if two signals “drive” at once?

 


Solution: Don't Do That!

Review: RAM

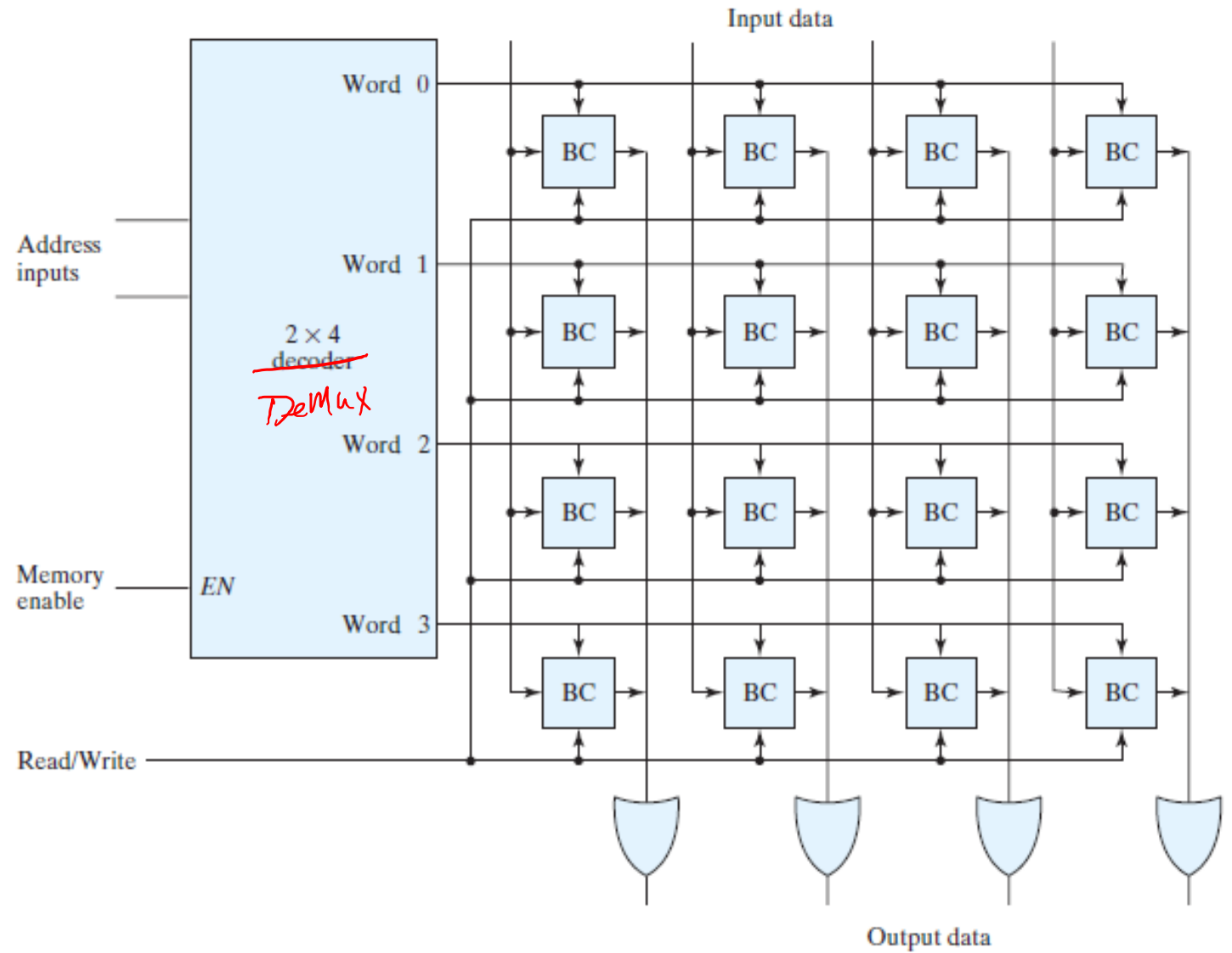 

Look-Up Table (LUT)

 


- DON'T compute a Boolean equation
- DO pre-compute all solutions in a table
- DO look up the Boolean result in the table

- Examples:

$$s = a \wedge b;$$

$$c = a \& b;$$

 


<u>a</u>	<u>b</u>	<u>Sum</u>	<u>carry</u>
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

RAM to LUT


- Can I use a RAM to build a Half-Adder LUT?

$$s = a \oplus b;$$




$$c = a \& b;$$

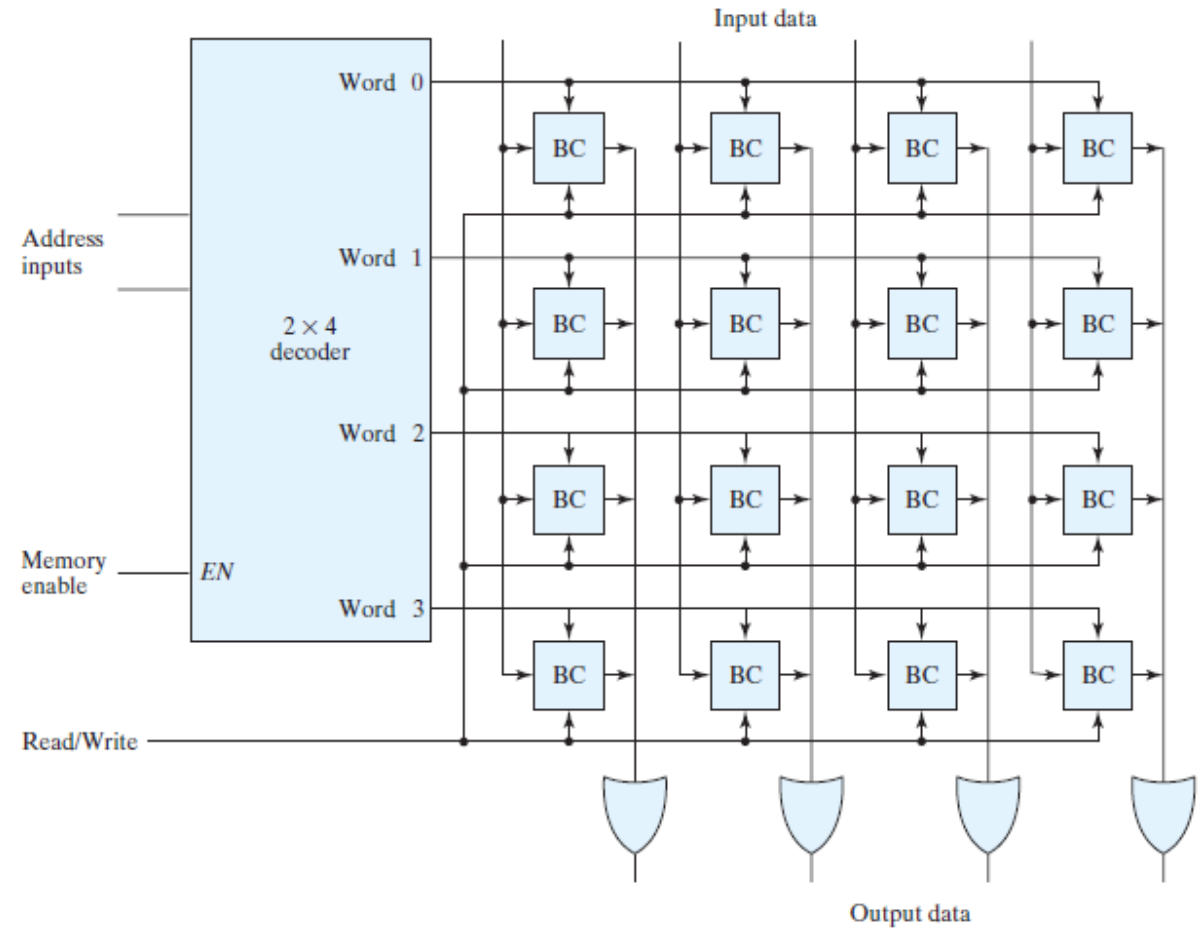




Full-Adder LUT

 

Input			Output	
A	B	Cin	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

   

N-input, M-output LUT

   


LUT size

1 output

~~3 in~~


- Why not a 1000-input, 100-output LUT?

 

- 3 inputs $\Rightarrow 2^3$ rows = 8 rows $\leftarrow 3_{in}, 1_{out}$
- 4 inputs $\Rightarrow 2^4$ rows = 16 rows $\leftarrow 4_{in}, 1_{out}$
- 5 inputs $\Rightarrow 2^5$ rows = 32 rows
- ...
- 64 inputs $\Rightarrow 2^{64}$ rows = 1.85×10^{19} rows

- LUT input size does not scale well.

2 output

 

$$8 \cdot 2 = 16$$


$$16 \cdot 2 = 32$$

$$32 \cdot 2 = 64$$

...

Divide and Conquer with LUTs


- 3-Bit Full Adder

 

a n n

Sequential Logic

 - Problem: How do we handle sequential logic?
 - LUTs cannot contain state
- Solution: Add a Flip-Flop



Basic Logic Element (BLE)

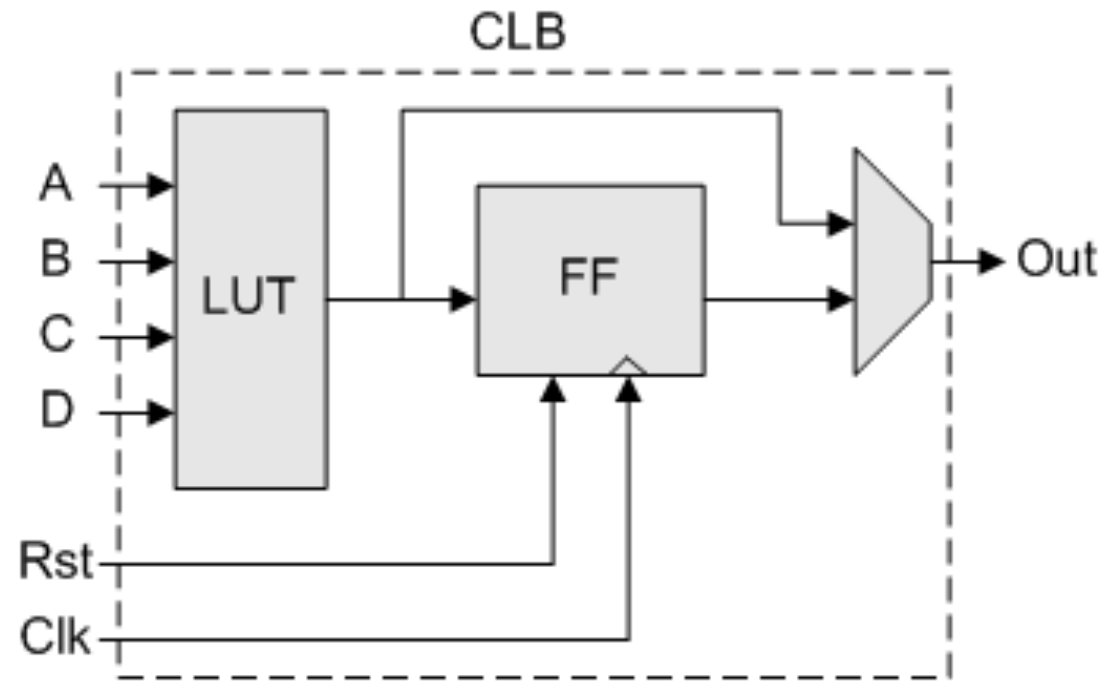


Fig.4 Example of Configurable Logic Cell.

Basic Logic Element (BLE)

- What if I only want to store a value?

A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1


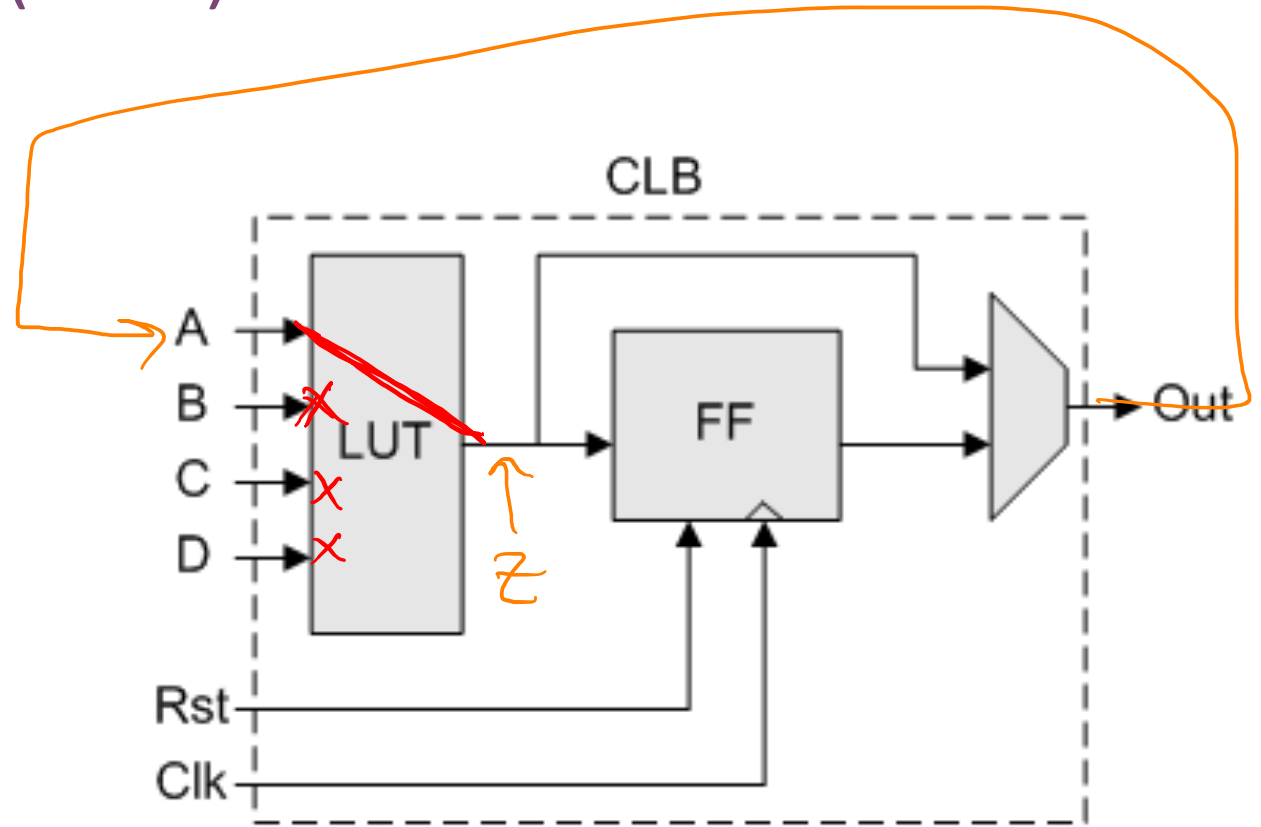



Fig.4 Example of Configurable Logic Cell.

6 input, 4 output CLB


Improved BLE

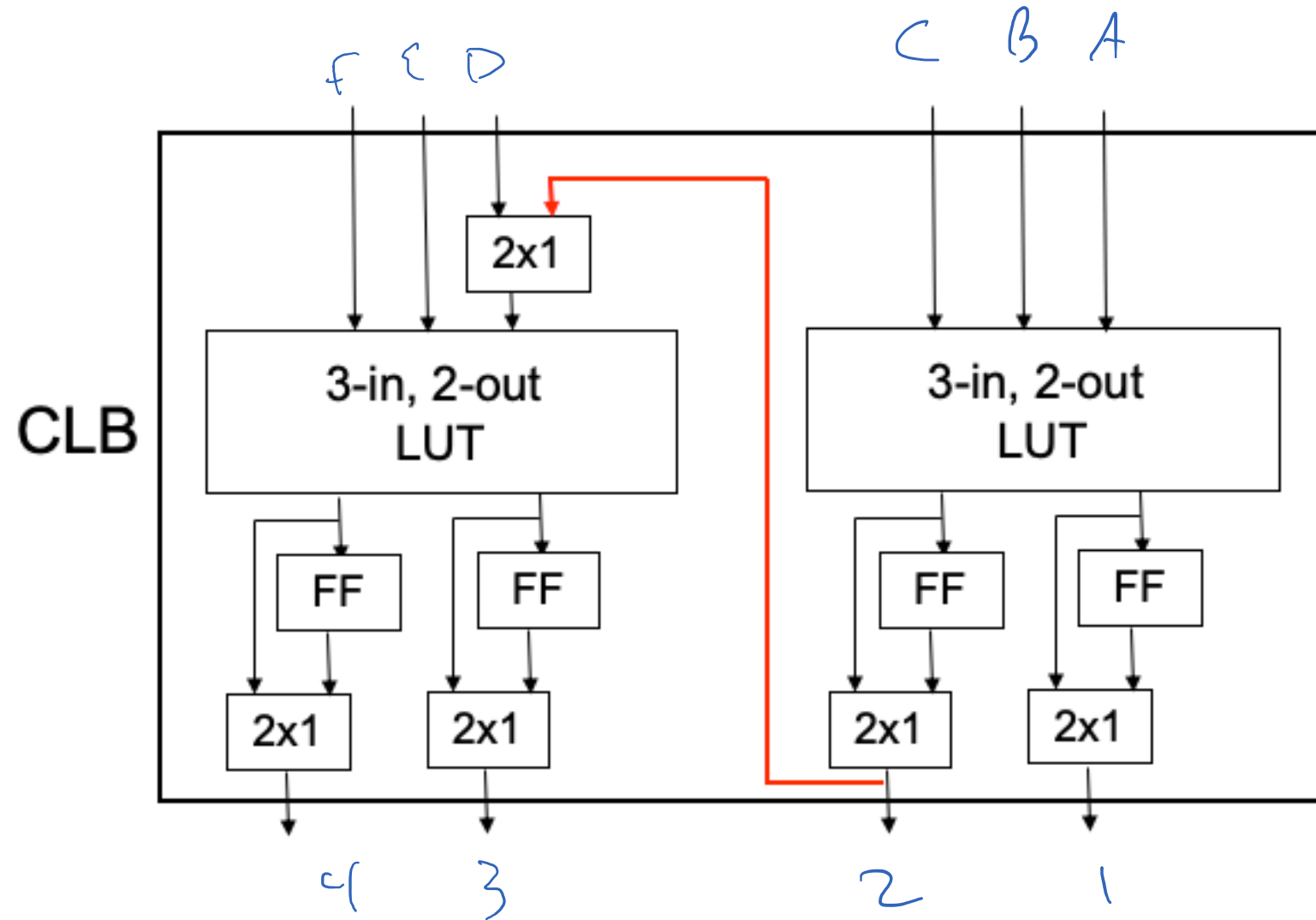


2-Bit Ripple-Carry w/ BLE

 

Realistic BLE: Xilinx

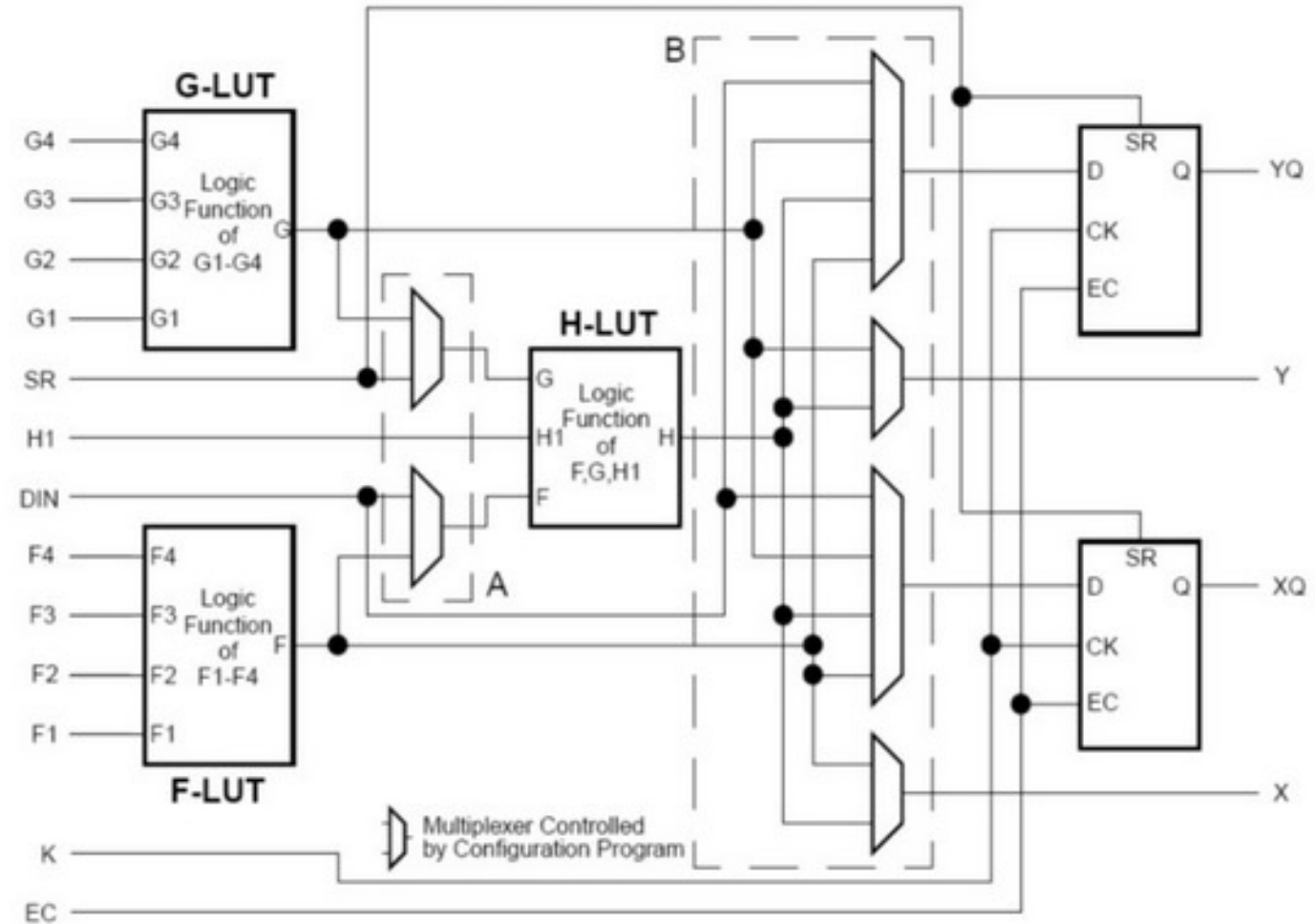


CLBs: Configurable Logic Block

 


Connecting CLBs

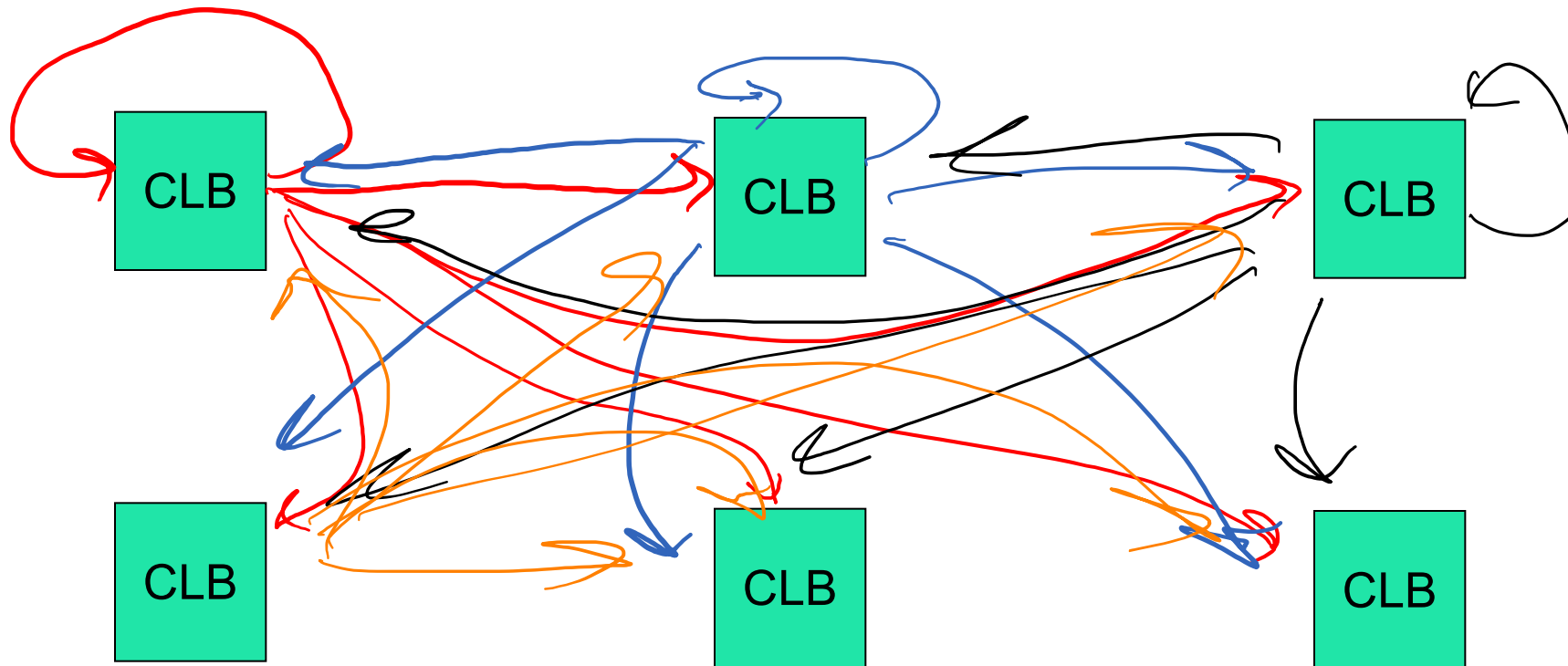- Q: How do CLBs talk to each other?
- A: Put wires everywhere!




Connecting CLBs

 - Q: How do CLBs talk to each other?
- A: Put wires everywhere (ok, almost everywhere)!




How to connect CLBs to wires?

 - “Connection box”
 - Device that allows inputs and outputs of CLB to connect to different wires




Connection Box Flexibility

 


Dots represent **possible connections*

How to connect wires to each other?

 


Switch Box

 
- Connects horizontal and vertical routing channels




Switch Box Connections

 

 - Programmable connections between inputs and outputs





Wilton

 


**Not all possible connections shown*

Switch Box Connections

  

FPGA “Fabric”


- 2D array of CLBs + interconnects

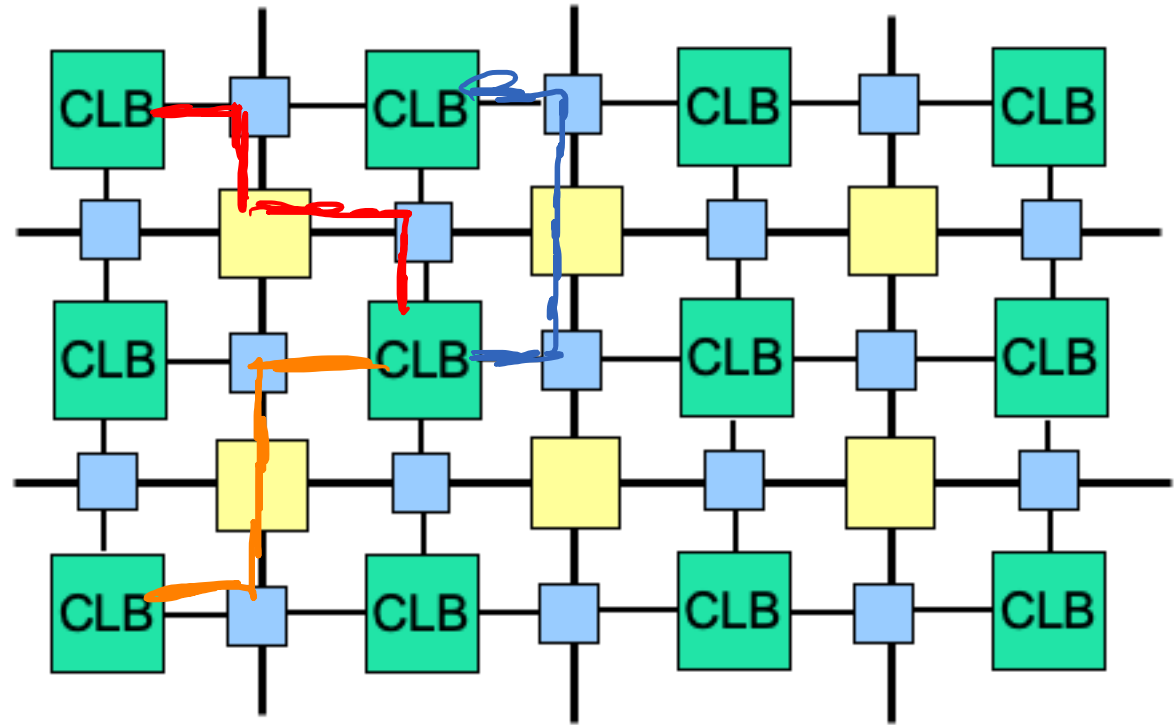

- Am I missing anything?


Block RAM

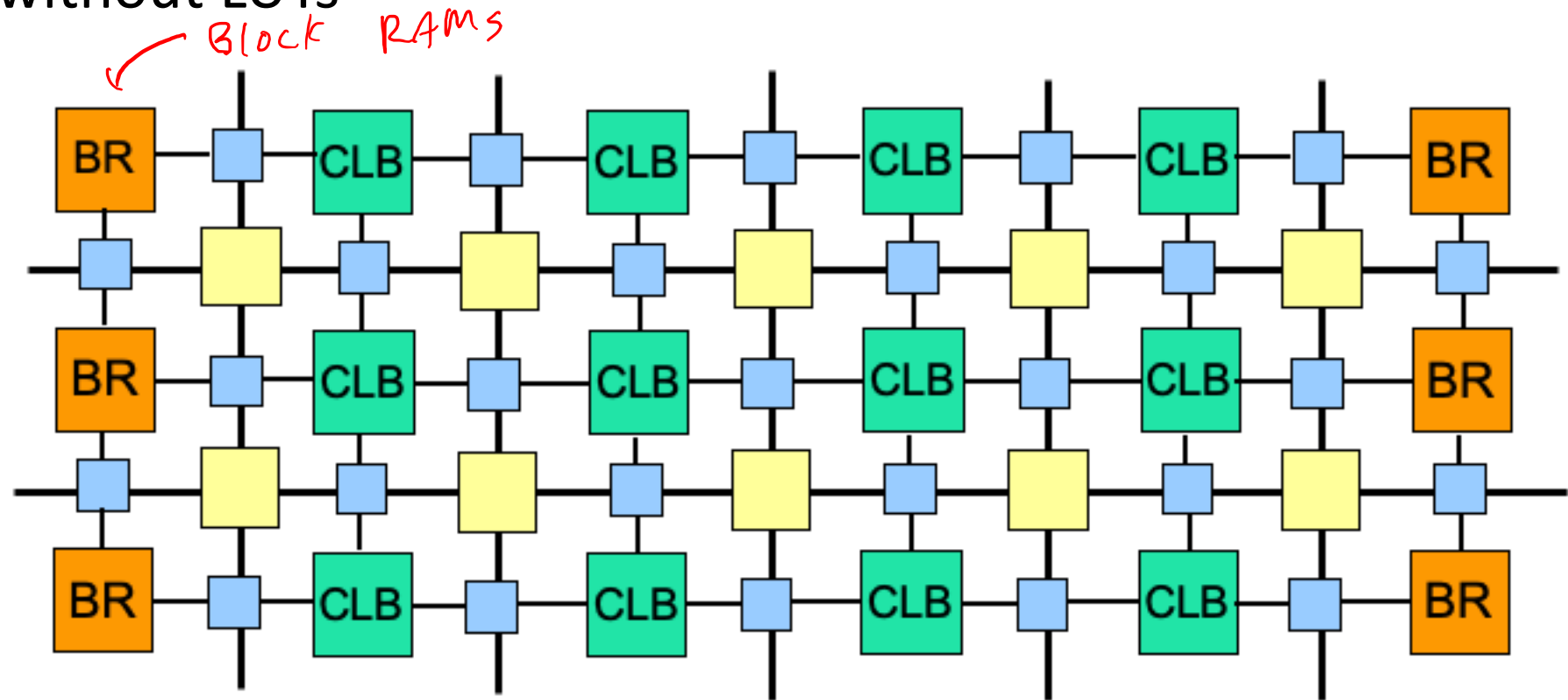- Special blocks of just RAM
- Big CLBs without LUTs



DSPs → Digital Signal Processor → dedicated math units

multiply

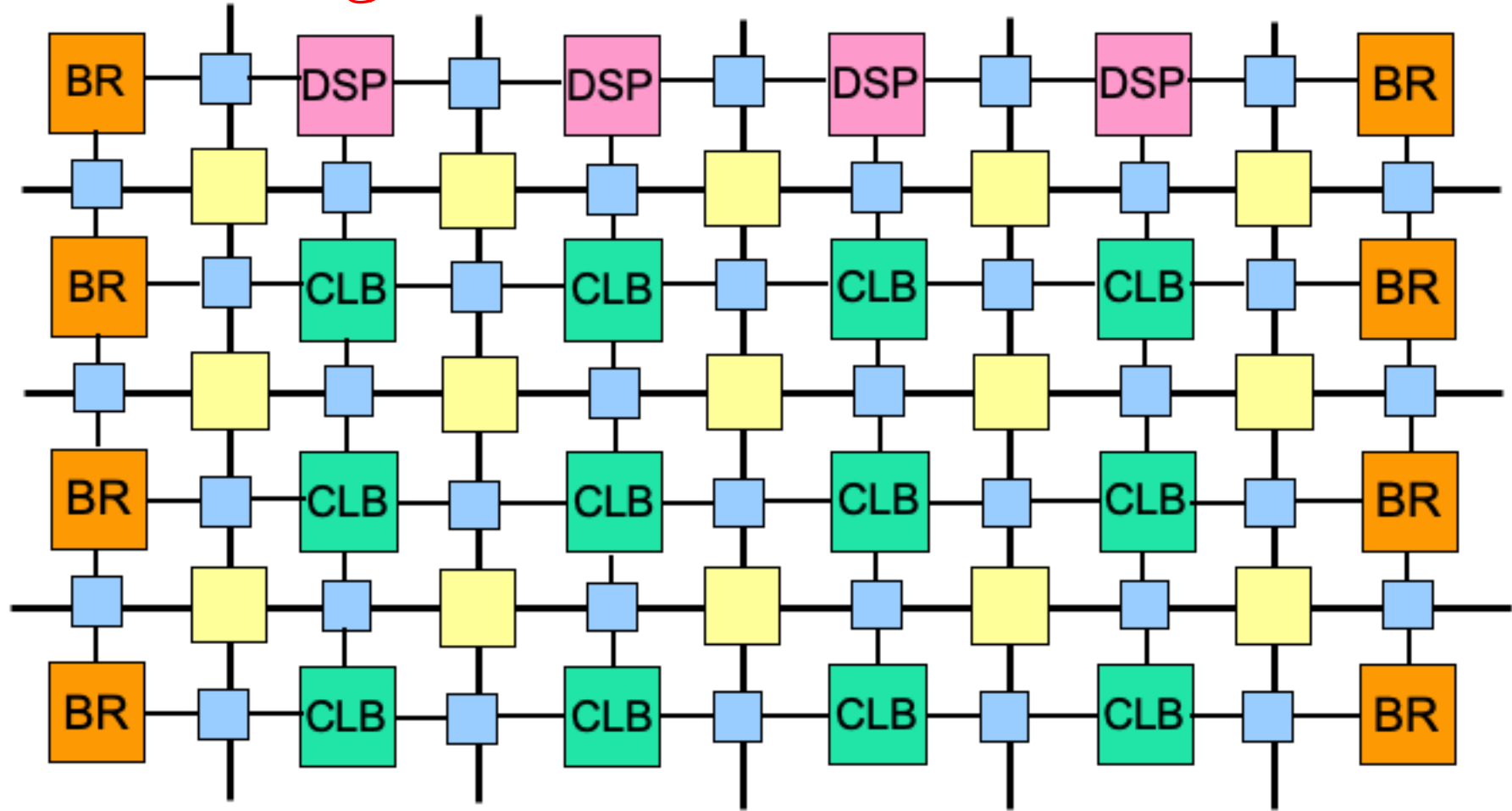

Input/Output (IO)

