

# Timing

Andrew Lukefahr  
Indiana University - Bloomington

# Calculator.py

- Lets you interact with the FPGA via the keyboard
  - Translates ASCII <--> Binary for you

```
$ python3 calculator.py -s /dev/ttyUSB1
```

```
$ python3 calculator.py --help
```


```
python3 (not “python”)
```

# Overview

- Circuit Timing
- ~~Binary Multiplication~~

Synchronizers (?)


# Review: The Compute Stack

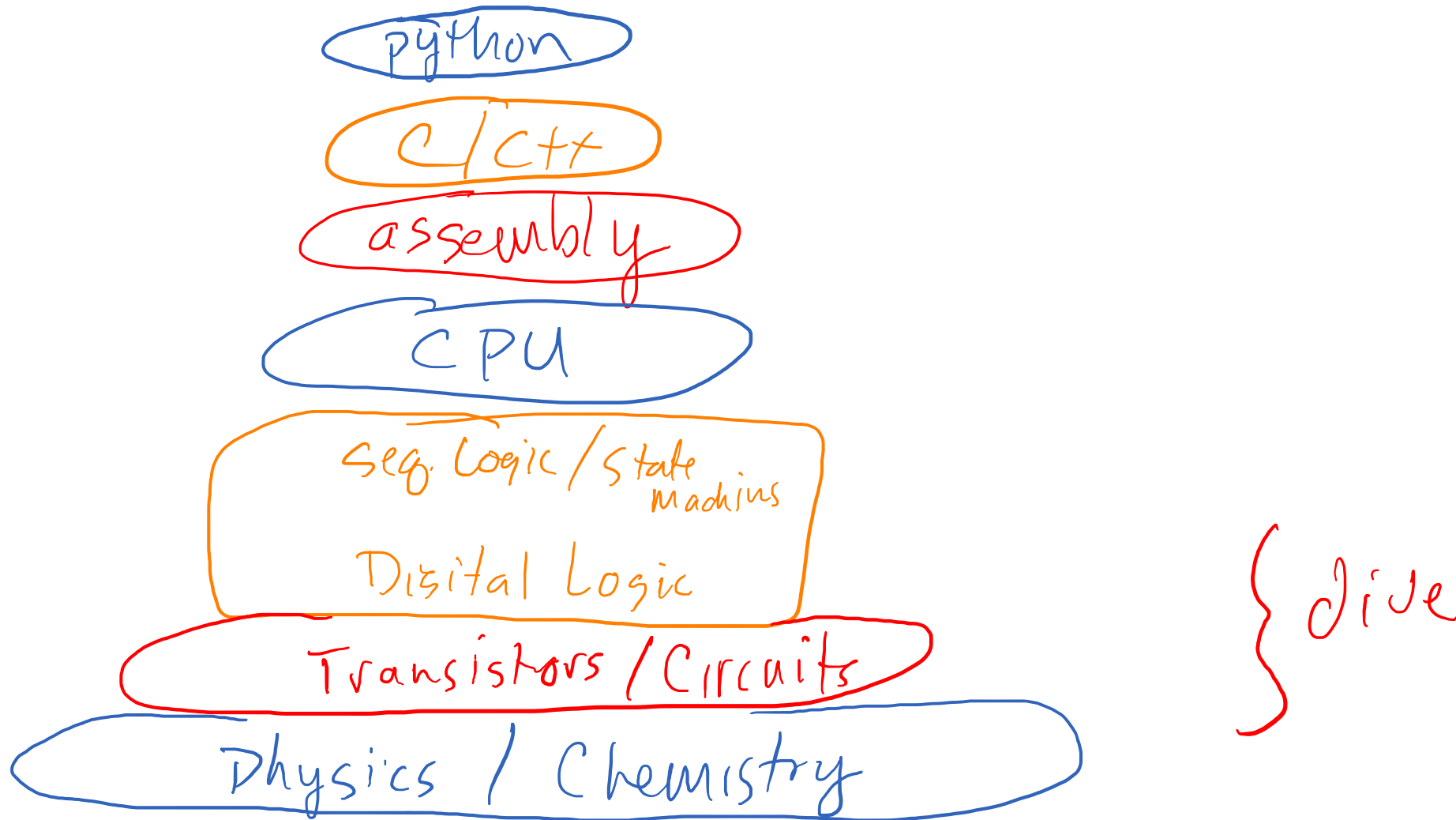


# Review: All logic is NAND

- It's not magic, it's an electronic circuit

NAND

 


NOR

 

# Review: MOSFETS



nFET

 



pFET









GND

  


VDD

  

# MOSFETS

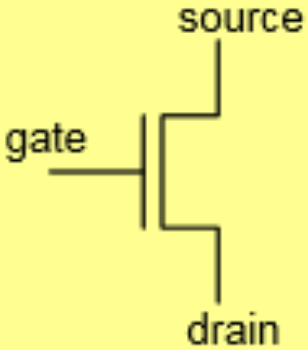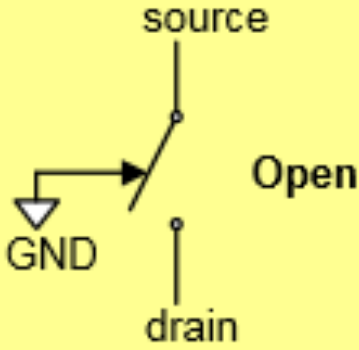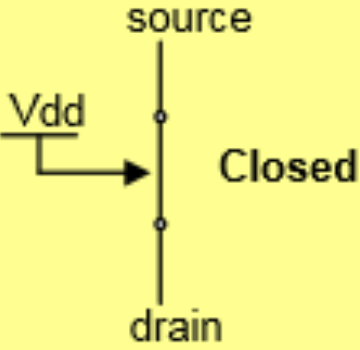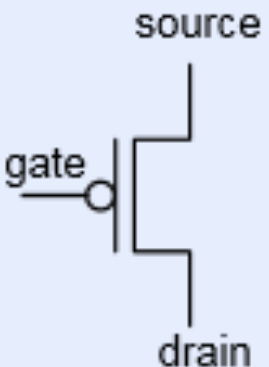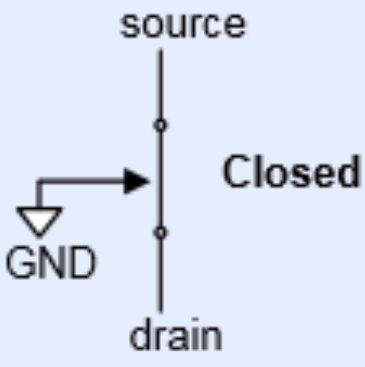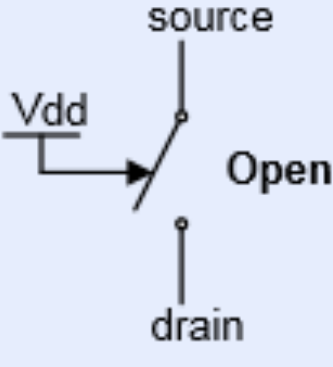	Symbol	$V_{gate} = GND$	$V_{gate} = V_{dd}$
<b>nFET</b>			
<b>pFET</b>			


# MOSFETS

 




# Correction: nFET vs. pFET

## n-type & p-type MOSFETs

 



**nMOSFET**  
Electron conduction

 

**pMOSFET**  
Hole conduction





# FET Delay

  

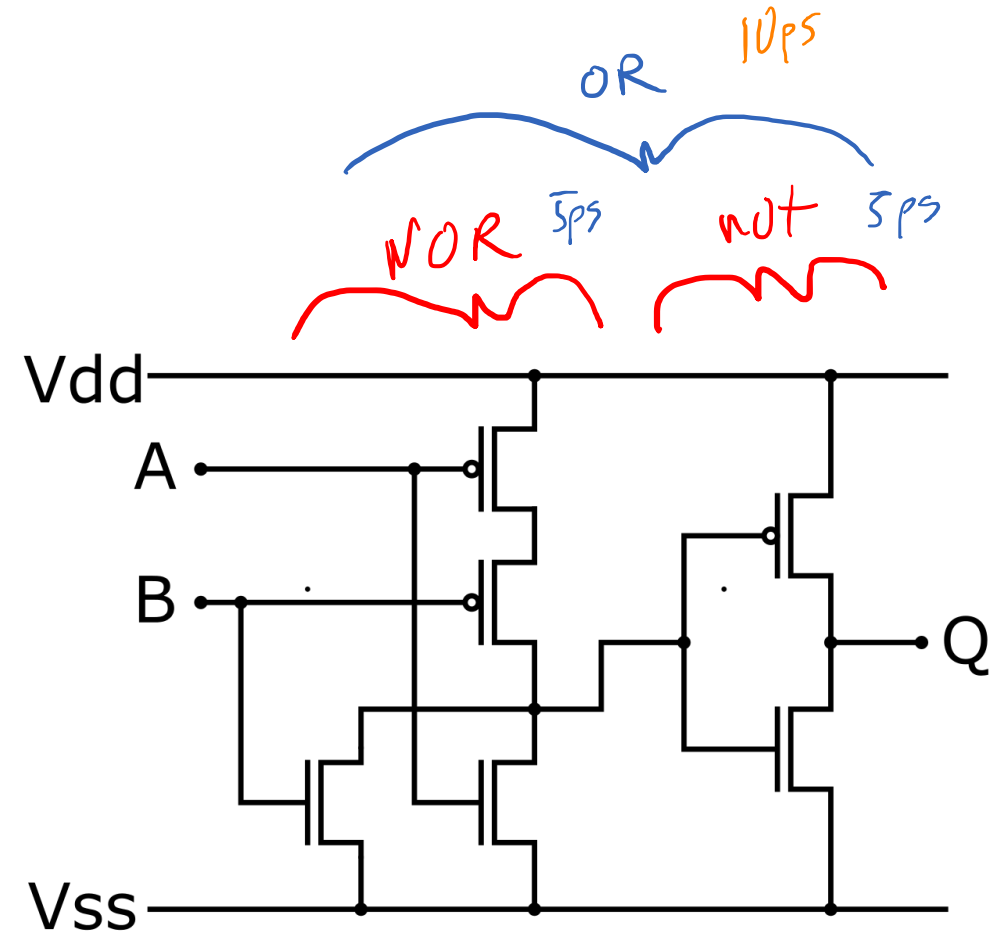 
# Gate Timing

- Assume 5ps / MOSFET  
*NAND  $\approx 5ps$*





# Flip-Flop Timing

- Assume 5ps/ MOSFET

 


# Setup Time Problems

- Assume 5ps/ MOSFET

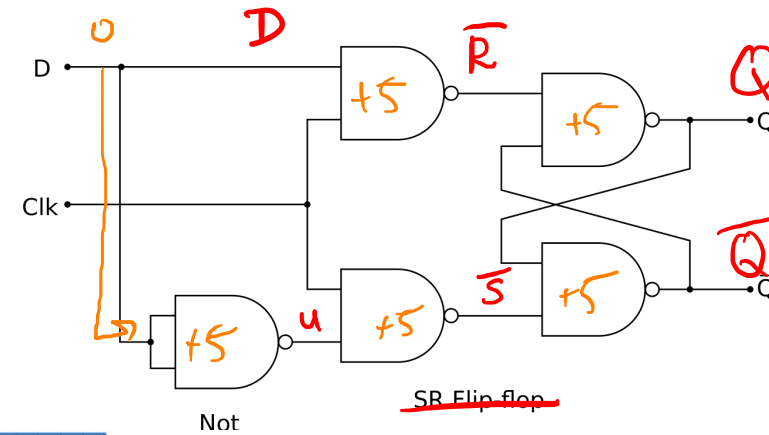 

Screwed  
this  
up  
redo  
next  
time...


# Glitch

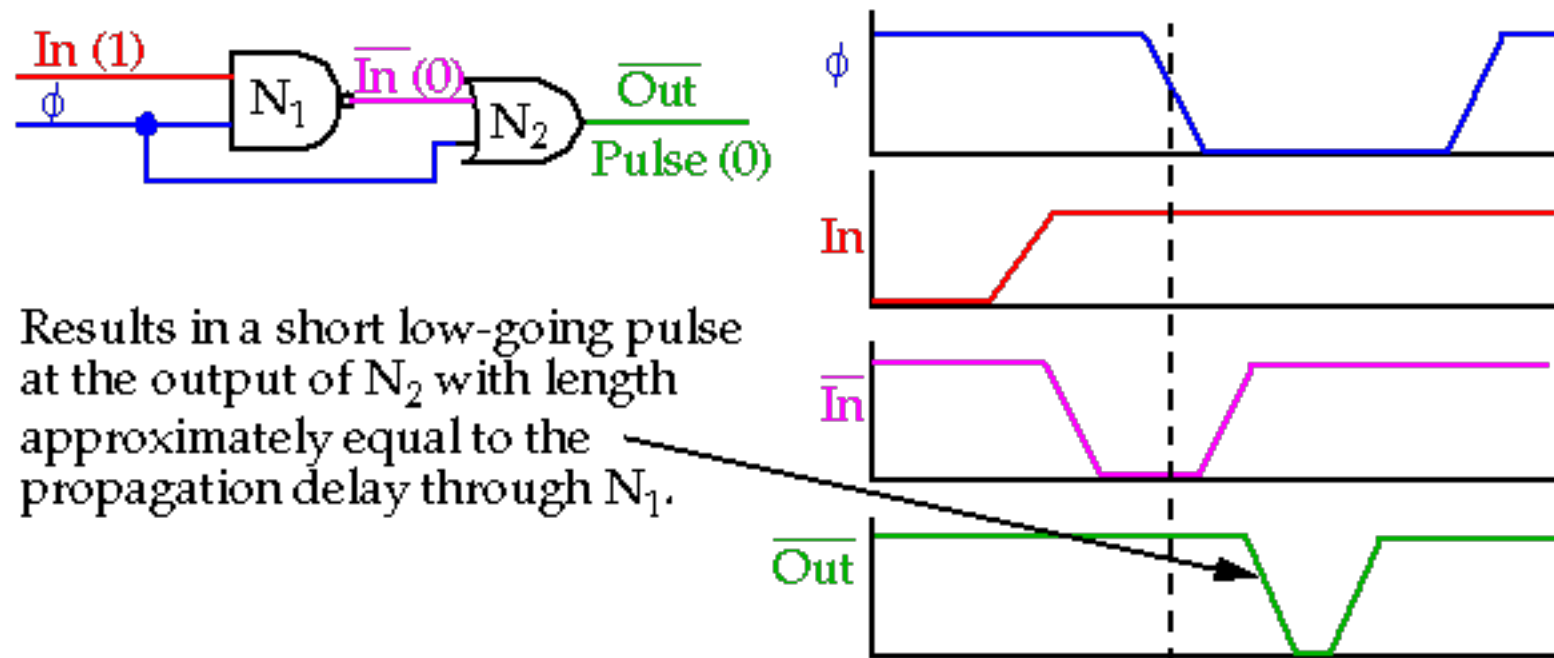

# Setup and Hold Time


- **Setup Time:** minimum time the inputs to a flip-flop must be stable before the clock edge
- **Hold Time:** minimum time the inputs to a flip-flop must be stable after the clock edge

# Setup Time

 







# Hold Time

 

# Setup/Hold Time

 

# Inter Flip-Flop Timing

   

# Inter Flip-Flop Timing

Register to register timing:


- output of a register  $Q1$
- some combinational circuit
- input to the next register  $D2$

Delays:


- $t_{co}$ , clock to output delay,
- $t_{pd}$ , propagation delay in combinational circuit
- $t_c$ , clock period

Timing requirement:

$$t_{co} + t_{pd} + t_{su} < t_c$$

 


$t_c = \text{time clock}$

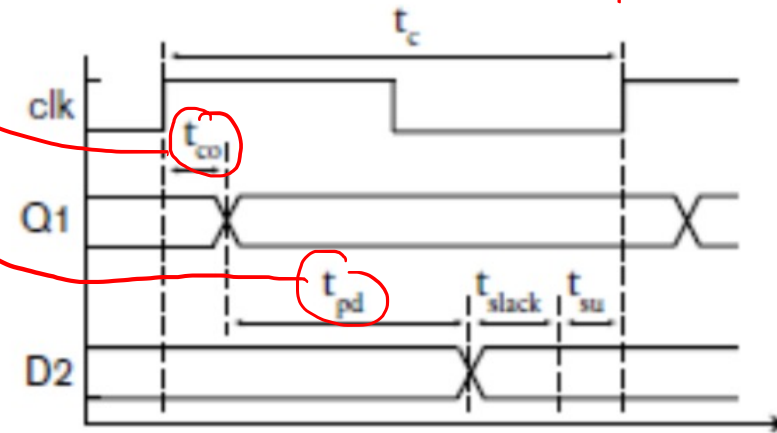

extra "Slack" time

Setup time

# Slack

 

- Extra time between combinational propagation delay and setup time
- ( Time between stable input and next clock edge)



- Vivado:
  - WNS: Worst-case Negative Slack
  - TNS: True Negative Slack







- If this number is  $<0$ , your circuit will (probably) not work
  
# Setup/Hold Times on External Signals


- What if I don't know when my signal will arrive?



# Out-of-Synchronization

   
 


# Synchronizers

 




# Metastability

  

meta stability: not 0, not 1, it's  $\frac{1}{2}$

# Synchronizers for Metastability

 

# Next Time

- Binary Multiplication
- Pipelining